

THE ELECTRONICS & COMPUTER MAGAZINE

FEBRUARY 1998

£ 2.75

FREE SUPPLEMENT

PC
TOPICS

STAGE LIGHTS CONTROL
WITH DMX512


80C32

80C32
BASIC CONTROL
COMPUTER


VFO
STABILIZER

AVC
FOR PCs




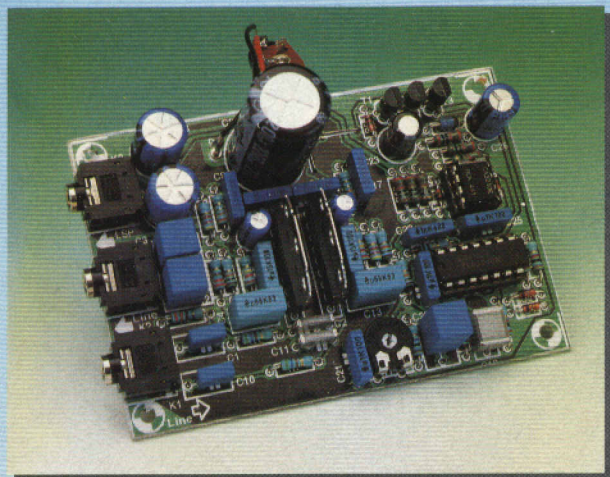

AVC for PCs 24

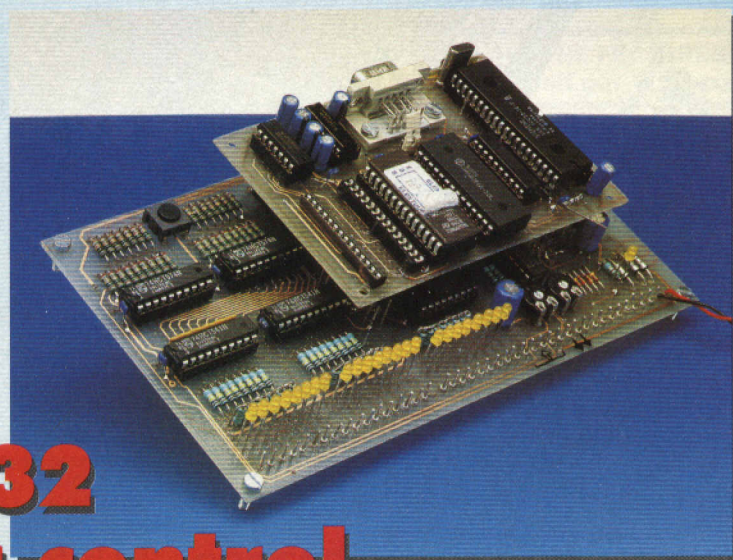

30 80C32 BASIC control computer

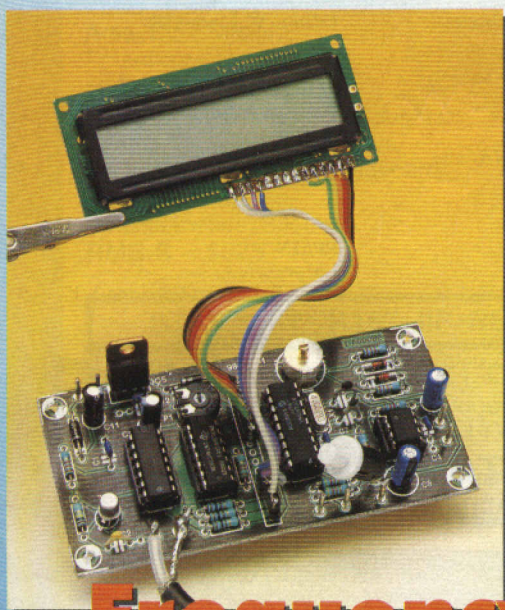

18 Frequency display & VFO stabilizer

CONTENTS

February 1998 Volume 24

Number 263 ISSN 0268/4519

FREE 16-page SUPPLEMENT

PC Topics
Centrefold

APPLICATION NOTE

- 48 AM/FM antenna impedance matching IC
A Temic Telefunken Application

AUDIO & HI-FI

- 24 PROJECT: AVC for PCs
☆☆ Design by T. Giesberts

COMPUTERS & MICROPROCESSORS

- 30 PROJECT:
☆☆ 80C32 BASIC control computer
Design by H.J. Böhling

FOCUS ON

- 52 Stage lighting control
By our Editorial Staff

GENERAL INTEREST

- 40 Introduction to Digital Signal Processing (2)
A six-part course
56 PROJECT: Functional trinket
☆☆ Design by T. Giesberts

MUSIC & ELECTRONICS

- 36 PROJECT: Simple electronic metronome
☆☆ Design by F. Hueber

RF TECHNOLOGY

- 18 PROJECT: Frequency display & VFO stabilizer
☆☆ Design by Eamon Skelton, E19GO

TEST & MEASUREMENT

- 12 PROJECT: JFET tester
☆☆ Design by M. Frankowski

MISCELLANEOUS INFORMATION

- 69 Data sheets: MCS-51 basic
11 Electronics now
39 Electronics on line: No more peeping
Toms on the Internet
74 Index of advertisers
45 In passing ...
59 New books
72 New products
74 Next month in Elektor Electronics
64 Readers' services
73 Switchboard

Copyright © 1998 Segment BV

A B C
AUDIT BUREAU OF CIRCULATIONS
CONSUMER PRESS

WEB SEARCHER IS A 'WORK OF ART'

A computer program that surfs the Internet has been launched as a work of art and even has the backing from the Arts Council of the United Kingdom.

Three artistic computer 'whiz-kids' have created the Internet surfing program that they say offers a new perspective on the World Wide Web.

The 'Web Stalker', as its creators call it, is completely different from other program – known as browsers – used to surf the Web. The Web Stalker provides users with 'a fast and high-profile trip' to the Internet.

It offers users a new way to explore the Internet by creating a dynamic map of web sites that people can use to explore new sites and see how they link to each other.

At the moment, the program only offers simple text-only Web browsing, but soon it will be able to handle pictures and other multimedia as well, said one of the programmers.

The Arts Council is sufficiently impressed with the project to make a small grant of several thousand pounds sterling to support it.
Escape Ltd, 42 Clink Street Studios, Soho Wharf, London, United Kingdom SE1 9DG. Phone +44 (0)171 407 0659 e-mail: escapecommittee@compuserve.com Web site: <http://www.backspace.org/iod/>

SOFTWARE CHALLENGE FOR STUDENTS

Four British students with a talent for computer programming have travelled to Cape Town, South Africa, to take part in an international software challenge.

The group will take part in the ninth International Olympiad of Informatics, during which they will compete in a series of tough challenges for which they must write computer programs to solve particular problems.

The team was chosen from 67 United Kingdom schools that took part in the British version of the same contest. During this initial round, entrants had to devise a program that could play the board game, Othello, and another that could solve Ancient Egyptian arithmetic.

In the final last April, held at Christ's College at Cambridge University, the contestants had to write programs that could play

chess, search for text, solve a three-dimensional maze or create a crossword puzzle, all within a time limit.

Rebecca Lloyd, Data Connection Ltd, 100 Church Street, Enfield, United Kingdom EN2 6BQ. Phone +44 (0)181 366 1177. e-mail: recruit@datcon.co.uk Web site: <http://www.christs.cam.ac.uk/bio/>

STRESS OVERLOADS COMPUTER EXECUTIVES

Technical staff in information technology (IT) departments are becoming overwhelmed with information, leading to stress, according to a recent report.

An 'explosion' of information, from sources such as the Internet, is threatening to overwhelm staff, it warns.

The report from Sequent Computers claims that the very people building the digital revolution – the managers of corporate computer networks – are the ones coming under the most stress.

Among the survey's findings are that

- two thirds of IT directors think new projects are more risky than they used to be;
- 95 per cent think that the amount of information available will double in the near future;
- half believe their computer systems will not be able to cope with so much extra data;
- 65 per cent said increasing stress at work was affecting their private lives; 17 per cent said this was extremely significant.

Sequent Computers, Sequent House, Weybridge Business Park, Addlestone Road, Weybridge, Surrey, United Kingdom KT15 2UF. Phone +44 (0)1932 851 111. e-mail: kaxelby@firefly.co.uk

SUPERHIGHWAY PIRATES WARNING FROM WATCHDOG

A British High Court judgement against two businessmen, who bought Internet domain names that were similar to major business trade marks, has been welcomed by the Institute of Trade Mark Agents (ITMA) of the United Kingdom.

In a statement, Mr John Slater, president of the ITMA, said the ruling in the case backed what his organization had been saying for some time about domain names. Business should keep monitoring the Internet and

checking on possible uses of their trade marks by third parties.

"For a long time we have been warning of superhighway pirates registering domain names and then offering them back, at a price, to the owners of registered trade marks," he said.

"Companies that make the effort to register their trade marks have the right to see that protection extended into new technologies. I am delighted by the court ruling and hope it will dissuade unscrupulous 'dealers' from repeating the practice."

"However, business people should remain on their guard and continue to exercise vigilance in monitoring the Internet for similar infringements."

Recently, the High Court ruled that Richard Conway and Julian Nicholson, of One in a Million Ltd, should assign the domain names they had registered in other trade marks, such as 'marksandspencer.com' to the trade mark holder. The court also ordered that the two pay costs of about 60,000 pounds sterling.
ITMA, Canterbury House, 2-6, Sydenham Road, Croydon, Surrey, United Kingdom CR0 9XE. Phone +44 (0)181 686 2052. Web site: <http://www.itma.org.uk/>

MAKING THE COM- PUTER INDUSTRY 'MORE ATTRACTIVE'

School leavers and graduates still see the computing and information technology (IT) industry as one for 'nerds', said a senior executive of a United Kingdom computer company recently.

Alan Stevens, chief executive of the computer services company EDS, was speaking on the day he took over the chairmanship of a body dedicated to cultivating training and developing new blood for the IT industry.

"It is up to us to persuade young people that it is not nerdy," he said. "The image of the industry is not good in terms of being an attractive place to work, especially for women."

Mr Stevens took over as chairman of the National Training Organization (NTO), an independent IT body supported by business. NTOs have been established in various industry sectors and they attempt to research patterns of demand in the labour market and match education and training to that demand.

"The UK IT industry is a strong and thriving one, especially

in the area of software development. But we need to attract more good people. It is quite clear that the industry needs to get a grip on this problem and fix it."

Sarah Scales, Hill and Knowlton PR, 5 Theobald's Road, London, United Kingdom WC1X 8SH. Phone +44 (0)171 413 3138; fax +44 (0)171 413 3216.

BIGGEST EVER CATALOGUE FROM TANDY

Britain's largest high-street retailer, Tandy, has launched its biggest ever and best ever catalogue, with 500+ pages packed with thousands of products.

The catalogue contains radio controlled boats and planes, night vision binoculars, a huge range of mobile phones and accessories, and replacement remote controls for virtually any TV or VCR.

By including a host of articles, from telescopes and electronic chess games to the wacky world of metal detectors, the catalogue caters for the whole family. To entertain youngsters, parents will find the catalogue containing Star Wars and Barbie walkie talkie sets, as well as dozens of powerful remote control cars starting at £9.99 for the Breeze Runner, rising to £399.99 for the Mercedes DMT. The catalogue also shows a wide range of specialist electronic components for which the company is renowned.

A new feature is Tandy 'Unlimited', which offers customers a mail order facility to products contained exclusively in the catalogue. By doing so, Tandy has supplemented the range of products available in their 340 high street stores, so giving customers access to increasingly unusual and state-of-the-art technology.

Using the catalogue, customers can simply order any item from the Tandy 'Unlimited' range by post, fax or phone, or simply by going into their nearest store. The product is then dispatched in 48 hours with just a nominal postage and packing charge.

The catalogue is available for £1 from all Tandy stores and includes £25 worth of redeemable vouchers.


Customers can also benefit from the 'Repair Shop at Tandy', which will repair a wide range of electrical items, whether or not they come from Tandy.



JFET tester

FET matching and testing made simple

Many designers shy away from using JFET transistors although numerous circuits would benefit from using these devices. Whenever very high input impedance, high operating frequency and relatively low noise are paramount design requirements, a JFET may be a good choice. This article aims at removing some of the general hesitation about using JFETs by describing a simple tester that allows you to measure two crucial electrical parameters of these devices.

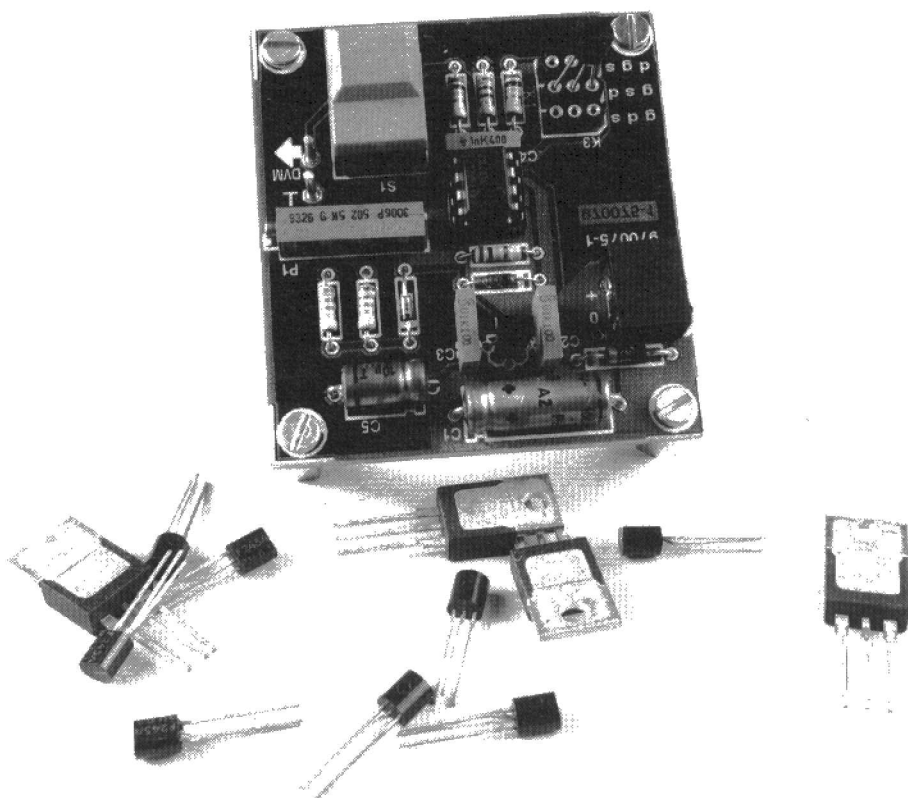

Although the staggering amount of data you can obtain from a FET's datasheet may cause the odd apoplectic fit with some of you, it can be upheld that there are two absolutely vital selection criteria (or 'electrical parameters') which help to identify an unknown JFET, or find so-called *matched devices* from a batch of JFETs (more about this further on).

The present tester is only suitable for *n-channel* small-signal JFETs (junction field-effect transistors). This does not detract from its usefulness however because chances are pretty small that you will ever encounter a p-channel JFET in your lifetime!

MEETING THE JFET

Although most of the background theory relevant to JFETs may be found in any reasonable electronics textbook, it may still be useful to present a brief recap in this article.

The circuit symbol of the n-channel JFET is shown in the basic connection diagram in **Figure 1**. The in-going arrow at the G (gate) denotes the n-

channel version. Although the symbol of a JFET is different from that of a bipolar transistor, it may help you think of the D (drain) electrode as the collector, the S (source) electrode as the emitter, and the G (gate) electrode as the base. Unlike an n-p-n transistor, however, the operating range of the parameter called 'gate-source voltage' (V_{GS}) is negative. In other words, the gate is made negative with respect to the source.

Now, let's first take a moment to explain the notation of the various parameters symbols you will find in the datasheets and this article. The above example, V_{GS} , should be read as follows: *Voltage* (V) between *Gate* and *Source* (GS). Note that the *index* 'GS' is printed smaller and lower than the capital letter V. Similarly, the symbol I_D means 'current (I) in drain (D) channel', and V_{DS} means 'voltage (V) between drain (D) and source (S)'. Once you are comfortable with the basics of this notation system, you will have little difficulty in unravelling the meaning of the various symbols used

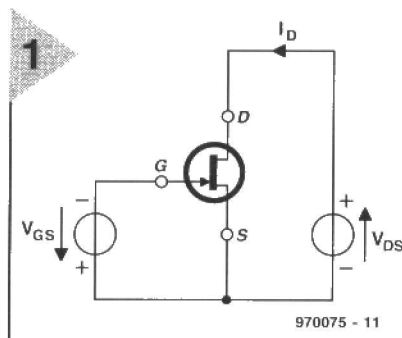


Figure 1. Basic JFET connection circuit.

to describe the electrical parameters of JFETs (and other transistors).

PINCH-OFF VOLTAGE

The first vital JFET parameter is called the *pinch-off voltage*, symbol $-V_{GS(p)}$ or simply $V_{(p)}$. Unfortunately, due to fabrication techniques, this parameter is subject to relatively large tolerance. In other words, the actual $-V_{GS(p)}$ spec of the JFET you have available may differ considerably from the value specified in the datasheets. The pinch-off voltage is the gate-source voltage at which negligible drain current flows. Hence the name: this voltage pinches off the current flow in the drain-source channel to virtually nought. The remaining current is due to leakage, and usually defined as 1 nA, 10 nA or even 10 μ A by the manufacturer. The pinch-off voltage is stated assuming that V_{DS} is held constant. Here, too, opinions differ: some manufacturers state $-V_{GS(p)}$ at $V_{DS} = 10$ V, others at $V_{DS} = 15$ V. It makes little difference, however, at long as you know that V_{DS} is a constant value, or nearly so. The JFET tester described here measures $-V_{GS}$ at $I_{DS} = 10$ nA, and does not use a constant voltage for V_{DS} . Yes, it can be done! Referring back to the graph in Figure 2, you can see that the I_D curve for values of $-V_{GS}$ approaching the $-V_{GS(p)}$ value (like $-V_{GS} = 4$ V) runs virtually straight from $V_{DS} = 2$ V onwards. In other words, I_D remains virtually constant as long as V_{DS} is between, say, 3 V and 15 V. So, the error caused by the non-constant value of V_{DS} in the test circuit is negligible, because V_{DS} is always in the range where I_D is virtually constant. That's why JFETs make great constant-current sources!

DRAIN SATURATION CURRENT

The second important JFET parameter is the value of the current through the drain-source channel when $-V_{GS}$ is at 0 V, and V_{DS} at 15 V (usually!). When these two conditions are satisfied, the drain current will remain practically constant at a certain maximum value. In other words, the drain-source channel is *saturated*; it will not pass more current. The symbol used for the drain saturation current is $I_{D(ss)}$. Like I_D , $I_{D(ss)}$ derates (worsens) with increasing temperature, as illustrated in Figure 3.

PRACTICAL CIRCUIT

Admittedly, that was rather a lot of theory to wade through. High time to discuss how the two measurements mentioned above are performed in practice. Let's look at the circuit diagram in Figure 4.

Pinch-off voltage measurement (S1 not pressed)

This measurement is performed when S1 is not actuated. The pinch-off voltage is indicated on the DVM (digital voltmeter) connected to the output of the tester. Imagine a JFET is inserted in the D.U.T. (device under test) sockets. A reference voltage of 100 mV is created with R1-D2-P1-R2, and connected to the non-inverting input of opamp IC2. The inverting input is connected to the positive supply rail by a 10-M Ω resistor (R3), as well as to the FET under test, which is included in the feedback path to the opamp output. Since the gate of the JFET is at ground potential, the voltage at the source is controlled to make the gate more negative than the source ($-V_{GS}$). Because the opamp will attempt to make the voltages at its inputs equal, it supplies a gain at which the voltage across R3 will equal 100 mV. Resistor R5 then drops 10 nA \times 100 k Ω = 1 mV. In this way, $-V_{DS}$ of the JFET is controlled until I_{DS} equals 100 mV/10 M Ω = 10 nA. The result is that $-V_{GS(p)}$ appears on the DVM. The error sources in this measurement are I_{D3} (10 pA), the input bias current of the TL071 opamp (<200 pA) and its input offset voltage (<10 mV).

Some JFETs have a pinch-off voltage between 0 and -2 V. To enable these devices to be tested also, a voltage regulator is used in the negative supply rail. By supplying the opamp

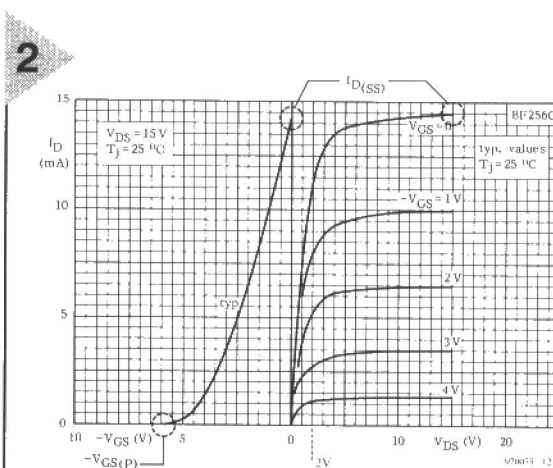


Figure 2. The pinch-off voltage $-V_{GS(p)}$ and the drain saturation current, I_D , are easily determined if you have a transfer characteristic graph like this available (example: BF256C JFET; source: Philips Components).

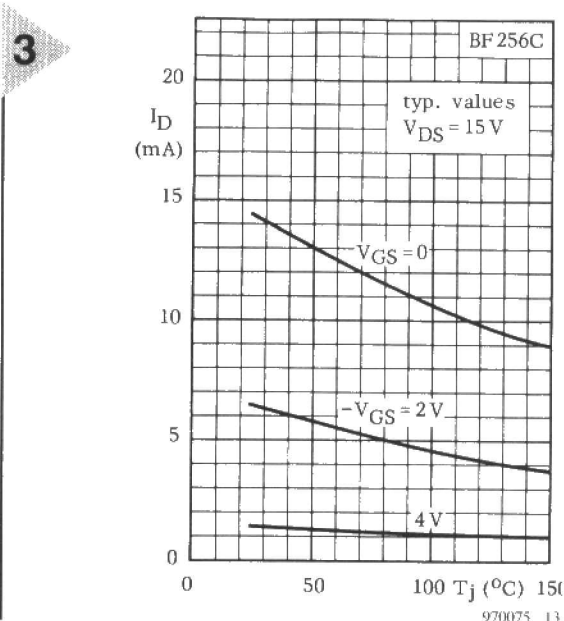


Figure 3. Drain current (I_D) derating as a function of junction temperature (T_j).

with 15 V rather than 12 V (as the rest of the circuit), the range of V_{GS} is extended to about +2 V.

Drain saturation current measurement (S1 pressed)

This is a much simpler measurement.

ULTIBOARD Studio
FOR PRIVATE USE AT £69
ULTIBOARD STUDIO LITE INCL. VAT

PROFESSIONAL HOBBYISTS:

The Studio Lite consists of ULTicap schematic capture, ULTiboard PCB design and ULTiroute GXR autorouter. Both Windows 95 and DOS versions are included in the CD-ROM. Actually you only pay for the 5 manuals! In which, besides tutorials and manuals, even shapes are described! Ideal for hobby and study and with sufficient capacity (500 pins). If higher capacity is needed you can opt (now or later) for an upgrade to the Studio Unlimited, without capacity limits, for £68 (incl. VAT). There are no further options or hidden extras, the ULTiboard Studio program is complete!

ULTIMATE TECHNOLOGY
Unit 1, Lodges Barn, Coxbury Lane,
St. Briavels, Lydney, Glos GL15 6QJ
phone: 01594-810100
fax 01594-810200

SEE ALSO THE ADVERTISEMENT ELSEWHERE IN THIS ISSUE

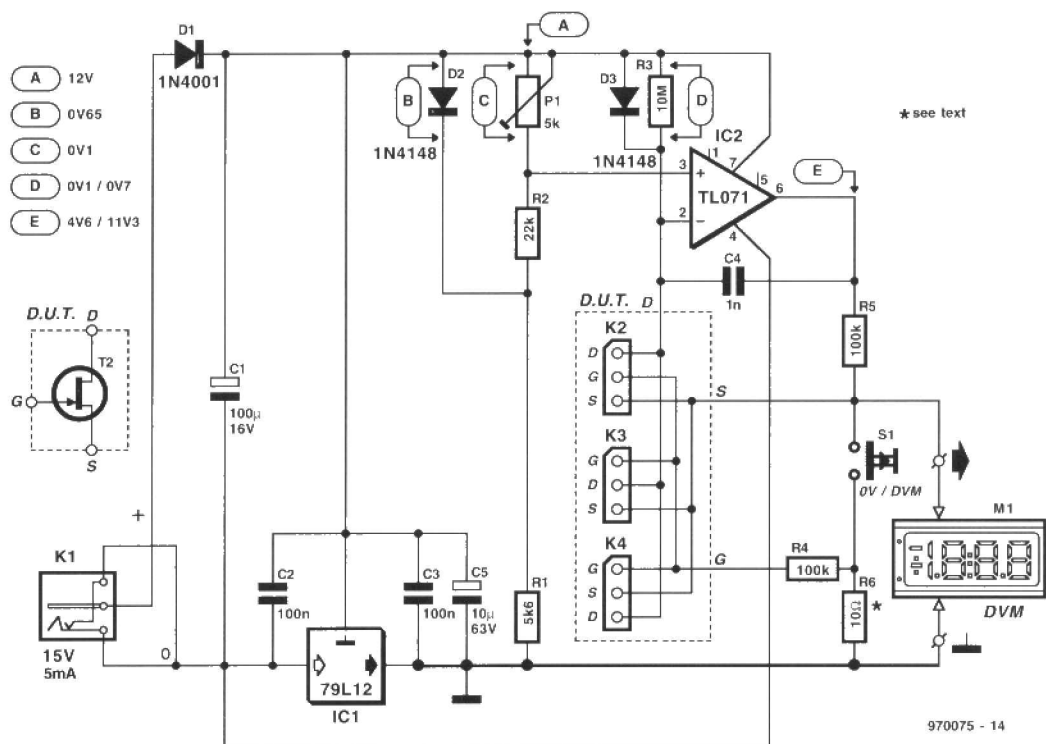


Figure 4. Circuit diagram of the JFET tester.

Pressing S1 causes the source to be connected to the gate, so that $V_{GS} = 0$ V. Although the reference voltage at the +input of IC2 remains 100 mV, D3 now drops its normal forward bias voltage of about 0.7 V. Consequently the opamp pulls its output to (practically) the positive supply level. Resistor R5 then carries $(12 - 0.7)$ V/100 k Ω or a little more than 100 μ A. This current also flows through R6, where it is added to the drain saturation current. As this will be in the mA region, the error is, we feel, insignificant for all practical intents and purposes.

Because R6 has a value of 10 Ω , the $I_{D(ss)}$ indication on the DVM is in (mA \times 10). Mind you, you are measuring a voltage that indicates a current! True, a value of 1 Ω would have been more logical because then the readout is simply in mA. A higher output voltage is used, however, to enable the DVM to be switched to a higher range with resultant higher accuracy (in general!). Owners of 4.5-digit DVMs may use a 1- Ω resistor in position R6. Whatever DVM you use, the accuracy of the tester will benefit from the use of a 1% (close-tolerance) resistor for R6.

The voltages indicated in the circuit are typical. The first voltage applies when S1 is not pressed, the second, when S1 is pressed. Unless otherwise indicated, measurements are with respect to the ground rail, i.e., the 0 V input of the DVM.

The circuit may be powered by an

inexpensive mains adaptor with an output voltage of about 15 VDC. Because the tester will only draw a few tens of mA when S1 is pressed to perform a drain saturation current measurement,

COMPONENTS LIST

Resistors:

R1 = 5k Ω
R2 = 22k Ω
R3 = 10M Ω
R4,R5 = 100k Ω
R6 = 10 Ω (1% if necessary)
P1 = 5 k Ω 10-turn cermet pre-set, vertical

Capacitors:

C1 = 100 μ F 16V
C2,C3 = 100nF
C4 = 1nF
C5 = 10 μ F 63V


Semiconductors:

D1 = 1N4001
D2,D3 = 1N4148
T1 = device under test (JFET)
IC2 = TL071CP
IC1 = 79L12

Miscellaneous:

M1 = digital voltmeter (DVM).
K2K3, K4 = 3 rows of 3 IC
socket pins, turned sockets.
S1 = Digitast press-key, 1
make contact (ITT-Schadow).
K1 = mains adaptor supply
socket, flat model.

Figure 5. Copper track layout and component mounting plan of the PCB designed for the JFET tester (board not available ready-made).

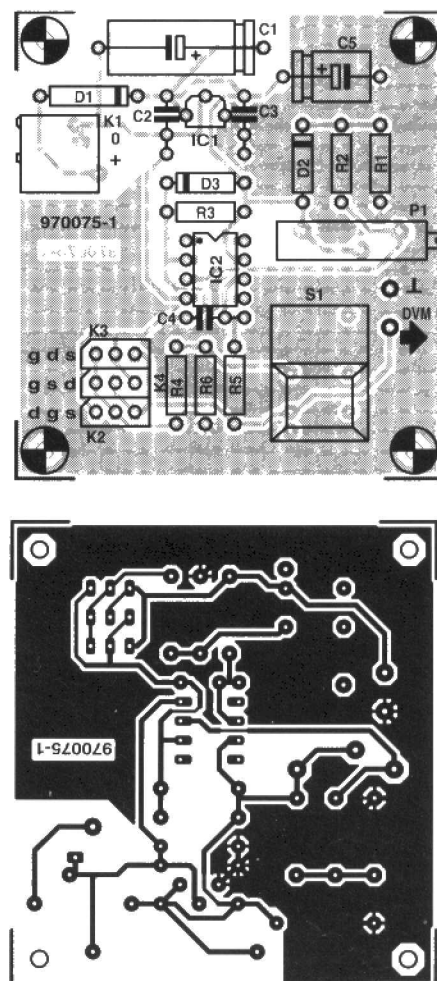

even very low power adaptors may be used. Any small adapter rated at 12 VDC should be suitable because it will typically supply at least 15 V when only a few milli-amps are drawn. When S1 is not pressed, the current consumption is about 5 mA.

CONSTRUCTION AND ADJUSTMENT

A ready-made printed circuit board is, unfortunately, not available for this project. The artwork to make your own board is, however, shown in Figure 5. Look carefully at the component overlay to make sure each and every polarized part is fitted the right way around. There are three D.U.T. sockets on the board to accommodate different pin-outs of the JFETs you want to test. Make sure you know the pin-out from a datasheet, else neither measurement will make any sense at all, and you may destroy the device under test.

Preset P1 is adjusted until it drops exactly 100 mV (use a 10-M Ω DMM for this adjustment).

Finally, a suggested front panel layout is shown in Figure 6.

HINTS AND KINKS

If you want to do some testing on known JFETs, we recommend the BF245 and BF256 series to start with. Another commonly used JFET (particularly outside Europe) is the 2N5486.

The highest drain saturation current that can be measured by the circuit is about 40 mA. If you see anything above this value on your DVM display, the measurement is probably not valid.


Take the internal resistance of your DMM into account when measuring the voltages indicated in the circuit; at some junctions, even 10 M Ω may be a relatively 'heavy' load.

MATCHING, WHAT'S IT FOR?

Some (audio) amplifier stages of the differential type use JFETs which have to be 'matched' for optimum performance. The two elementary tests carried out with the aid of the present tester should enable you to pick two JFETs with almost equal electrical properties from a batch of, say, ten.

(970073-1)

6

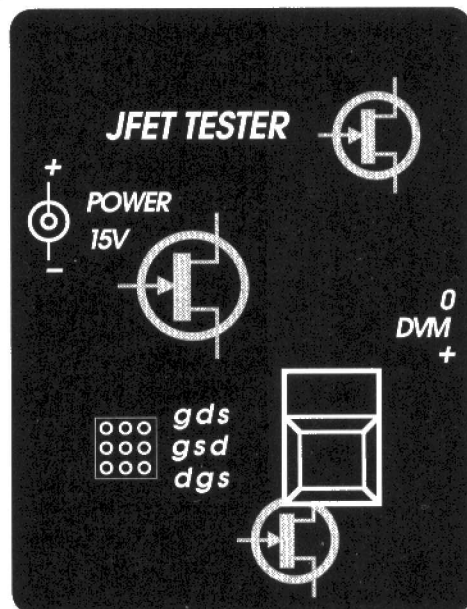

970075-F

Figure 6. Suggested front panel layout for the JFET tester.



IF AN ADVERT IS IN PRINT, IS IT PROPER?

Most advertisements are perfectly proper.

A few are not.

The Advertising Standards Authority not only monitors over 850 advertisements every month, it ensures compliance with the rules in the strict Code of Advertising Practice.

So when you question an advertiser, they have to answer to us.

To find out more about the role of the ASA, please write to the address below.

Advertising Standards Authority,
Department X, Brook House, Torrington
Place, London WC1E 7HN.



This space is donated in the interests of high standards in advertisements.

Great Sound is a work of art!

If you want to create your own great sounding works of art, Speaker Builder can show you how!



The publishers of *Speaker Builder* invite you to use your electronics know-how to explore the world of better sound. To subscribe, simply return this form with your payment or FAX your credit card order and receive 8 issues of *Speaker Builder* for a low introductory rate of \$45. That's a \$5 savings off the regular subscription rate. Or, double your savings and subscribe for 16 issues (2 years) at \$80 (that's \$10 off).

☐ \$45, 8 issues (1 year) ☐ \$80, 16 issues (2 years) ☐
Remit in US \$ drawn on a US bank only

MC / VISA NUMBER _____ EXP _____


NAME _____

STREET & NO. _____

CITY _____ COUNTRY _____ POSTAL CODE _____

Speaker Builder

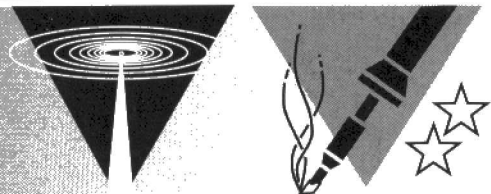PO Box 494 Dept. EUK5, Peterborough, NH 03458-0494 USA
Phone: (603) 924-9464 or Fax your order 24 hours a day to (603) 924-9467
Rates subject to change without notice.




Frequency display and VFO stabilizer

eliminates frequency drift in home-brew and 'surplus' HF receivers

One of the most frequent topics for discussion among the many 'Home Brewers' on the amateur bands is the difficulty of building a VFO that is stable enough to be used on all of the HF bands.

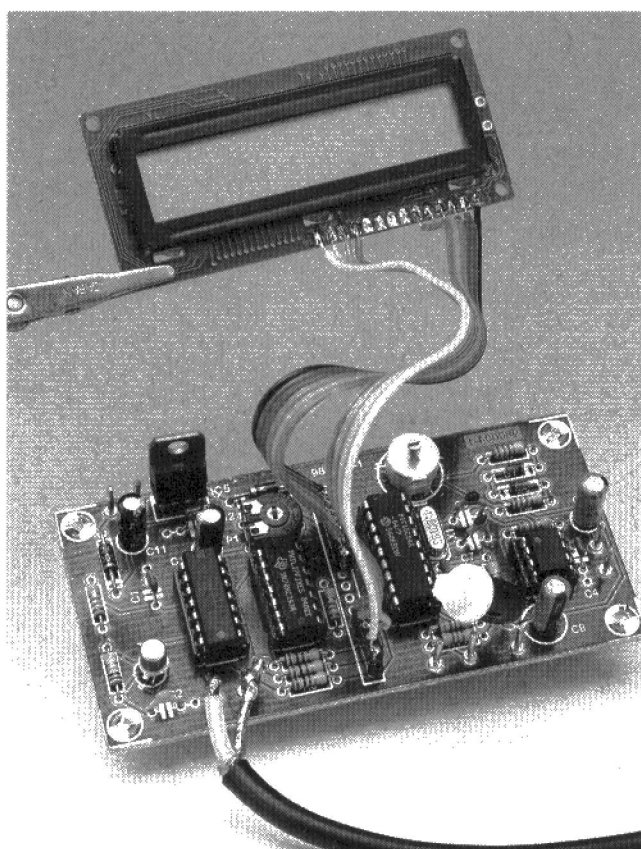The relatively simple circuit described here will stabilize the frequency of an HF VFO, and provide a digital frequency display. The display will allow for the different frequency offsets required for USB and LSB, and the fact that the VFO frequency may be above the signal frequency on some bands, and below it on others.



The circuit uses a microcontroller to count the frequency of an HF VFO (variable frequency oscillator), add or subtract the IF (intermediate frequency) offset, and display the signal frequency on a standard Hitachi intelligent LCD display module. The VFO frequency is stabilized by sending a correcting voltage to a varicap diode in the VFO. The circuit is based on a 'Huff & Puff' stabilizer that I have been using for several years.

The circuit design philosophy was to keep the hardware as simple as possible, and to use inexpensive and readily available components. This was made possible by using a microcontroller chip which was programmed to take care of most of the complex functions like counting, arithmetic, and dri-

ving the LCD display module. Two versions of the unit were built, one using the 8031 microcontroller, and this version using the PIC 16C54. I have tested the circuit at various frequencies between 8 MHz and 80 MHz.

CIRCUIT DESCRIPTION

The circuit diagram of the VFO stabilizer is shown in Figure 1. The circuit is basically a Frequency Locked Loop (FLL). As many of you will be aware, the PIC16C54 microcontroller is a complete computer on a chip with 512×12 bits of ROM, 32 bytes of RAM, a clock circuit, 12 I/O pins, a real time clock/counter, and several other useful features. For a full description of the PIC16C54 and its instruction set, see the Microchip data book or Microchip data sheet DS300151.

The RF signal picked up from the VFO is amplified and digitized by T1, then buffered by IC1b. The BSX20 is a fast switching transistor for use up to 200 MHz. The amplified signal is gated by IC1c and IC1d. A 100-ms gate pulse is generated by a software delay loop in the PIC. The square wave pulses from IC1d are counted by IC2 which is configured as an 8-bit counter.

The output of IC2b is connected to the RTCC input of the PIC through a 1.2kΩ resistor (R6). The PIC has a real-time clock/counter (RTCC) which can count pulses applied to the RTCC input (pin 3). The RTCC register is only eight bits wide giving a maximum count of 255. If the PIC's internal prescaler is set to divide by 256 the


maximum count is 65,535, effectively making a 16-bit counter. With a 1-ms gate time this would allow the counter to count up to 65.535 MHz but the resolution would be 1 kHz which is not good enough for our purposes.

The 74HC393 counter chip increases the count to 24 bits, or 16,777,215. With a 100-ms gate time this will allow a maximum count frequency of 167.77721 MHz and a resolution of 10 Hz, that is, if you can find logic chips that are fast enough. One problem with this arrangement is that it is not possible to read the least significant 8 bits directly from the 393 counter.

This problem is overcome by sending pulses to the counter input through gate IC1d. By counting the number of pulses it takes to make the counter overflow it is a simple matter to calculate the value in the '393 at the time the gate was closed. As the PIC internal prescaler can not be read directly, a similar method is used to calculate the value in the internal prescaler. Pulses are applied to the prescaler input by pin 13 of the PIC (RB7) until the prescaler overflows. The most significant 8 bits can be read directly from the RTCC register. This may seem like a strange way of reading the count but it is quite easy to implement in software and makes the circuit hardware very simple.

Now that we have the count result stored in the PIC, the IF offset must be added or subtracted; the result is the signal frequency in binary. This number is converted first to BCD, then to ASCII and finally sent to the LCD display module. A new count takes place about 9 times every second, the display is updated every second count, or just over 4 times a second. Updating the display more often than this causes the last digit to flicker, updating less often makes the display 'sluggish' when you tune quickly across the band. Before the first digit of the frequency is displayed a test is done to find out if it is a zero. If it is then a blank space is displayed instead, giving automatic leading zero suppression. Whether the IF offset is to be added or subtracted is determined by the state of the ADD/SUBTRACT (+/-) input, which is linked to an input pin on the PIC. Whether the offset is for USB (upper sideband) or LSB (lower sideband) is determined by the state of the OFFSET input pin. Suggested circuits for controlling the ADD/SUBTRACT (+/-) and OFFSET inputs are shown in Figures 2 and 3 respectively. Mind you, these are just examples, the exact configuration of the switches depends on the requirements of your HF receiver.

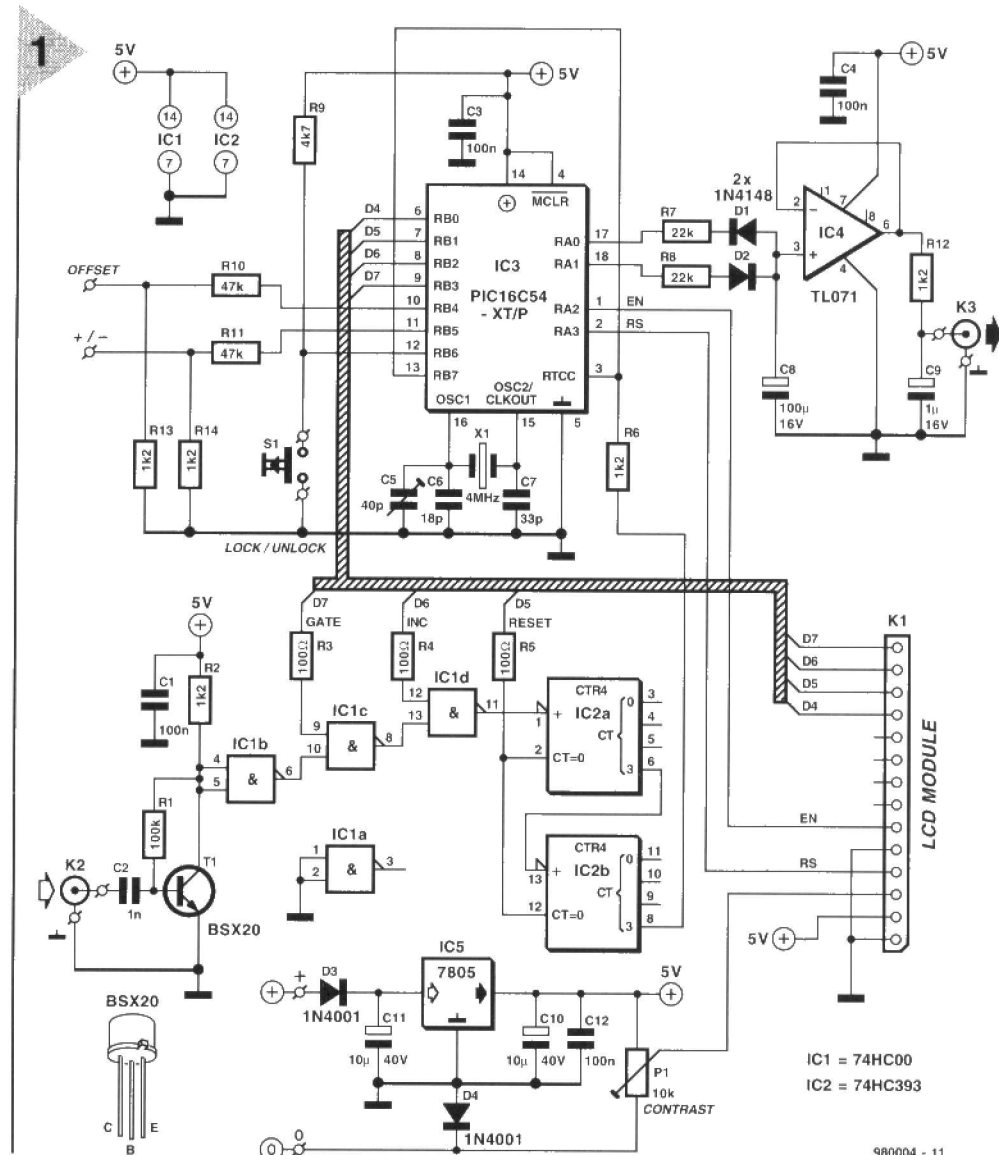So far the circuit is just acting as a frequency counter and display. At the



980004 - 11

Figure 1. Circuit diagram of the Fre-frequency Display and VFO Stabilizer.

end of each count/display cycle, the counters are reset and the cycle is repeated again. No attempt is made to control the frequency of the VFO. The control voltage at the output of the integrator is set at about 2.5 volts and remains there until the LOCK/UNLOCK button, S1, is pressed.

HOW THE VFO IS CONTROLLED

When you find a frequency that you want to stay on, press the LOCK/UNLOCK button. After the button is pressed there is a 100 ms delay, then the result of the most recent count is stored in three registers in the PIC. The result of all subsequent counts are compared with this value. If the current count is less than the stored value, the VFO has apparently drifted lower in frequency; a positive pulse is sent to the integrator (IC4) to correct the error. If the current count is greater than the stored value then a negative correction pulse is generated.

The width of the correction pulse depends on the degree of VFO drift. If the error is less than 10 Hz then a very short pulse of about 2 ms duration is generated. Greater frequency errors result in longer correcting pulses: 20 Hz = 4 ms, 30 Hz = 6 ms, 40 Hz = 8 ms and so on. This results in much tighter control of the VFO than can be achieved with a conventional 'Huff and Puff' circuit.

When the circuit is in locked mode, the LCD display readout changes: 'MHz' disappears from the display and is replaced by the 10-Hz digit. To the right of this is the error level display which is shown as E0 to E9. E0 means that the error is less than 10 Hz, E1 is an error level of 20 Hz, E9 is an error level of 100 Hz. If the error level is greater than 9, a '9' is still displayed. The last character on the display is the correction direction indicator: '>' indicates a positive pulse, '<' indicates a negative pulse. A low error level indication of 0 or 1 and a continuous rapidly alternat-

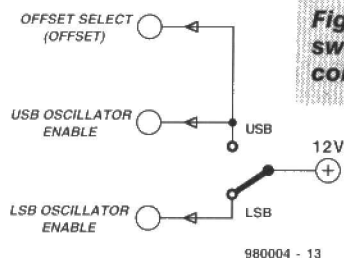


Figure 2. Suggested method of switching the ADD/SUBTRACT (+/-) control input on the board.

'MHz'. To lock to a new frequency simply press the LOCK/UNLOCK button again.

THE PROGRAM

Various interesting options are available as regards the control software which resides in the PIC microcontroller. To enable you to make your choice, we first tell you what's available for this project, and then make an important statement.

The items available for this project are (1) a **ready-programmed PIC** (for 10.7 MHz IF), (2) a **ready-made PCB** and (3) a **diskette** containing the **source code files** for the PIC control program. For prices, order numbers and other relevant information, please refer to the Readers Services pages elsewhere in this issue.

And now, a serious note. Although this frequency display/VFO stabilizer

ing up/down indication means that all is well, and the VFO frequency is within the control loop bandwidth of the system.

The varicap diode control of the VFO should be arranged so that the maximum frequency change is approximately ± 3 kHz. This should be sufficient range to keep a moderately stable VFO locked for hours or even days!

When you need to change frequency, press the LOCK/UNLOCK button again. This puts the device in unlocked mode, the integrator output is set at 2.5 volts and the display changes back to 6 digits followed by

is fairly easy to build, you should realize that *considerable experience may be required to establish the link with the VFO in your receiver*. Before building this project, you should, therefore be positive about the following points

1. The receiver is a heterodyne (mixer) design. The VFO frequency is between 8 and about 80 MHz.
2. The VFO has varicap control allowing a tuning range of ± 3 kHz to be produced by a control voltage swing of 5 V (2.5 V = centre tuning).
3. The VFO signal can be 'tapped' in a safe way (preferably by inductive coupling) and has a level of at least 100 mV_{pp}.

Most experienced radio amateurs (and not only those who actually transmit!) will be able to come to terms with these conditions, if necessary with the help of a fellow ham.

Back to your options! Here's what you can do.

1. I have a receiver with an IF of 10.7 MHz.

Simply order the PCB, the ready-programmed PIC and the source disk supplied through our Readers Services.

2. I have a receiver with an IF other than 10.7 MHz.

Order the PCB (980004-1) and the source code disk (986006-1) as separate items. Purchase a PIC16C54, and get hold of an assembler and a PIC programmer. Edit the source code as explained in the README file, and then program your own PIC.

3. I have a receiver with an IF of 455 kHz or 7.8 MHz.

Do the same as under 2. The necessary files are on the disk.

4. I can make my own PCBs and program my own PICs.

Order the diskette only (986006-1). Make your own PCB using the artwork shown in this article. Burn your own PIC for the IF you require. Tell your friends about it.

A PIC programmer can be built from one of the many published designs, or a commercially made unit can be purchased from one of several companies advertising in this magazine. The source code file on disk may be edited using any ASCII word processor. Details on modifying the IF offset are also available. Examples are available for 10.7 MHz, 455 kHz and 7.8 MHz.


CONSTRUCTION

If you use the PCB layout shown in Figure 4 and a ready-made board, construction of the circuit is fairly easy. Check the orientation of all polarized components (electrolytic capacitors, diodes, ICs, transistor T1). Use sockets

Huff and Puff

Although this circuit is generally referred to as the 'huff and puff' stabilizer among English-speaking hams, it should really be called the PA0KSB VFO stabilizer after its inventor, the Dutch radio amateur Klaas Spaargaren, PA0KSB. The circuit can act as an outboard enhancement with any reasonable VFO, keeping the output frequency stable within a couple of hertz without adding parasitics and other whistles to the VFO output.

A crystal oscillator, whose output frequency need not be a round value, is followed by a divider cascade which opens a gate for, say, 1 second. Next, a binary counter counts the VFO cycles within this gate period. On closing the gate, the last counter digit is compared to '8'. If it is smaller, the 2³ output of the counter is reset to 0. If it is greater, the output is made logic 1. The counter output is applied to a D-bistable. If the gate signal drops to 0, the first one-shot is triggered. Next, the second one-shot clocks the 1 or the 0 into the D-bistable. Finally, counter is reset by the third one-shot. If the counter signal was a 0, the \bar{Q} output of the bistable goes high, charging the capacitor and so causing the VFO frequency to go up. By contrast, a counter signal of 1 causes the frequency to go down. In this way, the VFO frequency 'puffs' at a rate of a few hertz around the stabilization point at which the counter detects an '8' as the last digit. Over the years, the basic design by PA0KSB was enhanced and followed by several variants using a raster of about 40 Hz, allowing virtually continuous tuning.

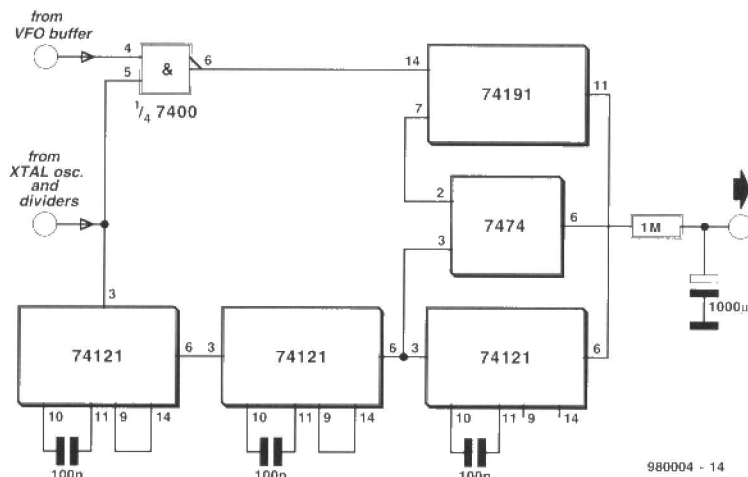

3

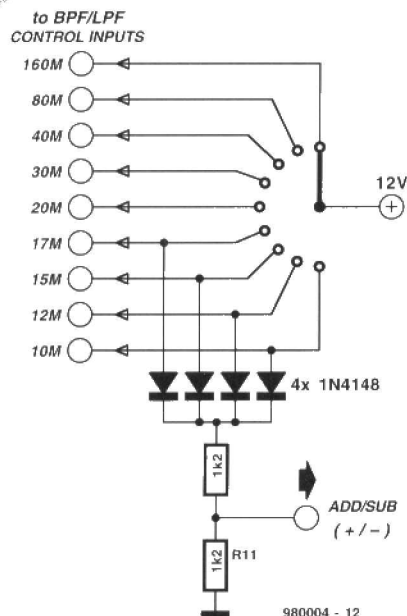


Figure 3. Method of switching the OFFSET select input on the board. Note that USB/LSB selection is only required on SSB receivers.

ues shown in the circuit diagram worked fine with several 4-MHz crystals from the author's junkbox. If the crystal you are using requires different capacitor values it may be necessary to change the value of C6.

In the author's HF transceiver, the circuit was put in a small box made from copper clad glass fibre board, this box was mounted on top of the VFO. The RF input and control output connections were made with miniature (RG174 or similar) coaxial cable. A short length of ribbon cable is used to connect the LCD module to the PCB. The OFFSET select input may be connected to the USB/LSB switch on the front panel of the rig. The ADD/SUBTRACT (+/-) input may be connected to the band switch of the rig using four diodes (see Figure 2). If you only need to subtract the IF offset, you can connect the add/subtract (+/-) input to ground.

(980004-1)

for the ICs if you want to experiment with different logic IC families, LS, ALS, HC etc. If you use 74HC or 74ALS series chips for IC1 and IC2 it will not be necessary to have a heat sink on the 5-V regulator. The circuit was tested with HC ICs, and worked reliably up to about 50 MHz. Higher input frequencies should be possible if you use ALS ICs.

The type of opamp used for IC4 is quite critical, the ADOP07CN gave very good results. If you do not have an ADOP07CN available, the TLO71CN also works quite well.

THE DISPLAY

Any general-purpose 1-line 16-character display that uses the Hitachi HD44780 chip should be suitable (the author used a type 16166 LCD display module). Some of these displays have LED or electroluminescent backlighting built in. Do not spend large sums of money on these displays, they are often advertised for less than £5.00.

TESTING

When the unit is first powered up, adjust preset P1 for best contrast on the LCD display. Connect your VFO to the input (C2), set the ADD/SUB input high to add the IF offset, or low to subtract the IF offset. Set the OFFSET switch for USB (high) or LSB (low). The display should show the approximate frequency of the VFO plus or minus the IF offset.

The best way to calibrate the counter accurately is to tune your receiver to a frequency standard signal or a station of known frequency accuracy, then adjust C5 until the displayed frequency is correct. The capacitor val-

Components list

Resistors:

R1 = 100 kΩ
R2, R6, R12, R13, R14 = 1kΩ
R3, R4, R5 = 100Ω
R7, R8 = 22kΩ
R9 = 4kΩ
R10, R11 = 47kΩ
P1 = 10kΩ preset H

Capacitors:

C1, C3, C4, C12 = 100nF
C2 = 1nF
C5 = 40pF trimmer
C6 = 18pF ceramic
C7 = 33pF ceramic
C8 = 100μF 16V radial
C9 = 1μF 16V radial
C10, C11 = 10μF 40V radial

Semiconductors:



D1, D2 = 1N4148
D3, D4 = 1N4001
T1 = BSX20
IC1 = 74HC00 (see text)
IC2 = 74HC393 (see text)
IC3 = PIC16C54-XT/P (order code 986502-1)
IC4 = TL071CP
IC5 = 7805


Miscellaneous:

X1 = 4 MHz quartz crystal
S1 = push-button, 1 make contact
K1 = 14-way SIL header
LCD module 1×16 characters
PCB only, order code 980004-1
Disk only, order code 986006-1
PIC only, order code 986502-1

Figure 4. Copper track layout and component overlay (board available ready-made through the Readers Services).

4

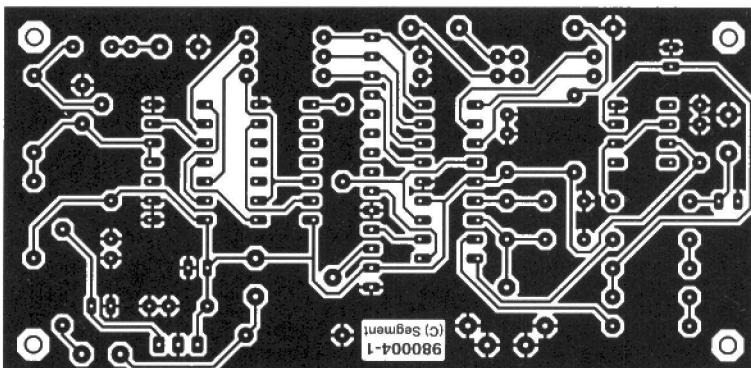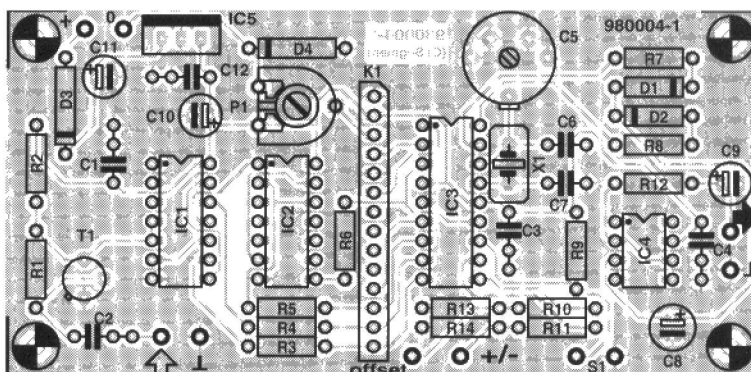

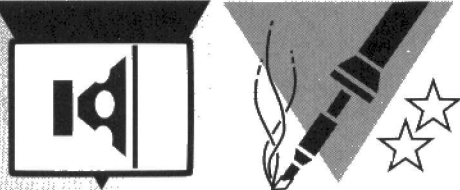


AVC for PCs

limits differences in sound level

An annoying phenomenon (not restricted to PCs) is that each and every programme that produces sound does so at a different level.

This means almost constant adjustment of the volume control to ensure audibility of one programme and protection of the ear drums with another one. The control circuit described in this article is designed to obviate this nuisance: it constantly monitors the signal even at the output of the sound-card and adjusts it when required. Use of the circuit is not restricted to PCs; it may also be used as a dynamic limiter in existing audio equipment.

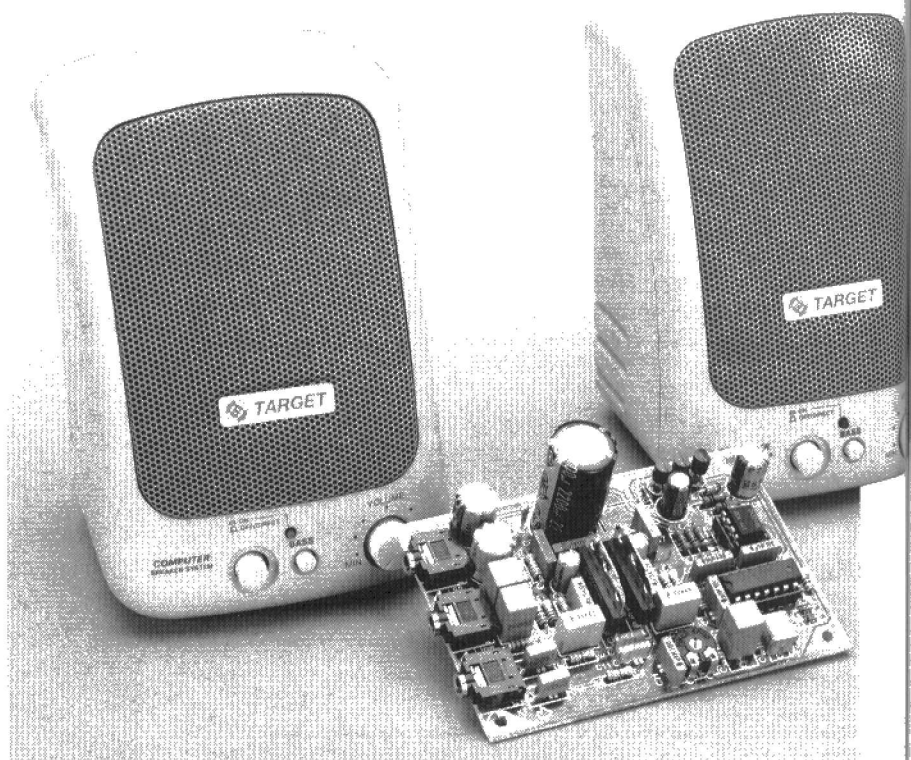

Brief specification

Power output	1.2 W
Maximum input	1 V
Compression	10:1
Supply line	12 V, 6 VA
Output load	8 Ω (LSP); 10 k Ω (line)
Input sensitivity	280 mV (gain line in to out = 0 dB; distortion at output = 1%)
	120 mV (gain line in to out = max; distortion at output = 1%)
Line in to LSP out (input voltage = 200 mV)	
THD+N	0.25% (2×0.5 W)
Signal-to-noise	70 dB for 0.5 W output at maximum gain
Channel separation	>45 dB

Line in to line out (input voltage = 200 mV; no loudspeaker connected)	
THD+N	0.047%
Signal-to-noise	80 dB
Channel separation	>73 dB

Design by T. Giesberts

In general, the signal levels in current audio equipment are equalized and standardized (although there are still some exceptions). Software manufacturers do not seem to know or care about this. Anyone who has ever opened two different sound programs will know of the quite different levels various effects often have. This is obviously an annoying situation and one which makes the constant adjusting of the volume control a necessity.

The present circuit offers a solution to this problem. It consists of a dynamic compressor with a control range of 10:1 which ensures that very loud and very soft sound passages are attenuated or amplified respectively. This results in a much narrower dynamic range of audio signals which makes adjusting the volume control a much less frequent necessity. It proves that something that appears difficult in software can be easily achieved by a small electronic circuit.

volume control (AVC) circuit is shown in Figure 1. The stereo audio signal at the output of a sound card used in a multimedia PC is applied to the line input. The active part of the circuit consists of two integrated amplifiers that contain a variable preamplifier and a compact output amplifier.

The signal from the output amplifier is freed from any direct voltage and then applied to a discrete rectifier. After the rectified signal has been processed, it is used to control the amplification fac-

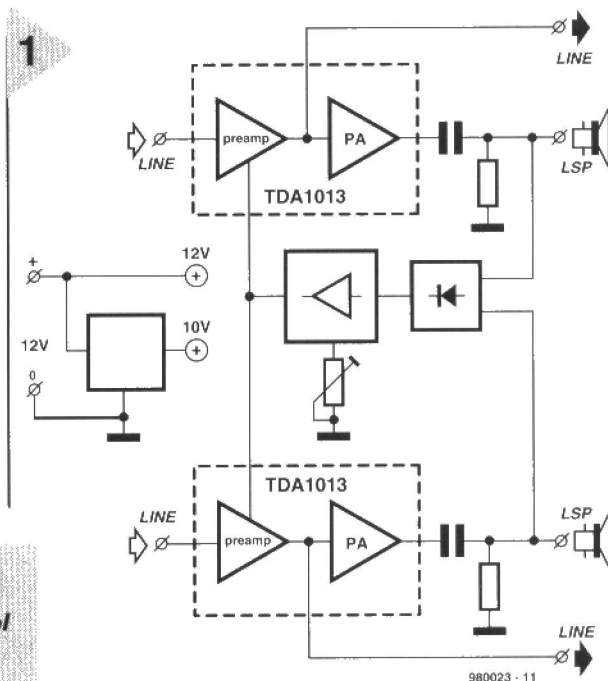


Figure 1. Block diagram of the automatic volume control circuit for PCs.

DESIGN

The block diagram of the automatic

tor of the preamplifiers. The control circuit is based on a number of discrete operational amplifiers. The design is an OR-type, so that the

sound channel (lefthand or righthand) with the highest peak signal level determines the amplification factor of

2

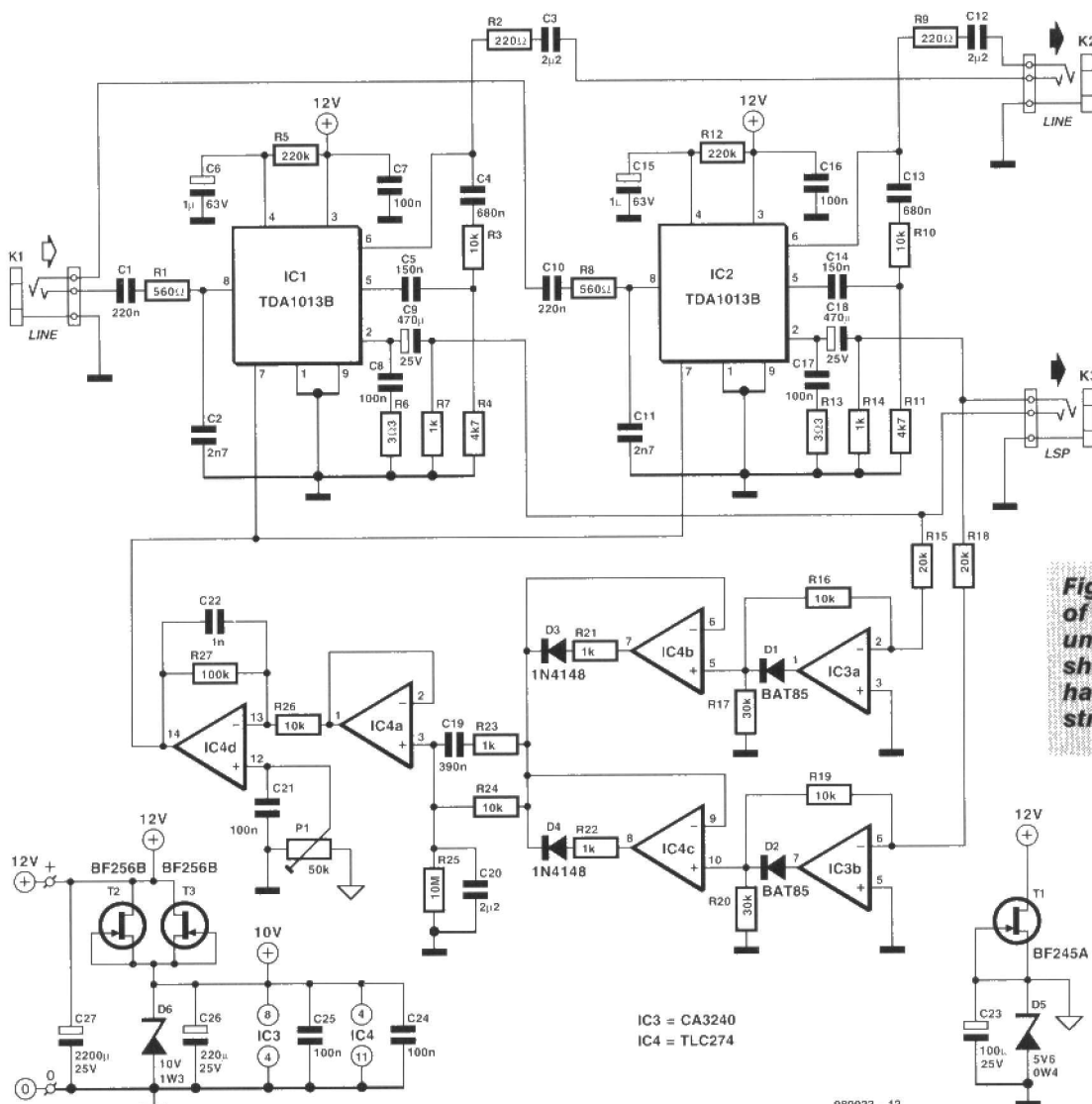


Figure 2. The diagram of the automatic volume control for PCs shows that the circuit has been kept straightforward.

IC3 = CA3240
IC4 = TLC274

Parts list

Resistors:

$R_1, R_8 = 560 \Omega$
 $R_2, R_9 = 220 \Omega$
 $R_3, R_{10}, R_{16}, R_{19}, R_{24}, R_{26} = 10 \text{ k}\Omega$
 $R_4, R_{11} = 4.7 \text{ k}\Omega$
 $R_5, R_{12} = 220 \text{ k}\Omega$
 $R_6, R_{13} = 3.3 \Omega$
 $R_7, R_{14}, R_{21}, R_{22}, R_{23} = 1 \text{ k}\Omega$
 $R_{15}, R_{18} = 20 \text{ k}\Omega$
 $R_{17}, R_{20} = 30 \text{ k}\Omega$
 $R_{25} = 10 \text{ M}\Omega$
 $R_{27} = 100 \text{ k}\Omega$
 $P_1 = 50 \text{ k}\Omega$ (47 k Ω) preset

Capacitors:

$C_1, C_{10} = 0.22 \mu\text{F}$
 $C_2, C_{11} = 0.0027 \mu\text{F}$
 $C_3, C_{12}, C_{20} = 2.2 \mu\text{F}$ metallized polyester (MKT), pitch 5 or 7.5 mm
 $C_4, C_{13} = 0.68 \mu\text{F}$
 $C_5, C_{14} = 0.15 \mu\text{F}$
 $C_6, C_{15} = 1 \mu\text{F}$, 63 V, radial
 $C_7, C_8, C_{16}, C_{17}, C_{21}, C_{24}, C_{25} = 0.1 \mu\text{F}$
 $C_9, C_{18} = 470 \mu\text{F}$, 25 V, radial
 $C_{19} = 0.39 \mu\text{F}$
 $C_{22} = 0.001 \mu\text{F}$
 $C_{23} = 100 \mu\text{F}$, 25 V, radial
 $C_{26} = 220 \mu\text{F}$, 25 V, radial
 $C_{27} = 2200 \mu\text{F}$, 25 V, radial

Semiconductors:

$D_1, D_2 = \text{BAT85}$
 $D_3, D_4 = 1\text{N}4148$
 $D_5 = \text{zener diode } 5.6 \text{ V}, 400 \text{ mW}$
 $D_6 = \text{zener diode } 10 \text{ V}, 1.3 \text{ W}$
 $T_1 = \text{BF}245\text{A}$
 $T_2, T_3 = \text{BF}256\text{B}$

Integrated circuits:

$\text{IC}_1, \text{IC}_2 = \text{TDA}1013\text{B}$
 $\text{IC}_3 = \text{CA}3240\text{E}$
 $\text{IC}_4 = \text{TLC}274\text{CN}$

Miscellaneous:

$K_1-K_3 = 3.5 \text{ mm}$ stereo audio socket for board mounting
 PCB Order no. 980023-1 (see Readers Services towards the end of this issue)

the stereo preamplifier.

The values of various components in the control circuit are chosen to ensure a fast attack time and a long release time. This ensures that short-duration signal peaks are effectively suppressed, whereupon the circuit recovers (relatively) slowly from the damping action.

Power for the circuit is derived from a standard 12 V mains adaptor.

CIRCUIT DESCRIPTION

In the circuit diagram in Figure 2, the preamplifier-output amplifier combination is contained in IC_1 and IC_2 . This type of IC is a compact 4 W audio amplifier with integral voltage-controlled volume control. The range of the logarithmic volume control is 80–90 dB with control voltages

3

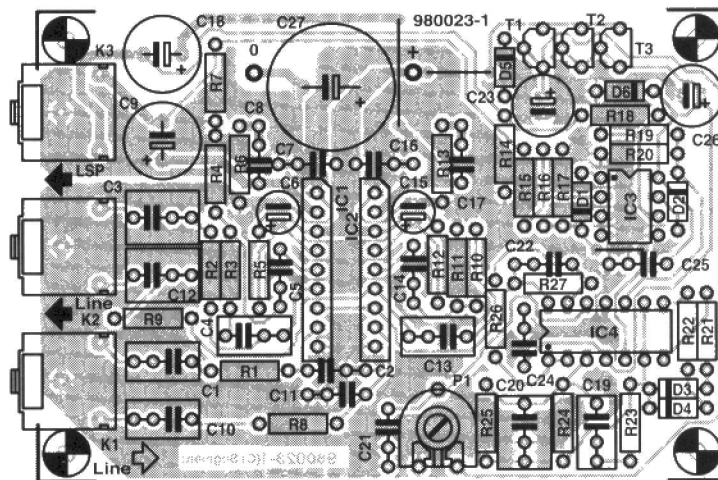


Figure 3. The printed-circuit board for the automatic volume control.

between 6.5 V (+5 dB) and 2.0 V (–80 dB).

The control voltage is applied to pin 7 of the IC. The line output is at pin 6, which is linked via a capacitor to pin 5, the input of the output amplifier.

The circuit has three stereo terminals: line in, line out, and power out.

The power output is 2.5 W for a loudspeaker impedance of 8 Ω and a supply line of 18 V, which is sufficient for most applications.

The analogue input signal at the line input, K_1 , is applied to pin 8 of IC_1 , raised in the preamplifier and output via pin 6. The transfer between pins 8 and 6 depends on the control voltage at pin 7.

The line signal is attenuated and its level made suitable for inputting to the output amplifier by networks R_3-R_4 and $R_{10}-R_{11}$. Assuming a supply line of 12 V, the output amplifier is driven fully ($P_{o(\text{max})} = \text{about } 1.2 \text{ W}$ into 8 Ω) by an input signal of 90 mV.

RC networks are provided at the inputs ($R_1-C_1-C_2$ and $R_8-C_{10}-C_{11}$) and

the line outputs (R_2-C_3 and R_9-C_{12}).

The output amplifier outputs are provided with large electrolytic capacitors, C_9 and C_{18} .

The supply lines are decoupled by C_7 and C_{16} .

Filters R_6-C_8 and $R_{13}-C_{17}$ ensure that the amplifiers remain stable at high frequencies.

RECTIFICATION AND REGULATION

The audio signal to be rectified is taken from the loudspeaker terminals and applied to IC_{3a} and IC_{3b} . The following description is based on IC_{3a} .

Negative signals are inverted by the op amp and amplified by a factor that depends on the ratio $R_{15}:R_{16}$. In the present circuit, this is –2, that is, attenuation. With positive signals, the op amp is overdriven and its output negative. Diode D_1 is then cut off and half the input voltage is available at its cathode [$R_{17}/(R_{15}+R_{16}+R_{17})$]. This means that the op amp behaves as a full-wave rectifier/amplifier, whose amplification is the same (0.5) for both

4

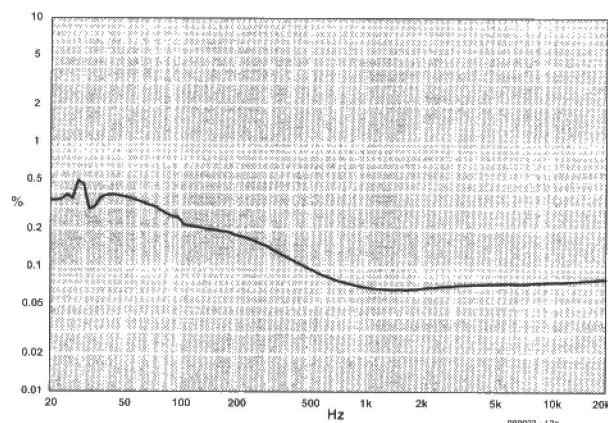
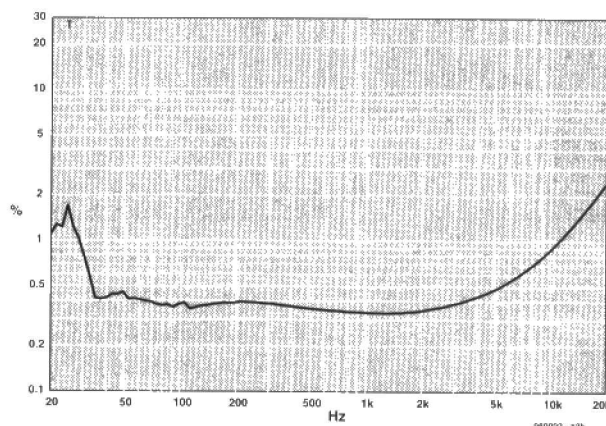
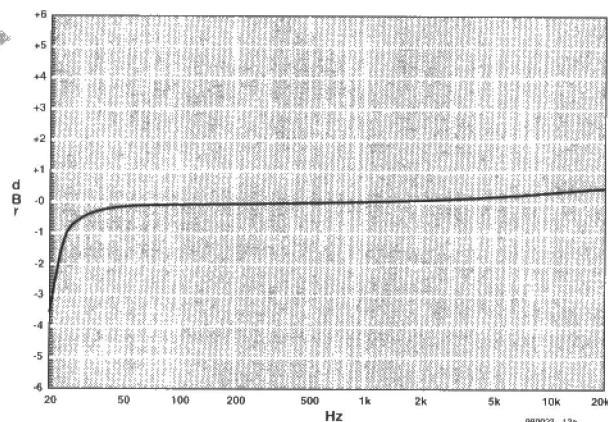


Figure 4. Some graphs to show a few of the electrical properties of the AVC. (a) is the frequency response curve measured between the line input and loud-speaker input terminals. (b) is the distortion characteristic measured at the loudspeaker output terminals (5 W into 8 Ω). (c) is the distortion characteristic measured at the line output terminals terminated into 10 k Ω .

halves of the input signal.

Operational amplifiers IC_{4a} and IC_{4b} are half-wave rectifiers whose outputs are interlinked by diodes D₃ and D₄. Because of these diodes, the output with the highest potential determines the extent to which capacitor C₂₀ is charged via resistor R₄. Network R₂₃-C₁₉ has been added to ensure that fast signal fluctuations are passed on very rapidly.

Capacitor C₂₀ is discharged slowly via resistor R₂₅, so that the control circuit returns to its default setting when no or a smaller input has been applied for some time. The potential across C₂₀ is buffered by IC_{4a}, while IC_{4d} ensures that the (fixed) default level is added to the signal. The resulting control signal is applied to the control input (pin 7) of IC₁ and IC₂.

With component values as specified, the compression is 10:1; in other words, a 20 dB change at the input results in a 2 dB change at the output.

The setting of P₁ depends on the signal level at the input of the circuit. Since this level varies largely from one

sound card to another, the design provides a wide control range.

SUPPLY LINES

As mentioned earlier, the circuit is powered by a standard 12 V mains adaptor, which is applied directly to the output amplifier. All other circuit elements are supplied with a regulated 10 V potential. This voltage is produced with the aid of current source T₂-T₃ and zener diode D₆.

The reference voltage of 5.6 V is produced with the aid of current source T₁ and zener diode D₅.

CONSTRUCTION

The circuit is best built on the printed-circuit board shown in **Figure 3** (see Readers Services towards the end of this issue). Start the construction with placing audio sockets K₁-K₃, the three wire bridges, and all solder pins, and follow these with first the passive components, and then the active ones. Mind the polarity of the electrolytic capacitors, diodes, transistors, and ICs.

After it has been fitted, set the preset to minimum volume (anticlockwise).

Solder the output leads from the standard mains adaptor from which power is derived to the relevant pins on the board. If the board is to be housed in an enclosure, a plug-and-socket arrangement should be used for linking the output from the adaptor to the board.

Check that the output voltage of the adaptor does not rise above 18 V with small loads.

When all is connected, the circuit can be tested. Passive loudspeakers may be linked directly to the LSP output terminals, but active ones should be connected to the line output terminals.

Finally, connect a sound source, for instance, the line output of a sound card or the output of a Walkman™ to the input of the circuit and adjust P₁ for the desired volume. From then on, any fluctuations in the signal input level will be minimized automatically.

[980023]

GREAT NEWS FOR YOU!

Over the past 11 years ULTimate Technology supplied more than 20,000 commercial versions, but also thousands of educational versions, which, having no Gerber Interface (high resolution photoplotter) are not suitable for commercial use, but are otherwise, identical to the, naturally far more expensive, commercial versions. After a worldwide test on Internet the ULTiboard Studio evolved, with the same well-considered limitation, at a price at which everybody can afford a professional design system.

ULTIMATE TECHNOLOGY
Unit 1, Lodges Barn, Coxbury Lane,
St. Briavels, Lydney, Glos GL15 6QJ
phone: 01594-810100
fax 01594-810200

ULTIBOARD Studio
FOR PRIVATE USE AT £69
ULTIBOARD STUDIO LITE INCL. VAT

SEE ALSO THE ADVERTISEMENT ELSEWHERE IN THIS ISSUE




80C32 BASIC control computer

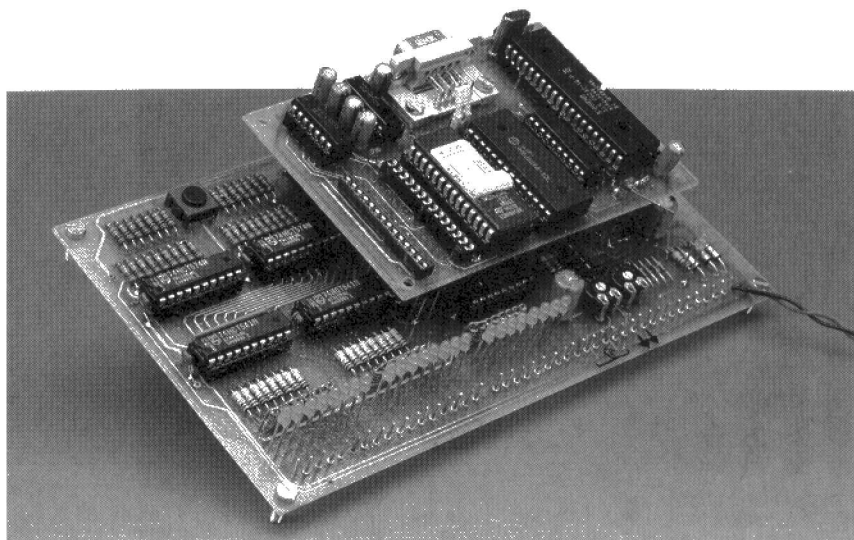Part 1: introduction and circuit descriptions

Faced with the ominous task of having to cajole an existing microcontroller board into managing a control function, many of you will recognize the problem of having to develop a more or less complex interface board. Another problem may be the complexity and general hassle of everything to do with assembly language.

The computer described in this article may be programmed in MCS-51 BASIC, and has been designed specifically for control purposes.



The 80C32 BASIC control computer consists of two boards which are interconnected via three single-row pin-headers. The smaller of the two boards (10×8 cm) is the actual control computer. The other board is considerably larger at 10×16 cm (Eurocard size), and contains all input/output circuits and 45 solder pins, or, if so desired, screw terminals.

The control computer runs the MCS-51 BASIC interpreter, and has been designed for maximum flexibility and optimum price/performance ratio. It can also be used in stand-alone mode. For this purpose a reset network (R1-C12) is provided, which may only be fitted if the computer is used in stand-alone mode.

Many options are open to those of you wishing to realize their own applications using the present control computer: for instance, the three pin-headers for the inter-board connections are arranged in a 0.01-inch raster which allows a piece of Veroboard or general-purpose stripboard to be used as a carrier.

The control computer was developed with low cost and simple construction in mind. Because of this, the address decoding is not handled by a costly PAL but by common-or-garden 74HCT logic. The same goes for nearly all I/O functions. With the possible exception of the type μ PD7002 A/D converter from NEC, the add-on mul-

tifunction board does not contain esoteric components either.

THE 80C32 MAIN COMPUTER BOARD

The design of the 80C32 BASIC control computer follows well-trodden paths. In addition to the microcontroller type 80C32 (IC1) with its low-address latch (IC20) the main board also contains three memory ICs: a 32-kByte static RAM (IC3), an EPROM (IC4) with a capacity of up to 32 kBytes for the 8-kByte BASIC interpreter and your own BASIC extensions, as well as up to 16 kBytes of EPROM (IC5) to hold your BASIC programs. The address decoding for IC5 is handled by a 74HC00 (IC6). No address decoding is required for memories IC3 and IC4 because each of them occupies a block of 32 kBytes in the lower memory range. That enables them to be addressed in a simple manner using address line A15 to control their (active-low) chip select inputs.

Jumper JP1 enables pin 27 of IC4 to be connected to A14 (for a 27256 EPROM), or to +5 V, so that 16-kByte as well as 8-kByte EPROM may also be used in this position. Position IC5 can only accommodate 16-kByte or 8-kByte EPROMs, because the upper address range is required for the I/O range, and only 16-kByte EPROMs may be used in any case as the BASIC program memory.

The 80C32 is a ROM-less CMOS version of the 8052 for which the MCS51-BASIC interpreter was originally written (by Intel). This interpreter requires a rather special memory structure, as illustrated in **Figure 1**.

The main board, of which the global structure is shown in **Figure 2**, provides a battery backup supply for the RAM chip, IC3. Normally, the +5 V supply line (pin 1 of K2) is connected through to pin 1 (VRM) of K1. This connection, as well as that between IC3 and A15, has to be broken. To make the board go into low-power mode, the \overline{CS} input (pin 20 of IC3) also has to be connected to pin 14 of K2. Because the multi-function does not make use of this option, the relevant connections remain intact.

The last noteworthy component on the main board is the MAX232 converter for the RS232 interface (IC7). This chip and the associated 9-way sub-D connector forms the gateway to the PC (or terminal/console) on which you develop your programs for the control computer.

MULTIFUNCTION EXTENSION BOARD

The circuit diagram of the multifunction extension board is given in **Figure 3**. It accommodates the power supply, the address decoding circuits for the I/O range, the watchdog timer, the digital inputs and outputs, as well as the analogue inputs and outputs. The operation of each of these sub-circuits is described in the following sections.

Power supply

The power supply is open to modifications to meet your specific requirements. All that is required really is a smoothed direct voltage of at least +12 V at about 150 mA which has to be applied to terminal block K25. Note that a capacity of 150 mA is only sufficient for the control computer and all LEDs. If K24 is not connected, driver IC8 (for the digital and analogue outputs) is supplied at just 11 V instead of 24 V. A higher voltage (up to about +30 V) should only be connected to K24 if higher driver output voltages are required, for example, to control 24-V relays which are often used in industrial equipment. Diodes D1 and D3 afford protection against reverse polarity.

Watchdog timer

The watchdog timer consists of a monostable (IC4d) with a period of about 10 s, using R4 and C11 as the timing elements. If no reset signal is available, then C11 will discharge across R4. This can only be prevented by permanent recharging by means of signals from CPU port P1.5, which are

transformed into suitable pulses by IC4e and IC4f, using C10 and R1.

The listing of the *Background Clock with Watchdog Timer Reset* program (available on the project floppy disk) shows how an on-time interrupt may be used to generate watchdog-feed pulses. Diode D4 prevents capacitor C11 from discharging across the output of IC4e. A reset can also be brought about by pressing S1. Fitting jumper JP1 disables the watchdog timer. LED D5 goes out when a reset arrives. Diodes D36 through D43, in combination with resistors R75 and R76, protect the CPU inputs against voltage surges.

Address decoding

The address decoding of the I/O (input/output) range relies on a 74HCT139 (IC3). This simple circuit selects the 8-kByte large address range between 0C000_H and 0FFFF_H, and also supplies four I/O select signals ($\overline{IO1}$ through $\overline{IO4}$).

This creates a cluster of 16 I/O addresses between 0C000_H and 0C00F_H (see table below).

The above address block is repeated from address 0C010_H, because 512 mirror images appear in the 8-kByte large I/O range.

16 digital inputs

The 16 digital (TTL-compatible) inputs are created with the aid of two 8-bit input drivers type 74HCT541 (IC5 and IC6). Resistors R59-R74 act as protection devices. The LEDs, D12-D27, not only indicate the status of the input signals (high/low) but also pull the inputs high via their series resistors R7 and R8. This is useful when nothing is connected to the inputs. Consequently, the inputs are active-low. If you want a particular line to be permanently low, simply tie it to 0 V (ground). Although this 'inverse logic' has been taken into account when you start programming the computer, it has a definite advantage in that no +5-V supply is needed outside the control com-

Figure 1. This rather special memory structure is required by the MCS51-BASIC interpreter.

program memory (PSEN = 0)	data memory (RD or WR = 0)
0FFFFH	not used
0E000H	
0DFFFH	I/O range
not used	(motherboard)
0C000H	
0BFFFH	
	max. 16Kbyte EPROM for BASIC programs (IC5)
08000H	
07FFFH	
max. 32 Kbyte EPROM (IC4)	32 Kbyte RAM (IC3)
02000H	
01FFFH	
8 Kbyte MCS-51- BASIC-Interpreter	
00000H	

980002 - 13

puter. The example program called *DO* and *DI Test* on the project diskette shows how the inputs are interrogated.

8 digital outputs


The 8 digital outputs are beefed up by an ULN2803 (IC8), an integrated darlington driver with open-collector outputs capable of switching loads of up to 50 V at 0.5 A. Each output of the ULN2803 has a built-in suppressor diode which allows inductive loads like stepper motors and relay coils to be controlled without problems. If you really want to go up to 50 V with the

Select signal	Address	Read	Write
IO1	0C000H	digital inputs 1-8	digital outputs 1-8
	0C001H	digital inputs 1-8	digital outputs 1-8
	0C002H	digital inputs 1-8	digital outputs 1-8
	0C003H	digital inputs 1-8	digital outputs 1-8
IO2	0C004H	digital inputs 8-16	analogue output 1
	0C005H	digital inputs 8-16	analogue output 1
	0C006H	digital inputs 8-16	analogue output 1
	0C007H	digital inputs 8-16	analogue output 1
IO3	0C008H	not used	analogue output 2
	0C009H	not used	analogue output 2
	0C00AH	not used	analogue output 2
	0C00BH	not used	analogue output 2
IO4	0C00CH	ADC status register	ADC status register
	0C00DH	ADC high data	not used
	0C00EH	ADC low data	not used

2/98

{980002-1}


280002 - 12

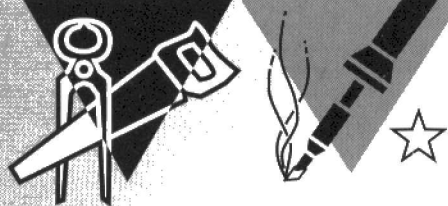

simple electronic metronome

with 440 Hz generator

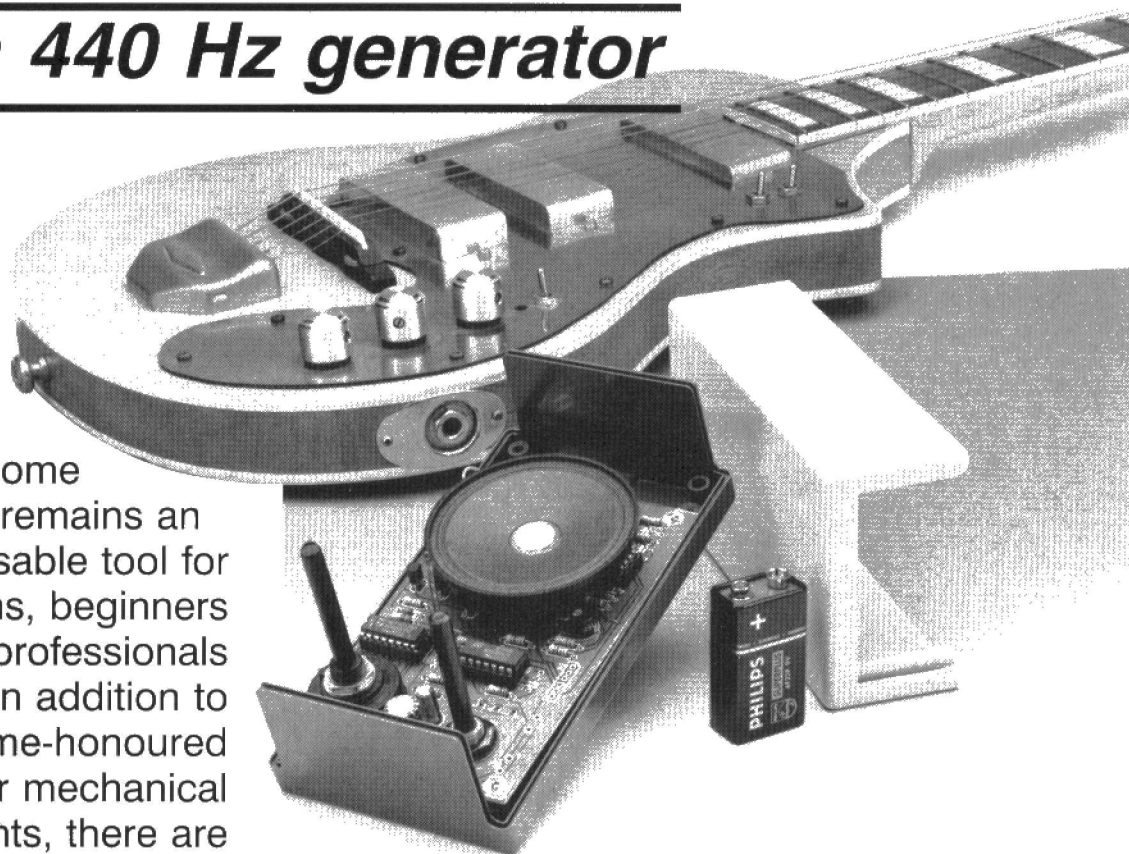A metronome is and remains an indispensable tool for musicians, beginners and professionals alike. In addition to the time-honoured triangular mechanical instruments, there are now electronic models on the market. This article describes a simple DIY metronome that may prove useful to beginners in music.



A metronome is an apparatus for sounding an adjustable number of beats per minute and therefore for fixing the tempo of a composition. The idea of the clockwork model patented by Maelzel seems to have been appropriated from the Dutch inventor D N Winkel.

The one most commonly used is a pyramidal wooden instrument at the front of which a perpendicular steel strip about 3.5 in long by 0.5 in wide is pivoted. The principle is that of a double pendulum (an oscillating rod weighted at both ends). The upper weight is movable along the steel strip and according to its position on the rod the number of oscillations per minute can be made to vary between 40 and 208. The rod beats (or ticks) as it swings back and forth. Maelzel's graduated scale, fixed to the case, gives speed of oscillation. A composer who wants, say, 78 crotchet (US: quarter-note) beats in a minute will write M.M. (Maelzel metronome) $\text{♩} = 78$.

The electronic metronome described here has a useful feature in emphasizing the first beat in a bar. This is done acoustically by increased volume as well as electrically by the light-

ing of an LED. Another useful feature is the provision of a generator for tuning string instruments.

CIRCUIT DESCRIPTION

Metronome

The generator producing the beats consists of the two halves of a Type 556 CMOS timer, IC₁. Section IC_{1a} is configured as an astable multivibrator, whose frequency can be adjusted with P₁ between 60 and 250 beats per minute. If the lower figure is too fast, the value of C₁ may be increased slightly. On the other hand, the upper limit of 250 beats may be raised (although this is unlikely to be required for music applications) by reducing the value of R₁ to about 1 kΩ.

To ensure a regular, stable frequency, C₁ should preferably be a tantalum capacitor, but if need be, a good-quality electrolytic may be used.

The output of IC_{1a} triggers the other section, IC_{1b}, a monostable multivibrator, via C₂. The monostable generates pulses of constant width in the rhythm of the clock frequency.

The output of IC_{1b} is split into two: one part is applied to the clock input

* In music and audio engineering, a third is a melodic and harmonic interval, taking three steps in a scale (major or minor) counting top and bottom notes. So, *major third* (C up to E), *minor third* (C up to E_b), and *diminished third* (C# up to E).


Design by F. Hueber

of decade counter IC₂, and the other to low-frequency output amplifier T₁-T₂ via R₅.

Outputs Q₀-Q₈ of the counter are successively enabled and actuated, that is, in this case, they are changed from logic low to logic high (0 to 1). This is particularly important as

reset after 3-8 pulses. In the time signature, which is placed on a sheet of music immediately after the clef sign, the numerator in these fractions indicates the number of beats in a bar and the divisor the value of each beat. Thus, a time signature of 3/4 means that there are three beats in each bar

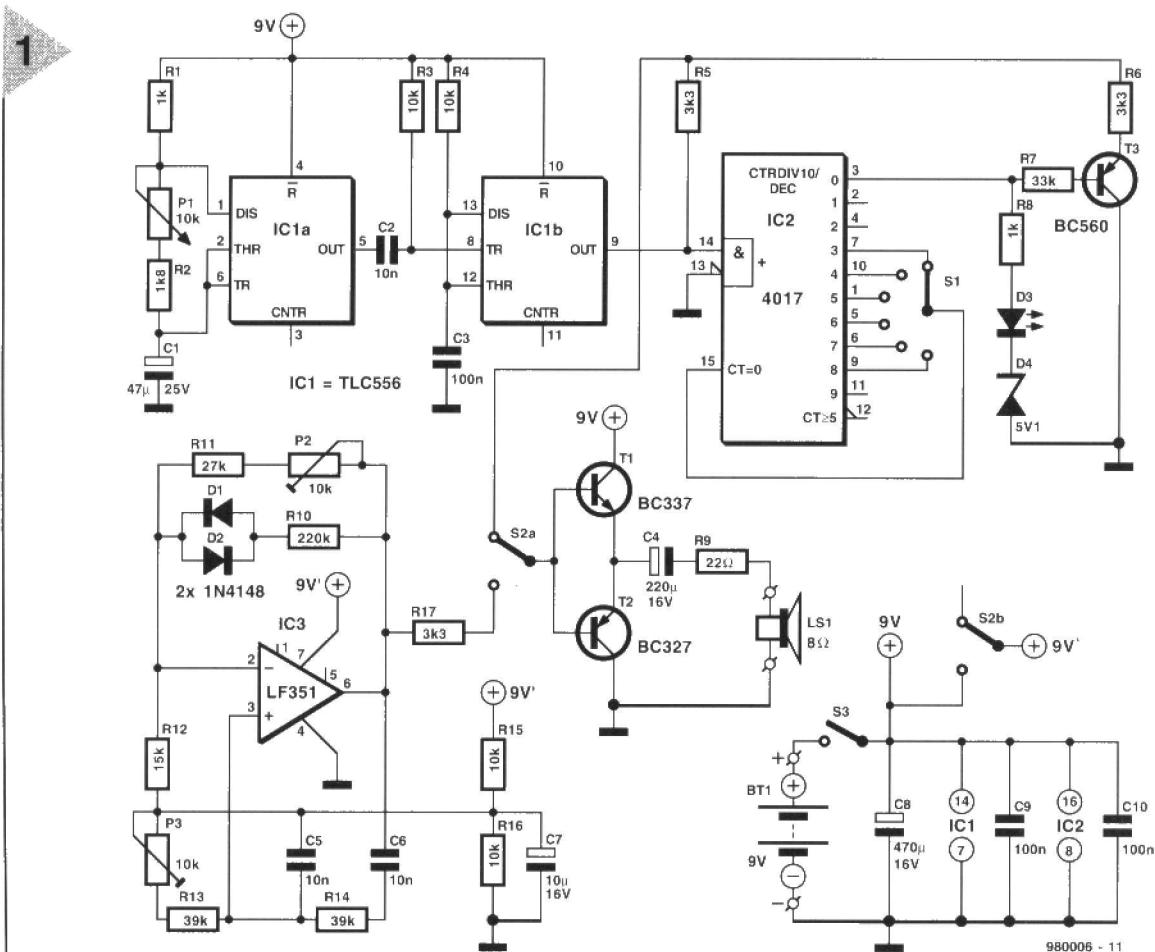Diodes D₁ and D₂ ensure that the output signal is a nearly pure sine wave. The 'nearly' is caused by the inevitable cross-over distortion resulting from the output stage operating without quiescent current. The output frequency is that of the international concert pitch, that is, the tuning-note



regards Q₀ (pin 3), since this is held low for the longest period of time to keep transistor T₃, which functions as a switch, on.

Potential divider R₅-R₆ is then actuated, which results in the pulses arriving from IC₁ being applied at only half amplitude. Output Q₀ goes high only at the first beat in a bar, when the potential divider is not actuated, whereupon the relevant pulse arrives at T₁-T₂ at full strength. Consequently, this beat is rather louder than the others and also sounds a little different. At the same time, the high level at Q₀ causes D₃ to light briefly. This LED also serves as a battery indicator: when the battery voltage drops below about 6 V, zener diode D₃ ensures that the diode remains extinct.

The number of beats in a bar (US: measure) is set with S₁. Depending on the setting of this switch, the counter is

Figure 1. The metronome proper is based on IC₁ and IC₂, while the Wien bridge oscillator, based on IC₃, provides the tuning frequency.

and that the value of each beat is a crotchet or quarter note.

Transistors T₁ and T₂ together form a simple push-pull output stage that operates with virtually no quiescent current. The sound level may be

adapted to individual taste by changing the value of R₉ between the output stage and the loudspeaker. Note, however, that the sum of this resistor and the ohmic value of the loudspeaker must not drop below 20 Ω to prevent overloading of the transistors.

440 Hz generator

The push-pull output stage can be switched from the metronome proper to the output of frequency generator IC₃. This is a classical Wien bridge oscillator whose output level is set with P₂. The type of op amp used is not important: almost any type, even a 741, will do.

A (=440 Hz), but may be altered slightly, if desired, with P₃. The actual frequency-determining components are R₁₃, R₁₄, C₅, and C₆.

Power supply

Power is supplied by a 9-V dry battery. Switch S₃ is the on/off selector. Switch section S_{2b} arranges power to be supplied to oscillator IC₃ when the unit is switched to 'tuning'.

With average use, the battery will last quite a long time. The metronome circuit draws a current of about 8 mA and the frequency generator one of around 15 mA.

CONSTRUCTION

The metronome/generator is best built on the printed-circuit board shown in Figure 2, which is, however, not available ready made.

Rotary switch S₁ and preset P₁ may be fitted directly on the board.

The space at the right-hand side of the board is intended to house the

SEE ELEKTOR
MARCH 1995
P63
CORRECTIONS
& UPDATES
RELATES TO
P63 ARTICLE

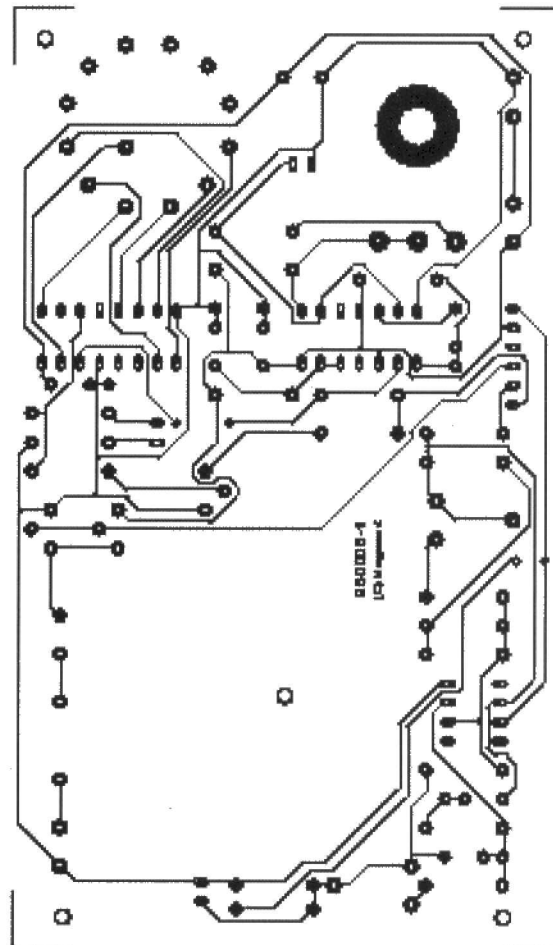
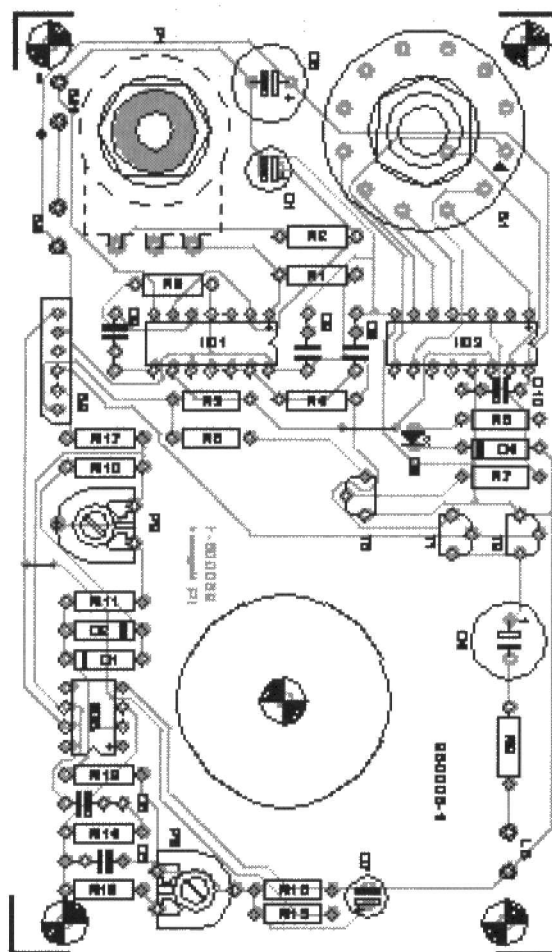


Figure 2. The printed-circuit board for the metronome is designed to accommodate the potentiometer and the rotary switch.

Parts list

Resistors:

$R_1, R_8 = 1 \text{ k}\Omega$
 $R_2 = 1.8 \text{ k}\Omega$
 $R_3, R_4, R_{15}, R_{16} = 10 \text{ k}\Omega$
 $R_5, R_6, R_{17} = 3.3 \text{ k}\Omega$
 $R_7 = 33 \text{ k}\Omega$
 $R_9 = 22 \Omega$
 $R_{10} = 220 \text{ k}\Omega$
 $R_{11} = 27 \text{ k}\Omega$
 $R_{12} = 15 \text{ k}\Omega$
 $R_{13}, R_{14} = 39 \text{ k}\Omega$
 $P_1 = 10 \text{ k}\Omega$, linear
 $P_2, P_3 = 10 \text{ k}\Omega$ preset

Capacitors:

$C_1 = 47 \mu\text{F}$, 25 V
 $C_2, C_5, C_6 = 0.01 \mu\text{F}$
 $C_4 = 220 \mu\text{F}$, 16 V, radial
 $C_7 = 10 \mu\text{F}$, 16 V, radial
 $C_8 = 470 \mu\text{F}$, 16 V, radial

Semiconductors:


$D_1, D_2 = 1\text{N}4148$
 $D_3 = \text{LED}$
 $D_4 = \text{zener diode, } 5.1 \text{ V, } 400 \text{ mW}$
 $T_1 = \text{BC337}$
 $T_2 = \text{BC327}$
 $T_3 = \text{BC560}$

Integrated circuits:

$\text{IC}_1 = \text{TLC555}$
 $\text{IC}_2 = 4017$
 $\text{IC}_3 = \text{LF351}$

Miscellaneous:

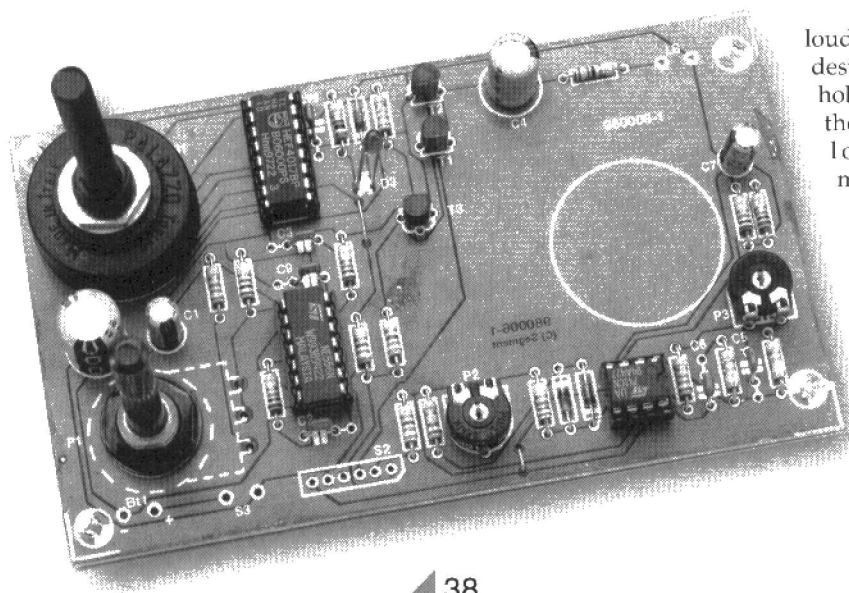$S_1 = 1\text{-pole, } 12\text{-position rotary switch for board mounting}$
 $S_2 = \text{double-pole change-over switch}$
 $S_3 = \text{single-pole switch}$
 $\text{BT}_1 = 9\text{-V battery with connecting clips}$
 $\text{LS}_1 = \text{loudspeaker, } 8 \Omega$
 Enclosure, $150 \times 80 \times 55 \text{ mm}$



loudspeaker. If desired, a suitable hole can be cut in the space for the loudspeaker magnet.

The finished board and battery are best housed in a suitable enclosure, such as the one specified.

TUNING

Tuning the frequency generator with P_3 to 440 Hz is, of course, best done with the aid of a suitable frequency meter. If such an instrument is not available, the A-note struck on a well-tuned piano may be used to compare the generator output with (this needs a critical ear, of course!).

FINALLY

Bear in mind when selecting a value for R_9 and setting P_2 that the sound from the loudspeaker is much louder in the enclosure than when it lies on the table!

[980006]



ELEKTOR
ELECTRONICS

EXTRA

2
**a simple
PC network**
a cable is all you need

6
**RS232 interface
for 68HC11**
with a program loader for
small systems

10
**USB and
FireWire**
connecting all digital
devices via a single cable

14
**light intensity
measurement
with a PC**
no external power supply
required

PC TOPICS


The term 'computer hobbyist' brings to mind the image of a lonely father sitting in a spare bedroom, typing cryptic machine-language code deep into the night. The wife is of course also lonely, which in the course of time results in the computer finding a place in the living room, in spite of its rather hideous appearance.

The space which thus comes free in the bedroom is soon filled, at first with children and after that with a second computer. And with the second computer comes the need for a network.

By Peter Smit

a simple PC network

a cable is all you need...

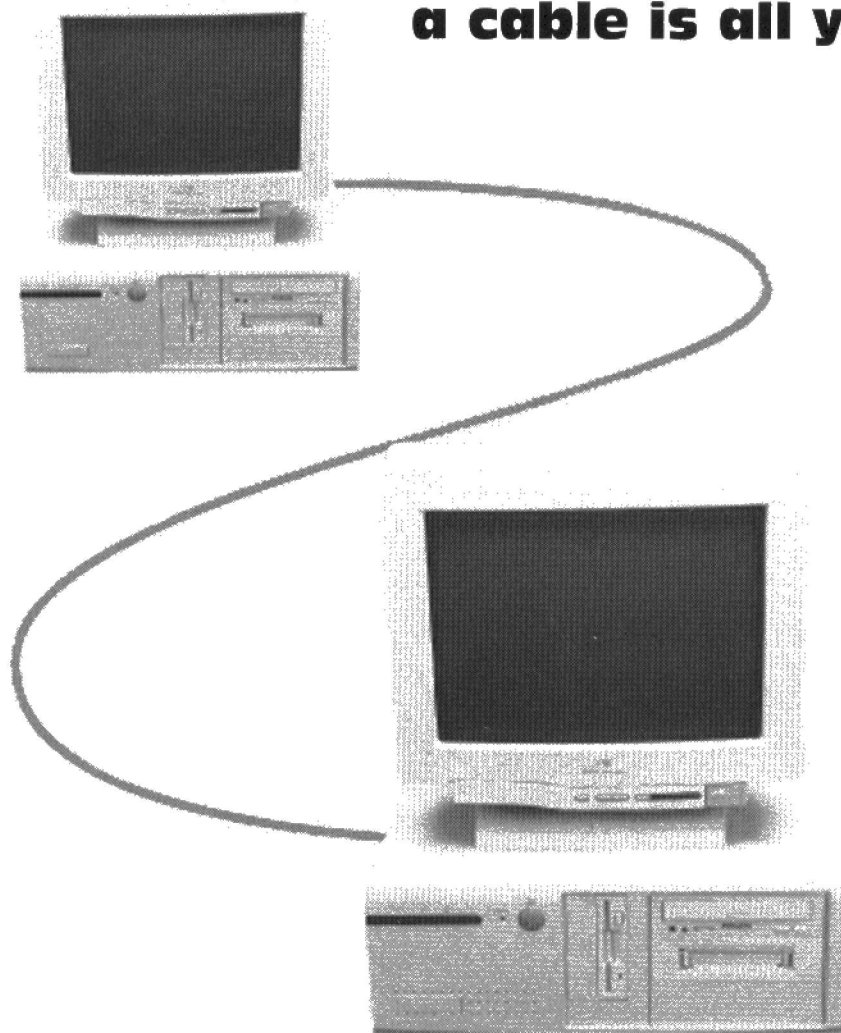

In addition to allowing communication via e-mail, interconnecting two or more computers has the advantage that files, printers, modems, disk drives, ZIP drives and CD-ROM drives can be shared. With the Internet boom it has become totally 'in' to run 3D games in multiplayer mode. With this option, multiple persons can participate in the

game at the same time. They can play together in a three-dimensional maze or fly through space together. Some well-known games which have this option are Doom, Duke Nukem 3D, Quake, Outlaws, X-Wing versus T-Fighter and so on. Some of these run on a central server via the Internet, but they can also be run via a TCP/IP network,

an IPX network, a modem or a null-modem link.

The type of link which is most appropriate for interconnecting individual computers depends on the application which we intend to use via the link.

Null-modem cable

A null-modem cable is a good choice when relatively small data volumes need to be transferred. This inexpensive serial link is only suitable for transferring small amounts of data and for playing some multiplayer games. The maximum speed which the RS232 port can achieve with such a cable is 115,200 baud. For serial data transmission with 1 start bit, 8 data bits and 1 stop bit, this results in an effective transfer rate of 10,250 bytes per second (36 MB/hour). For this data rate, both computers must be fast (486 or better) and should preferably be fitted with a type 16550 UART (Universal Asynchronous Receiver/Transmitter).

One can easily check whether such a chip is present by means of the program MSD (provided standard with DOS). When MSD is run, it displays the type of UART present for each COM port: 8250, 16450 or 16550. An 8250 can only manage 9600 baud. Starting with AT machines one finds only the faster types (16450, 82450 and 16550), which can handle up to 115,200 baud. Many 'snoop' programs report the slower 8250 when a 16450 is fitted. Only the 16550 has a

buffer. Modern internal modems and Pentium motherboards have a 16550 as standard. Multitasking operating systems, such as Windows 95, Windows NT and Linux, can experience timing problems if a UART buffer is not present. This shows up as lower data rates, loss of data packets etc.

It's advisable to disable the 16550's FIFO buffer for the port to which the mouse is connected. Problems such as the mouse pointer 'freezing' after a few movements can sometimes be caused by this buffer. In Windows 95 the buffer can be disabled via the Control Panel/System/Device Manager/Ports/COM1 (mouse)/Properties/Settings/Advanced/Use FIFO Buffers. In case of communication problems the FIFO speed can also be somewhat reduced via this route. With Windows 3.11 one must include a line in SYSTEM.INI under the heading [386Enh]: 'COM1FIFO=0' disables the FIFO buffer for the mouse connected to the COM1 port. Always make a copy of SYSTEM.INI before making any changes!

Now that we've dealt with UART pitfalls, let's return our attention to the null-modem cable. Such a cable provides a link between the serial (RS232) ports of two computers. The RS232 port was originally intended to be used for interconnecting a DTE (Data Terminal Equipment) and a DCE (Data Communication Equipment). A D25 cable between a computer and a modem is an example of such a DTE/DCE link.

A null-modem cable, by contrast, is used for a DTE/DTE link. It requires that certain leads be interchanged between the two connectors. The most important of these are TxD (Transmit Data) and RxD (Receive Data). These two leads plus a ground lead represent the simplest possible 'three-wire' null-modem cable. The only problem with a three-wire link is that there can be no hardware handshaking between the two computers.

In a three-wire cable, the connector pin for the signal which asks whether data can be sent (Request to Send) is connected directly to the pin which is intended to receive the answer from the other computer (Clear to Send). This results in a sort of 'narcissistic' connection: the computer wonders whether it can send data, while 'thinking' that it is talking to a second computer. And like a true narcissist it naturally provides the answer to its own question. In other words, "Can I send? Yes, I can always send and I decide that for myself."

Whenever the two computers do not have the same level of performance,

the slower one must be the *host* machine, since the host machine determines the data transfer rate. If there are communication problems with the link, it's a good idea to check whether data transfers in the reverse direction work well. If this is the case, then there is a timing problem between the two computers. In order to properly solve such a problem we must use a connection with more than three leads, since this is the only way to have hardware handshaking (see **Figure 1**). Programs which only recognize hardware handshaking will thus not work with a three-wire null-modem cable.

A full null-modem connection consists of 7 leads. A 25-pin or 9-pin sub-D connector is used. A male connector is always used at the back of the computer, so that we must use two female connectors for the cable. Normally the mouse is connected to the COM1 port via a 9-pin connector, so that the 25-pin connector of the COM2 port is usually used for this sort of experiment.

There are several types of null-modem connections. The most expensive solution, which is also the most flexible, consists of two universal modem cables together with a null-modem adapter. A universal modem cable is a 25-lead cable which has a 25-pin male connector at one end and both a 25-pin female connector and a 9-pin female connector at the other end. A null-modem adapter is a small block fitted with two 25-pin female connectors. We connect the adapter between the two cables, using the single 25-pin connectors of the two cables. With this combination we can cope with all D9 and D25 COM ports. With two 1.8-metre cables, such a combination costs approximately £15.

For roughly £10 we can make do with a single universal modem cable and a null-modem adapter. However, the adapter has threaded posts which mate with the fixing screws of the cable connector. These are in the way if the adapter is to be plugged directly into the computer's COM-port connector. It's possible to dismantle the connector and remove these posts on one side of the adapter so that it can be plugged into the COM-port connector. However, this is not a particularly elegant solution, since the modified adapter cannot be secured to the connector.

One can also purchase a D25 serial female/female interconnection cable and modify it oneself according to Figure 1, at least if it does not have

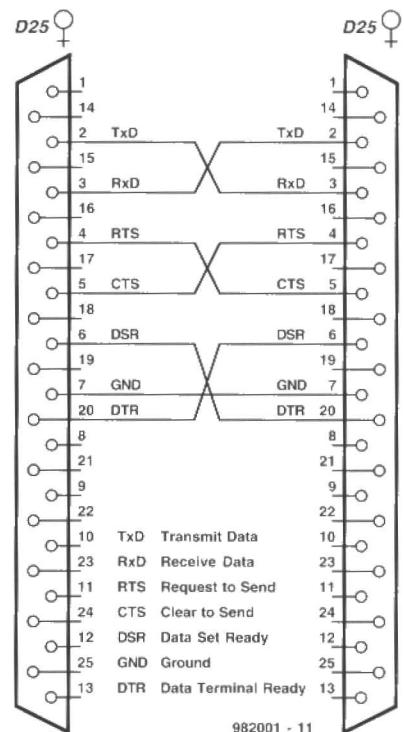


Figure 1. Wiring scheme for a full DTE/DTE null-modem cable.

moulded-on connectors.

The ease of use of a null-modem link is largely determined by the software used. The PC BIOS can (or at least could) only manage 19,200 baud. All MS-DOS null-modem software thus accesses the UART registers directly, rather than via the BIOS. This is the only way in which it is possible to achieve a 115,200 baud data rate.

The best-known interconnection software is LapLink, but Norton Commander also has a Link option. From MS-DOS 6.x onwards, Interlink provides a standard means for interconnecting two computers, and Windows 95 has the Direct Cable Connection option. For occasional use I prefer Norton Commander (V4.0). Since this program is anyhow often used to provide a user interface, it is natural to also use it for the link. Version 4.0 has the additional advantage that the contents of multiple directories can be selected concurrently and copied. With a bit of patience it is possible to transfer an entire hard-disk partition in one operation. Of course, at a data rate of 35 MB/hour this does not go particularly fast.

In Norton Commander one selects Menu/Right or Left/Link, by means of which the first computer is configured as the master and the second as the slave. (Pay attention to the selection of the correct COM ports.) The drives of the slave computer then appear at the master as a normal window within

which one can select, copy and delete items and create subdirectories. Norton Commander V4.0 also can be used with a parallel interconnection cable for a faster link.

An Interlink cable

If we wish to transfer data more quickly, then we will want to use a modified parallel cable. LapLink was the first to introduce this possibility, and Norton later followed suit in Norton Commander starting with Version 4.0. Microsoft adopted this idea starting with MS-DOS 6.x in the form of Interlink. In Windows 95 this option is called *Direct Cable Connection*. A disadvantage of the parallel link is the relatively short distance which can be bridged (a few metres). The greatest advantage of a parallel link is its speed. The maximum speed depends on the type of printer port and the sort of cable which is used.

Various types of parallel link cables can be used. First, there are standard 4-bit versions which work with LapLink, Norton Commander and Windows 95. Then there is a modified 8-bit version for Norton Commander. An ECP cable, which is faster, can only be used with ECP/ECP ports. Finally, there is an 'intelligent' Universal Connection Module (UCM) which checks for itself which types of parallel ports are present and configures itself either in standard 4-bit mode or ECP mode. In standard 4-bit mode the transfer rate lies between 40

and 70 kbyte/s. In ECP mode the transfer rate can range up to 400 kbyte/s.

Officially, a Centronics port is bidirectional (data can be transferred in both directions). In practice, a more economical implementation has been used, since for years printers just swallowed data and only protested when they were out of paper. Modern printers are more mature and more inclined to 'talk back', which has resulted in the development of bidirectional parallel interfaces (PS/2, EPP and ECP).


The old-fashioned Centronics interface has 8 data lines which can only be used to send data. There are three registers for controlling the parallel port: an 8-bit data register (read/write), a 5-bit status register (read-only) and a control register (read/write). The status lines are 'misused' by the Interlink cable in order to allow data to also be received. If the incoming 5 status lines are cross-connected to 5 outgoing data lines at the 'other end', a 5-bit parallel link is created. The basic cable results from cross-connecting pins 2 through 6 with pins 11, 10, 12, 13 and 15; pin 25 serves as the ground lead (see **Figure 2a**). If better screening is desired, then additional ground lines are used (pins 18 and 24). This cable thus allows 5 bits to be transferred in parallel. One of these is used for handshaking, leaving a 4-bit data stream.

The control register contains a bit which allows a bidirectional parallel port to be enabled or disabled. If one

were to interconnect the outputs (data lines) of two standard parallel ports, there's a good chance that one set of outputs would not survive the experiment. Moreover, it's not possible to read in data via a standard parallel port: what is read from the data register is not the data presented to the port from an external source, but the data which were last written to the register by the computer itself.

With a true bidirectional port, the output lines are placed in a high-impedance state when the bidirectional mode is enabled (control bit set). Data which are written to the data register remain in a buffer without being transferred to the output data lines. When the data register is read, the current status of the port's data pins is read. From this it is apparent that a bidirectional port does not support duplex operation. The bidirectional control bit serves to make the port act as either an output or an input. By properly using one or more status lines for handshaking, the two interconnected ports can be correctly switched between send and receive modes, so that true 8-bit data communication is possible. In order to use a parallel port in this manner, one must use an 8-bit ECP cable; a standard 4-bit cable cannot be used. An ECP cable interconnects all 8 data lines and cross-connects various status lines (see **Figure 3**). If such a cable is used with a non-bidirectional port, damage to the outputs (data lines) can result.

Figure 2. Three types of parallel-interface cables between two computers: a simple 4-bit cable (a), a 4-bit cable for Windows 95 (b) and an 8-bit cable for Norton Commander (c).

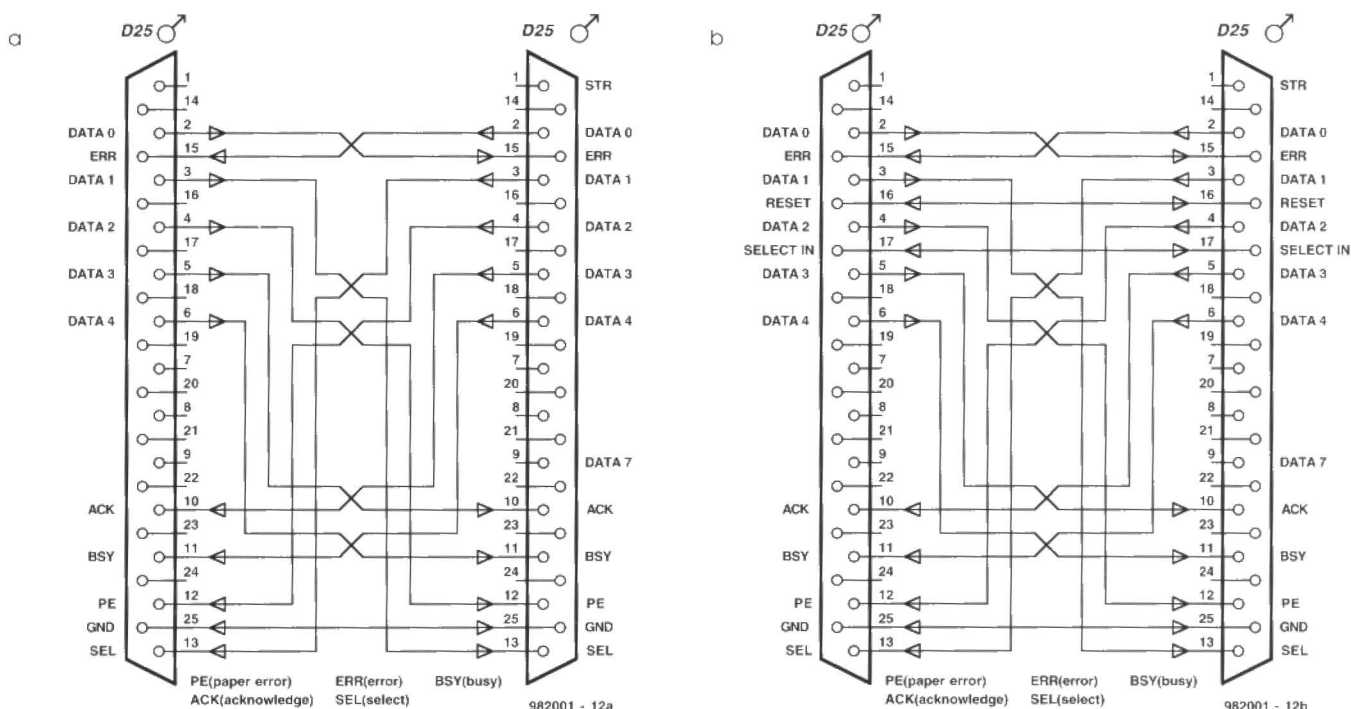

The modern Extended Capabilities Port (ECP) is bidirectional and has an extended control register which (among other things) allows the operating mode (SPP, EPP or ECP) to be configured. The ECP port uses an interrupt (IRQ7 for LPT1, IRQ5 for LPT2) to capture the data stream; it has a FIFO buffer and DMA support, it has a decompression mode and it handles its own handshaking. It is thus better suited for multitasking operating systems and much faster for the Direct Cable Connection. The transfer rate ranges between 200 and 400 kbyte/s. The transfer rate of a normal 4-bit cable is also increased when it is connected between two ECP ports. In order to achieve the highest data rates (200 to 400 kbyte/s) a special ECP or UCM cable must be used.

The way that a UCM cable works can be gleaned from the various information scattered about the Internet. There is software in C++ which is able to recognize whether a specific port is standard or ECP. An electronic switch which is normally in 4-bit mode can be switched to ECP mode via a software-generated status signal.

As soon as a parallel port's ECP mode is enabled (via the BIOS), the port uses an interrupt (7). This frequently results in an interrupt conflict if a sound card is installed. If the ECP mode is to be used, then the sound card must be configured to use a different interrupt (5).

A search via the Internet yielded six different descriptions of standard 4-bit Interlink cables. We have combined two of these plus the Norton Comman-

der cable into a single figure (see **Figure 2**).

The simple version (**Figure 2a**) works with LapLink, Fastlynx, Ebox, XLink and MS-DOS 6.x Interlink. The version for Windows 95 (**Figure 2b**) has two extra leads which interconnect pins 16 and 17.

The only connection scheme which supports 8-bit data transfers with standard parallel ports is the Norton Commander Link option (V4.0 and V5.0). Norton Commander uses three additional bits in the control register to allow the remaining 3 data bits to be read. A true 8-bit link results from the added connections (pins 1/7, 7/1, 9/16, 16/9, 8/14 and 14/8) without using bidirectional ports (**Figure 2c**). In ECP mode, the control register cannot be used to read data. The 8-bit Norton Commander cable thus cannot be used with a parallel port operating in the ECP mode.

An important difference between the Windows 95 cable and the Norton Commander cable relates to pin 16. This can either be interconnected with pin 16 or cross-connected with pin 9. One must choose between an 8-bit

cable version which only works with Norton Commander or a 4-bit Norton Commander version which can also be used with Windows 95. The Windows 95 version is the most compatible. Unless you plan to work only with Norton Commander, I would advise you to choose the Windows 95 version.

The ECP cable can only be used with bidirectional ports. For those of you who wish to experiment with an ECP cable, a diagram from


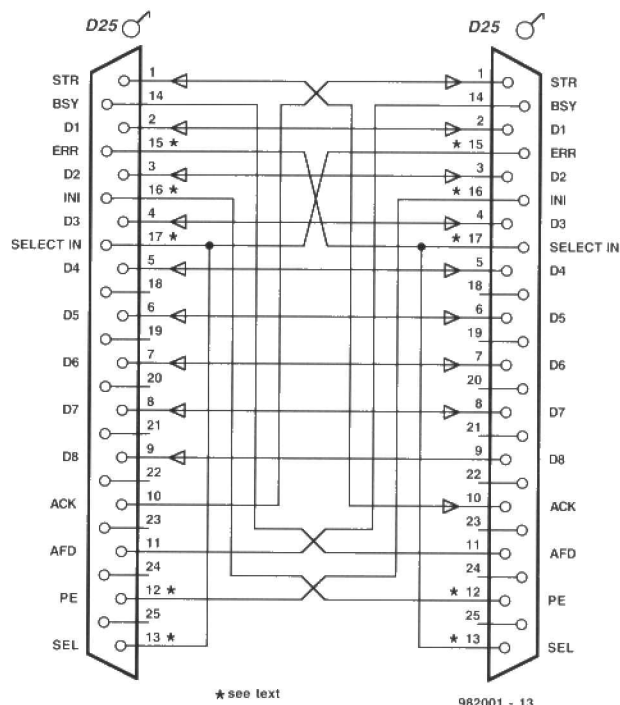


Figure 3. A special cable is required for bidirectional parallel ports (ECP). Don't forget that this cable must never be used with standard parallel ports!

Microsoft is included (see **Figure 3**). Remember that a standard port can be damaged if an ECP cable is used with it! In a working situation in which two specific computers are always connected to each other via ECP ports, this does not present a problem. On the other hand, something can always go wrong, such as for example if someone just wants to quickly copy a file to his 486 notebook.

In a situation in which various persons work with a variety of computers (including notebooks), use a UCM cable. Such a cable is fast, safe and problem-free in use. With Windows 95, a UCM cable approaches the capabilities of a true network with regard to functionality and speed. There is even ODI software available for such cables, which allows them to be used in a Novell or Lantastic network. The UCM cable is less expensive than a separate network adapter attached to the parallel port of a PCMCIA network adapter. This is also a good option for connecting a notebook to a computer which is itself connected to a network. The notebook then receives a network connection via the UCM cable. For more information refer to the Parallel Technologies Internet site (<http://www.lpt.com/>). If the flexibility of the UCM cable is not necessary, then the money (£50) can be better invested in a network. A network is significantly faster and can easily be extended.

(982001)

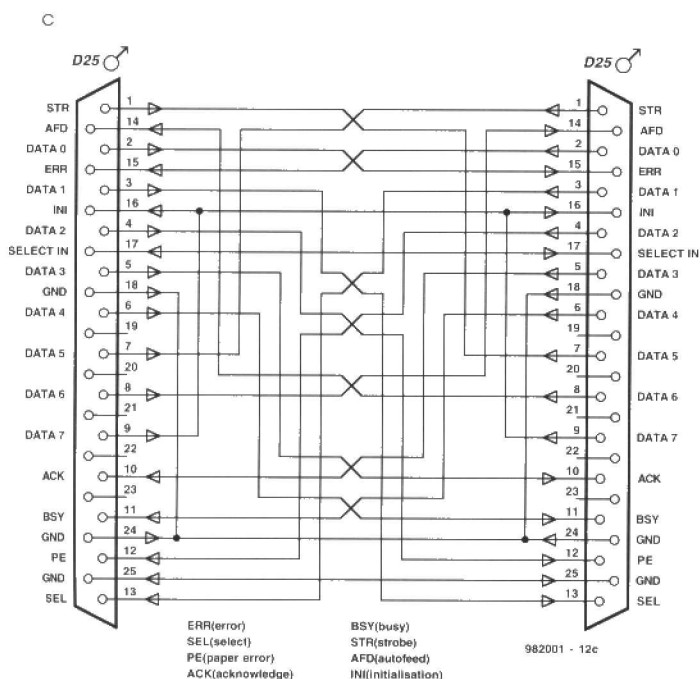


The Motorola 68HC11 microcontroller is packed with features and consequently requires very few parts to make a minimum system configuration. In principle, such a system does not need an RS232 interface because that is usually only necessary to be able to load programs into the controller's on-chip EEPROM memory. For the actual use of the program, the interface is not required. The RS232 interface described here is therefore built on a separate little board, and may be used at any time for programming and troubleshooting 68HC11 controller applications.

Design by J. Dietrich

RS232 interface for 68HC11

with a program loader for small systems

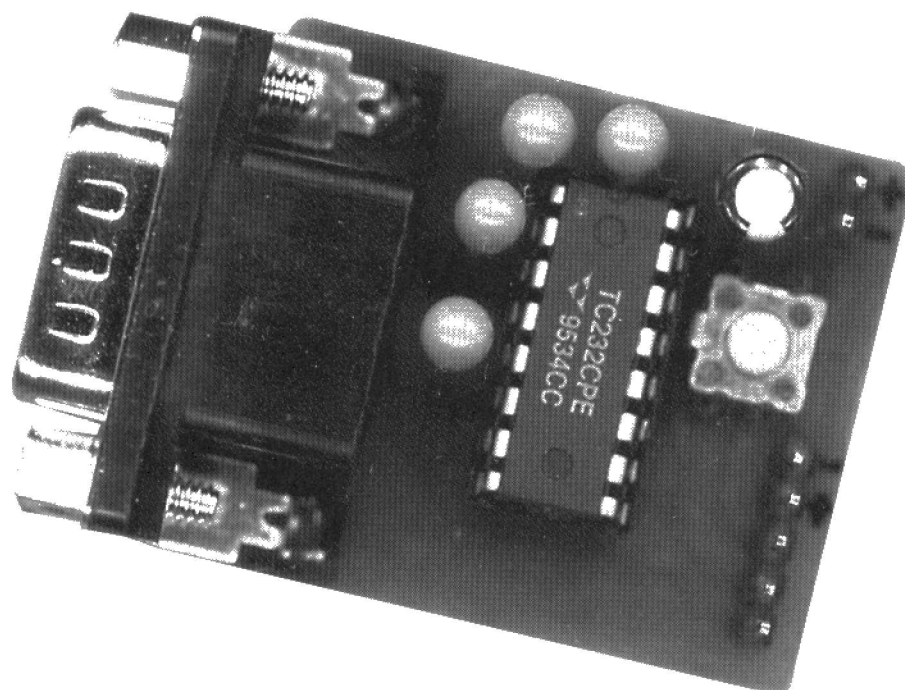

An 68HC11 Processor Board was published in the April 1994 issue of *Elektronika*. The 68HC11 is supplied in a 52-pin PLCC case. It features up to 40 freely programmable input/output lines distributed across five ports, an EEPROM memory with a size of up to 2kBytes, and a small RAM memory. Because the EEPROM is used as program memory, there is no

need to burn EPROMs. The serial interface available on the chip allows ports, RAM or EEPROM cells to be read and written.

As illustrated in **Figure 1**, a minimum system using the 68HC11 requires only eight additional components. Even this small amount of external parts is sufficient to enable interrupt programs to be run and the eight A-D converter

inputs to be employed.

The interface described here is built once only on a separate board, and migrated to future 68HC11 applications when and where necessary. It is only connected to the target system (here, the minimum system) for diagnosis and programming jobs.

Circuit and circuit board

The circuit diagram of the interface is given in **Figure 2**. Actually, it consists of just one IC, the unavoidable MAX232 RS232 driver/level converter which is capable of creating a fully RS232 compliant interface with symmetrical inputs and outputs, all on basis of a single 5-volt supply. Although the output line levels at pins 7 and 14 are at about $\pm 9V$ only, that is still within the RS232 specification.

The interface is connected to a PC using a cable with 9-pin sub-D sockets at both ends. Wires 2 and 3 in the cable should be crossed, all others travel pin-to-pin. The link to the target system (the 68HC11 processor board) is made via a 5-way cable connected to boxheader K2. This cable also carries the 5-V supply voltage for the interface. Connector K1 is only intended for situations where a 5-V supply is connected to the interface board, and the controller board is powered by the inter-

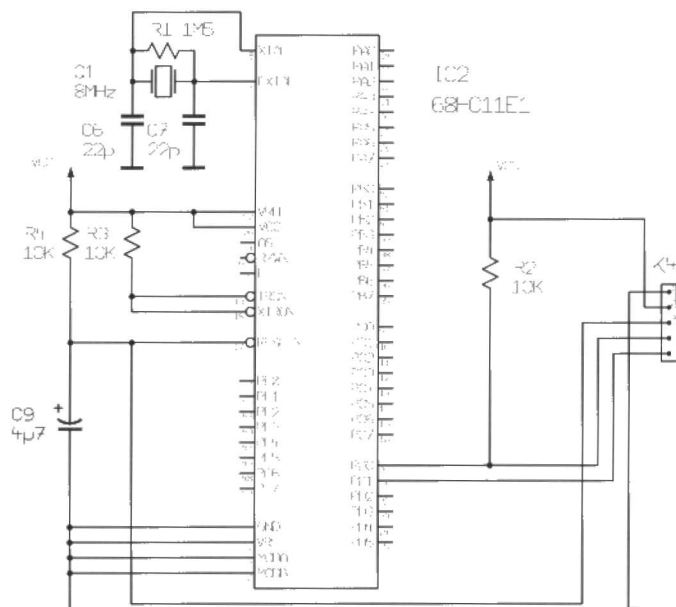


Figure 1. Apart from the microcontroller, a minimum system based on the 68HC11 requires only eight components.

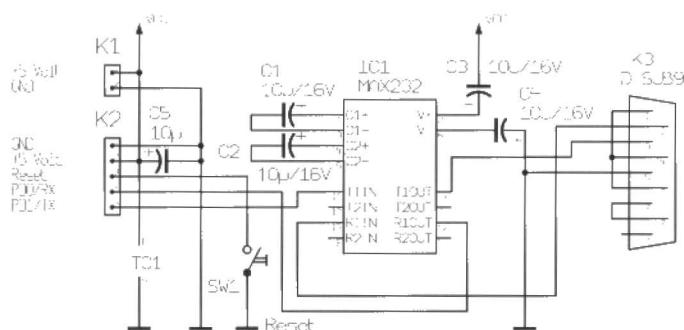


Figure 2. The RS232 interface is only built once, separate from the microcontroller system, and may then be used with all future experiments and applications of the 68HC11. In general, it is only connected-up for program development or debugging work.

face, via K2 and the 5-wire cable. A push-button on the interface board allows the microcontroller to be reset. Without the interface board, the controller uses its own, internal, reset logic which does not require a push-button. The artwork for the single-sided printed circuit board is given in **Figure 3**. In view of the small number of parts, a components list is not given. As usual, watch the polarity of the vertically mounted electrolytic capacitors before soldering them on to the board. Capacitor C5 decouples the supply voltage, and is safely rated at 10V.

Software

The software you will need to get going with the 68HC11 processor board and the present interface is available free

of charge from Motorola. The author used a packed file called ELEKT494.ZIP (66,304 bytes) which was downloaded from the Motorola BBS in Munich, Germany, telephone (+49) 89 92103111. This file may be found in subdirectory /mc68hcxx/m68hc11. The zip file contains, among others, an assembler with documentation, as well as programs for checking (MINIBUG) and programming EEPROMs (EEPROMIX). The list with short descriptions of all files held on the mailbox is called ALLFILES.BBS, and may be found in the directory /info. How is the software transferred to the microcontroller? For test purposes, the software may be moved to the RAM area starting at address 0. This is done by means of the ORG (originate) statement. 68HC11 versions are available which, like the -E1, have an equal amount of RAM and EEPROM. For pro-

gram testing in RAM, enter the following:

1. Produce the assembler file using a simple word processor (pure ASCII file with the extension .ASC). Example: TEST.ASC.
2. Launch the assembler
ASMHC11 TEST.ASC;b=256 (for CPUs with 256 bytes of RAM)
ASMHC11 TEST.ASC;b=512 (for CPUs with 512 bytes of RAM)
- Three files are generated with the following extensions:
TEST.S19 for EEPROM programming
TEST.LST ASCII documentation file
TEST.BOO for direct copying into the RAM memory
3. Configure the PC's serial port in a DOS window (example: COM2)
MODE COM2:1200,N,8,1
4. Copy the program into the 68HC11 RAM

COPY TEST.BOO/B COM2:

Once received the program is immediately executed.

Programming the on-chip EEPROM also requires a modification to EEPROMIX, which comes with the Elekt494 file:

1. Modify EEPROMIX as follows:

```
...
LDS #SFF
LDX #$1000 offset for control regs
CLR $35,X !! insert this line!!
CLR SCCR1,X initialize SCI for 8 data bits, 9600 bd
LDD #$30
...
```

2. Launch assembler by typing
ASMHC11 EEPROMIX.ASC;B=256

Next, program the EEPROM:

1. Produce the program using Editor, then assemble it.
2. Configure the PC serial port in DOS window
MODE COM2:1200,N,8,1
3. Copy the once modified program into RAM
COPY EEPROMIX.BOO/B COM2:
4. Close the DOS window, and launch HyperTerminal (Windows 95) select Direct Cable Connection on COM2
configure as 9600 bits/s, 8 bits, no parity, 1 stop bit, hardware handshaking protocol
Do File → Settings → ASCII Configuration, and set a character delay of 5, click on OK to leave the menu.
5. Type an upper-case I in the terminal window
(selects internal programming of the

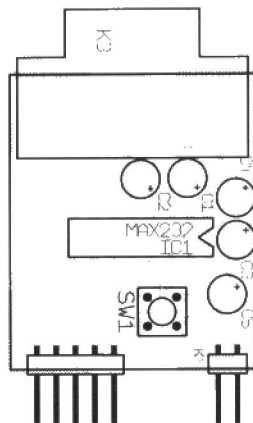
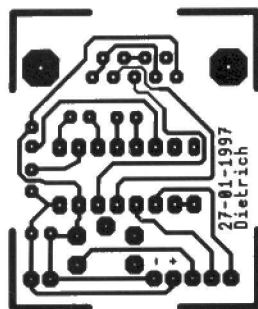


Figure 3. Track layout and component mounting plan of the small interface board.

EEPROM)

6. Transmit (upload) the relevant \$19 file using Transmit Text File.

Example: TEST.\$19.

To be able to start the EEPROM resident program without the interface connected to the HC11 board, fit a jumper on contacts 4,5 of header K4. The pro-

gram is then automatically launched when the supply voltage is switched on. Like EEPROGIX, the previously mentioned program MiniBug is transferred into the controller RAM using the COPY command and a bit rate of 1200/s. Next, the serial connection to the board may be established using HyperTerminal and a bit rate of 9600/s.

Finally

As already hinted at, the 68HC11 comes in three basic flavours:

- MC68HC11A1 (256 bytes RAM, 512 bytes EEPROM)
- MC68HC11E1 (512 bytes RAM, 512 bytes EEPROM)
- MC68HC11E2 (256 bytes RAM, 2048 bytes EEPROM)

The MC68HC11 is also available from second source Toshiba under the type designation TMP68HC11E1T.

The modifications to the EEPROM programmer software (EEPROGIX) are only necessary if you use the -E versions, because only these have a special protection byte for the EEPROM. An important point to keep in mind for your own applications and experiments is that this byte **must** be erased before any writing is done to the EEPROM in an -E version.

(9/2/97)

Component sets to ELEKTOR Electronics

We are a mail order company and manufacturing parts sets dedicated to ELEKTOR since 1985. The following sets included all required components:

ELEKTOR-PCB/software, according to the components list, fit on ELEKTOR PCB, in high quality from major manufacturer IC-sockets.

The sets included not description, mains transformer and enclosure.

For prices and more informations please visit our homepage:
<http://ourworld.compuserve.com/homepages/steletron>

970085	Sound-press-meter	£ 21.58
	Enclosure HE 222	£ 5.36
980007	Stereo microphone f. PC	£ 27.67
970053	Uninterruptable power supply	£ 12.51
980021	Electronic die incl. battery	£ 9.39
970068	Smartcard reader/writer complete incl. 976512 and 976014	£ 47.75
970086	Running lights for christmas	£ 34.05
970090-1	Electronic handyman w/o AT90S1200	£ 7.18
970090-2	Dockingst. f. handyman AT90S1200	£ 36.33
974001	PIC controlled light barrier	£ 25.41
974010	D.C. protector	£ 5.83
974020	Optocoupler	£ 11.09
974037	Auto volume control	£ 29.88
974038	Bass extension incl. transf.	£ 19.25
974053	Carbooster incl. housing	£ 20.67
974070	Object protect	£ 8.05
974072	Revolution counter	£ 25.61
974076	PIR-doorbell	£ 14.24
970065	Hygrometer	£ 36.22
970066	Video copy processor incl. mains transformer	£ 46.74

970083	Stereo microphone amplifier incl. mains transformer	£ 66.55
970087	80-metres receiver	£ 7.88
970027	Distortion (fuzz) unit	£ 24.75
970057	4-way serial port switch	£ 35.33
970060	Analogue measurement	£ 26.92
970063	DC nullifier for oscilloscope excl. PZ 5032	£ 43.25
976513	PZ 5032 programmed	£ 19.00
976016	Disk source code PZ 5032	£ 4.67
970064	IR-volume control (10 k)	£ 30.30
970077	Frequency meter/event ctr	£ 50.44
970079	Directional microphone	£ 16.76
970020	Dual continuity tester	£ 10.24
970023	Electronic code lock	£ 27.38
970050	Chipcard reader/programmer incl. ITT-connector	£ 20.64
	Chipcard connector ITT-Canon	£ 6.45
970053	Centronics relay card	£ 38.85
970055	Charging booster	£ 25.22
970059	Data acquisition system	£ 58.70
962008	Hexadec. keyboard for PC	£ 37.03
974012	Digital tester	£ 20.24
974019	Active windscreen wiper	£ 12.74
974024	Switch mode power supply	£ 15.70
974041	Stepper motor controller	£ 8.91
974042	RGB video amplifier	£ 30.44
974077	Supply board	£ 34.05
974078	Mains on delay circuit	£ 10.11
974100	Stand-alone-MIDI-synthesizer w/o Yamaha-board	£ 27.42
970025	Battery condition monitor	£ 37.76
970028	LRC-meter incl. transform.	£ 163.67
970028	Enclosure-set	£ 47.40
970039	Temp.volt. contr. for DMM	£ 7.57
970045	RC biswitch	£ 14.08
970046	Earth leakage meter incl. case 435	£ 36.97
970048	80C537 single board computer w/o IC 2, incl. software and battery	£ 91.63
972015	Mini progr. EEPROM	£ 5.20
972016	Mini progr. PIC	£ 4.70
976005	Software remote control	£ 7.50
976007	Software mini programmer	£ 4.80

970021	Wideband Millivoltmeter incl. enclosure E440 w/o DVM	£ 46.96
	3.5 digit LCD DVM module	£ 6.40
970041	Long distance IrDa	£ 38.89
970042	4-channel logic analyser	£ 6.18
970043	Compact 50-watt audio amplifier incl. heatsink w/o power supply	£ 66.71
970043-N	Power supply	£ 65.15
960112	Digital thermostat	£ 57.33
970022	2-wire domestic alarm system w/o enclosure	£ 35.43
970031	Optical/coax converter	£ 17.22
970036	Universal power supply	£ 12.58
960096	Electronic fuse	£ 27.93
970003	Battery-operated AF-signal generator	£ 22.03
970006	Battery simulator	£ 17.82
970010	Eprom programmer	£ 34.83
970003	Software	£ 14.85
970037	uC-controlled mixer-board	£ 74.96
960094	Battery-operated AF-amp. w/o case, battery, brass	£ 153.55
	UC 202 enclosure	£ 26.28
960095	Motor contr. f. R/C models	£ 33.42
970007	Mini LED running light	£ 5.72
970008	68HC11 emulator	£ 78.67
970009	Self-inductance meter	£ 21.05
970015	"Speaking doorbell"	£ 24.55
960089	Dongle switch incl. case	£ 13.12
960100	Magnetic-field meter incl. case	£ 22.63
960113	Speed regulator incl. enclosure and knobs	£ 29.55
970001	Monitor to guard fridge temperature incl. enclosure	£ 26.01
966022	Small workshop disc	£ 10.00
960068	Remote control by visible light w/o case, battery, brass	£ 23.18
960082	Guitar-effects switch	£ 35.79
960098	RS 232 data acquisition card incl. software 956508, 956018	£ 39.42
960106	Primary-battery refresher	£ 24.51
960110	20-bit A-D converter	£ 10.00

	incl. mains transformers	£ 169.03
964031	AC-mV-adaptor incl. case	£ 10.96
964062	Electrically isol. I2C bus	£ 12.43
964070	Mains voltage cleaner	£ 25.49
964082	EMI tracer	£ 17.57
964088	Stroboskop f. motorcycles	£ 24.38
964089	Capacitance comparator	£ 11.62
960079	50 Watt AF-amplifier w/o power supply incl. heatsink	£ 22.48
960107	IrDa-interface w/o option incl. enclosure, software 966020	£ 32.63
960107-O	Parts "optionally"	£ 3.76
960109	Headphones amplifier	£ 12.03
960075	Mini metal detector incl. M1 and wire w/o search coil	£ 20.04
960076	Video test chart generator incl. transformer, modulator, software	£ 107.73
960078	Mini flash programmer incl. Disk 966015 and test socket	£ 36.32
960093	Sampling rate converter incl. 966511 and X1=33.8688 M	£ 102.41
960085	Digital compass incl. case	£ 52.99
960090	RS232 interface for ICL 7106 incl. disk 966016 and ICL 7106	£ 21.18

Not mentioned sets for past issues are still available!
All components and PCBs as single parts available.

You also get these sets by your native dealer:

Indonesia :
PATTRA ELECTRONICS
Jl. Pagarish no.184/87 Bandung 40262
Jl. Dulatip no. 67 Bandung
Tel./Fax 022 433179

Israel :
Elektor Ltd.
P.O.B. 41096 Tel Aviv 61410
Tel. 03 6591991 Fax 03 6596244

Sweden :
PB Elektronik AB
Box 5516 S-14105 Huddinge
Tel. 08 7100370 Fax 08 7401806

Stippler-Elektronik

Inh. Georg Stippler

P.B. 1109 D-86656 Bissingen / GERMANY

Tel. and Fax -49 9084 463


eMail 09084463-0001@t-online.de

STE

Following the introduction of the USB (Universal Serial Bus) and in its wake FireWire (IEEE 1394), almost all hardware and software vendors in the computer world have ranged themselves behind the serial-bus concept. USB has thus become *the* standard for connecting peripheral devices to the PC. Thanks to this development, there is finally a single interface standard which allows all computer devices to be connected to each other. In the meantime, manufacturers of consumer electronics have also embraced the new FireWire standard.

USB and FireWire

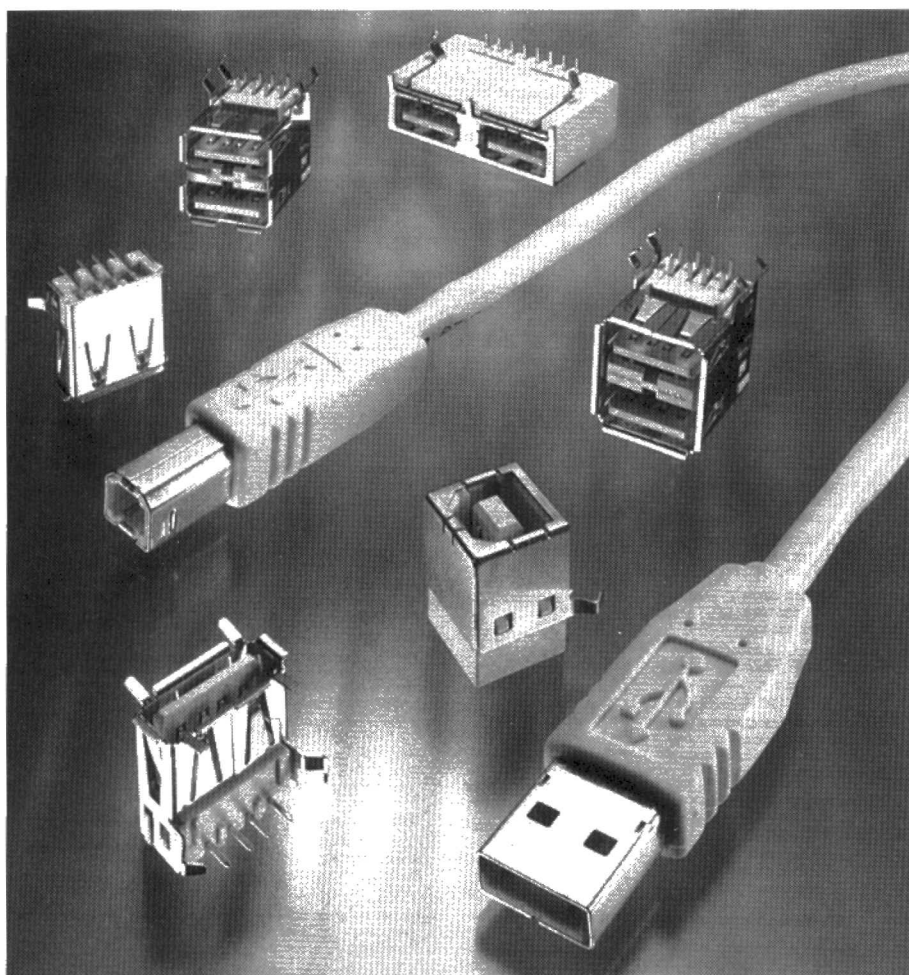connecting all digital devices via a single cable



arbitrary time (switching off the power is not even necessary!). The operating system scans the USB every few seconds and responds appropriately whenever a new device is detected. Memory is automatically allocated and a suitable interrupt is assigned. A maximum of 127 devices can be connected to the bus, and smaller devices can draw their operating power directly via the bus interface.

In the meantime, Microsoft has announced that Windows 98 will fully support the USB protocol. There are even rumours that a new OEM version of Windows 95 will appear with USB support.

There are two different categories of connection available within USB: one with a maximum data rate of 1.5 Mbit/s and the other with a maximum data rate of 12 Mbit/s. The slower variant relates to relatively slow devices such as mice, barcode readers, card readers and keyboards. The faster variant is intended for data communication with video recorders and audio systems, as well as for use with high-performance peripheral devices such as hard-disk drives.

Cabling


The USB uses a daisy-chain cabling technique. This means that the devices are connected to the cable in sequence, one after the other. Thus in theory the computer need have only one USB interface to allow up to 127 peripheral devices to be connected.

Of course, the USB has its limitations. The maximum extent of the cable is 5 metres. Longer distances can be achieved by using *hubs*, which are buffer/splitter devices. A hub can be

The problem is a familiar one: you purchase a new piece of equipment for the PC, search for matching cables, get all tangled up in the nest of cables behind the PC, and then have to look for a suitable driver. After that the correct interrupt and DMA channels must be assigned. Add to this the fact that every device needs its own mains power connection, and the chaos is

complete. Even the computer manufacturers themselves find this all a bit too much.

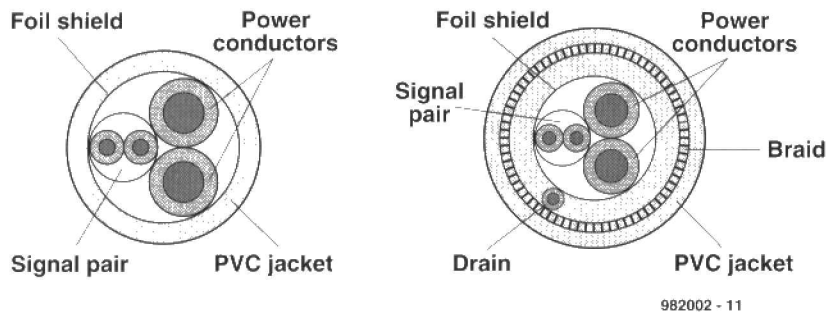The Universal Serial Bus shows that a better, and above all more user-friendly approach is possible. The USB offers a completely integrated 'Plug & Play' solution for all devices. For the user this means that any given device can be connected to the computer at any



982002 - 11

Figure 1. The construction of a standard USB cable and of a version with extra screening.

incorporated in a peripheral device, but it can also be included in a link as a stand-alone buffer and/or splitter. If a device includes a hub, then it is easily possible to incorporate two or more functions in a single enclosure. For example, one could imagine a keyboard with a built-in card reader, touchpad and/or mouse. A USB link can be extended a maximum of seven times, which means that its a total length can reach up to roughly 40 metres.

The USB link uses a 4-lead cable (see **Figure 1**). The two thinner wires are used for data communication, while the two thicker wires provide power to the connected device interfaces. A special, screened version of the cable is available for critical applications. The power leads can supply a total current of up to 500 mA at 5V. This means that small devices, such as modems and card readers, no longer need to have their own, separate power supplies. The connection to the cable is made via a compact 4-way plug, which measures only 12 mm × 4.5 mm.

FireWire: a step further

Applications for the USB are limited to data streams with a maximum rate of 12 Mbit/s. For many applications related to the PC this is more than adequate. However, there are conceivable applications for which significantly higher data rates are desirable. One example would be the loss-free (uncompressed) distribution of digital television signals. For such applications, a new communication standard has been developed: IEEE 1394, commonly known as FireWire. FireWire is platform-independent, and its performance far outstrips that of other existing interfaces, including even the most advanced SCSI versions. The most important characteristics of the FireWire interface are low cost, ease of use thanks to a compact connector, complete 'Plug & Play' capability and especially high performance. The currently-used I/O interfaces (Centronics, RS232, Ethernet, SCSI and so forth) can thus be replaced by a better system, and communications between the


computer and a wide variety of peripheral devices, or directly between individual devices, can be considerably simplified. In terms of performance, FireWire lies between USB (maximum 12 Mbit/s) and fibre-optic links (1 Gbit/s). With this level of performance FireWire could displace existing networking standards such as Ethernet (10Base-T), but in practice FireWire is presently too expensive for this. In addition, Ethernet has emerged from the computer world, while FireWire is clearly destined to play a dominant role in the arena of modern consumer electronics products for digital communications. The configuration shown in **Figure 2** clearly illustrates the mutually complementary nature of USB and FireWire and demonstrates how they can be used to extend each other. Each has its own particular region of application. In the illustrated configuration, USB is used for devices directly connected to the PC, while FireWire forms the digital link between a D-VHS recorder, a set-top box and a digital television.

The performance level of FireWire presently lies at around 100 Mbit/s, with speeds of 200 Mbit/s and 400 Mbit/s approaching feasibility. Just as with USB, a simple connector is used which can be attached with a minimum of effort.

The protocol


In a significant departure from existing interfaces, FireWire allows for *isochronous* data transmission in addition to the existing *asynchronous* data transmission (what this all means is explained in the following text). In addition, the interface specification allows FireWire to be used in both cable and backplane environments (a backplane provides the internal connections between the various components of a computer). The protocol is thus usable both inside and outside of the computer enclosure. Depending on the specific electronic components used, data rates of 25 to 50 Mbit/s are possible on the backplane, and as much as 400 Mbit/s is possible with cable. A maximum of 16 hubs may be included in the cable system, and the separation between any two hubs can be a maximum of 4.5 metres. The maximum total extent of the cable is thus 72 metres.

Figure 3 illustrates a configuration in which two computers and a number of I/O devices communicate with each other via the IEEE-1394 bus. Note that the serial bus is also used on the backplane.

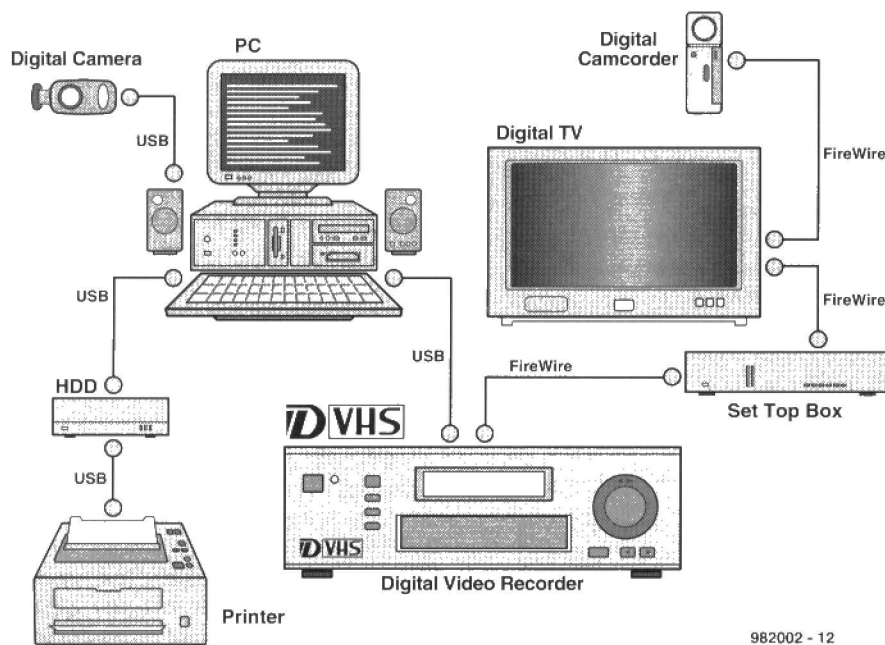

982002 - 12

Figure 2. A configuration in which both USB and FireWire play a role.

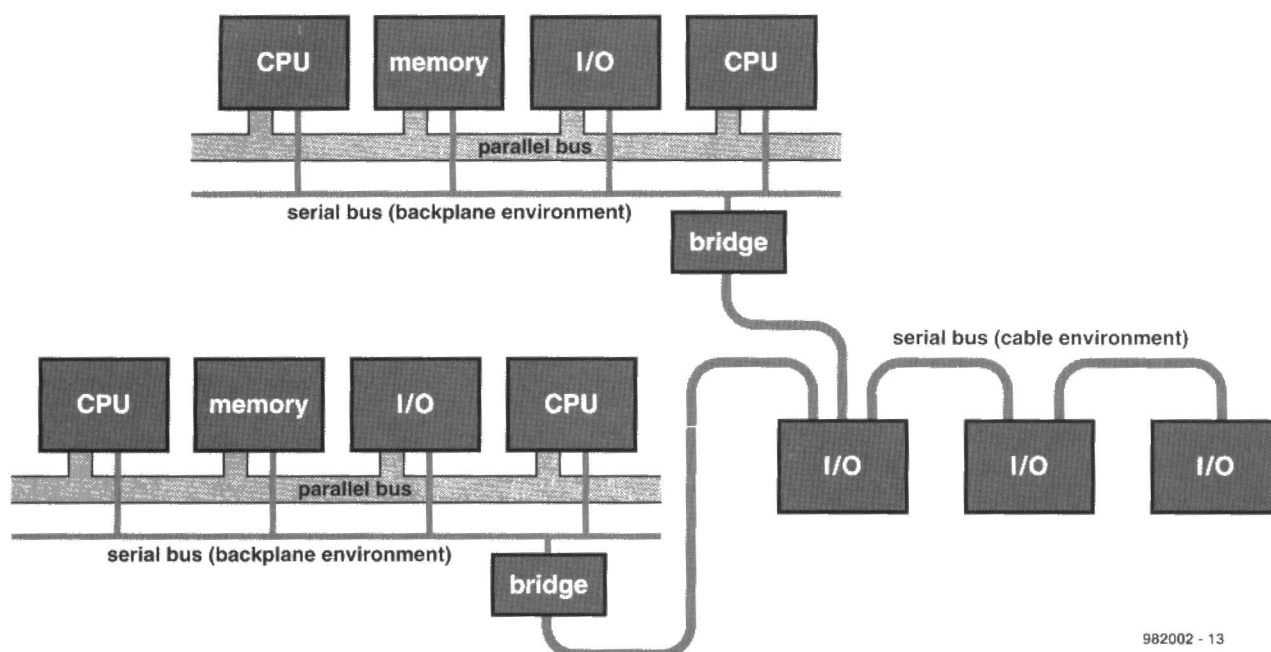

982002 - 13

Figure 3. Two computers communicate with each other and with peripheral devices via FireWire. Note that FireWire is used for both the cable connection and the backplane.

Since FireWire is based on high data rates, it places unusually severe demands on the cabling material. While USB works with a 4-lead cable, FireWire uses a 6-lead cable. This is illustrated in **Figure 4**. Two leads are reserved for distributing electrical power. The allowed dc voltage may lie between 8V and 40V, with a maximum total current of 1.5A. The signal lines are implemented as two individually-screened twisted pairs.

The model

The specification of the FireWire protocol is based on three *layers*: the Transaction Layer, the Link Layer and the

Physical Layer. These are depicted in **Figure 5**.

Transaction Layer

The Transaction Layer manages data transfers between two devices via the Serial Bus. The system recognizes three types of transactions: *read* (data is transmitted from a device to the main system), *write* (data is transmitted from the main system to a device) and *lock* (data is transmitted from a device to the main system, which in turn sends the processed data back to the device). The bus supports the IEEE 1212 standard, which uses 64-bit addressing. The topmost 16 bits of the address are treated as an identifica-

tion code (node ID) within each device. The 16 bits of the node ID are further divided into a 10-bit bus ID and a 6-bit offset ID. Since the highest possible address (all one's) is reserved for special applications, an actual system configuration can have up to 1023 buses, each of which can have up to 63 independent device connections (nodes).


Link Layer

The Link Layer looks after delivering information packets according to a half-duplex protocol. Each individual packet is sent via a process called a *subaction*. Two types of subaction are possible:

- *asynchronous subaction*, in which an arbitrary amount of data plus some Transaction Layer information is sent to a specific node (device address), following which a confirmation (acknowledgement) is returned from the destination device;
- *isochronous subaction*, in which a variable amount of data is sent at regular intervals, with simplified addressing and without confirmation from the destination device.

Each subaction can have up to three distinct phases:

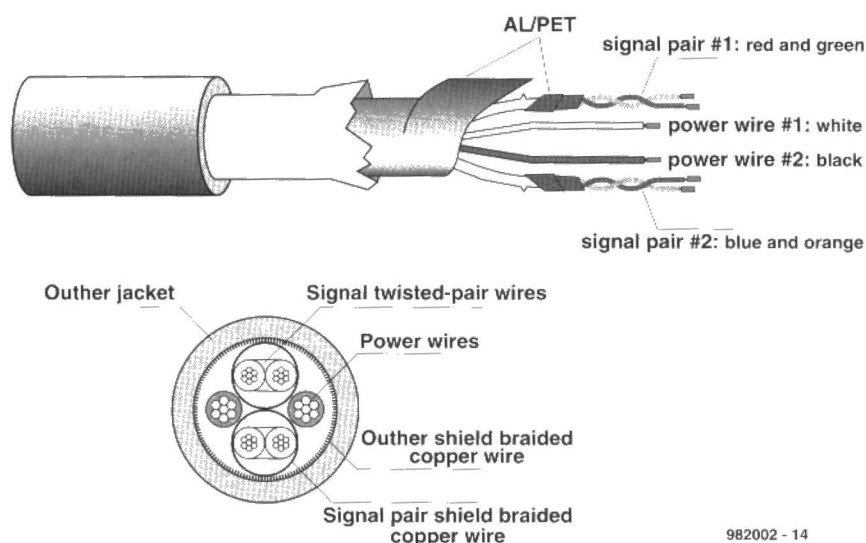- *arbitration sequence*: a device which wants to transmit data sends a bus access request to the Physical Layer. If the device already controls the bus as the result of a just-completed subaction, it receives immediate access to the bus.



982002 - 14

Figure 4. The construction of a cable which is suitable for FireWire.

- **data packet transmission:** the source device transmits a data packet containing coded speed, format and transaction information, the addresses of the source and destination devices and the data. Isochronous packets contain a short channel identification code (ID) in place of the addresses of the sender and receiver.

- **acknowledgement:** a uniquely-addressed destination device will return a confirmation code which indicates that the data was properly received and contains information regarding the action taken on receipt of the data. Isochronous subactions and asynchronous broadcast subactions do not require acknowledgement.

All asynchronous subactions are normally separated from each other by short intervals during which the bus is in an 'idle' state; these are called *subaction gaps*. An additional gap occurs in the interval between the completion of the data packet transmission and the receipt of the acknowledgement. The length of this gap depends on the physical system configuration. **Figure 6a** depicts the organization and timing of asynchronous subactions. Gaps also occur between isochronous transmissions; these are called *isoch gaps* and are depicted in **Figure 6b**.

Physical Layer

The Physical Layer has three functions. First, it translates the logical levels of the Link Layer into electrical signals for the cable, and in the reverse direction

it translates signals from the cable back into proper logical levels for the Link Layer. In addition, it determines the actual electrical and mechanical configuration of the connection. Finally, the Physical Layer acts as a sort of referee which grants devices access the bus when they wish to send data.

The future is what counts

USB and FireWire have a lot to offer. Although the first equipment to use these interfaces (both computers and

peripheral devices) is already appearing on the market, it's still too early to proclaim that the serial bus interfaces will be a great success. A few years will be necessary before this can be judged. Readers who wish to follow further developments in this area can keep a good eye on them via the Internet. Information about USB can be found at <http://www.usb.org>, and FireWire has its own site at <http://www.firewire.org>.

(FRED KOP)

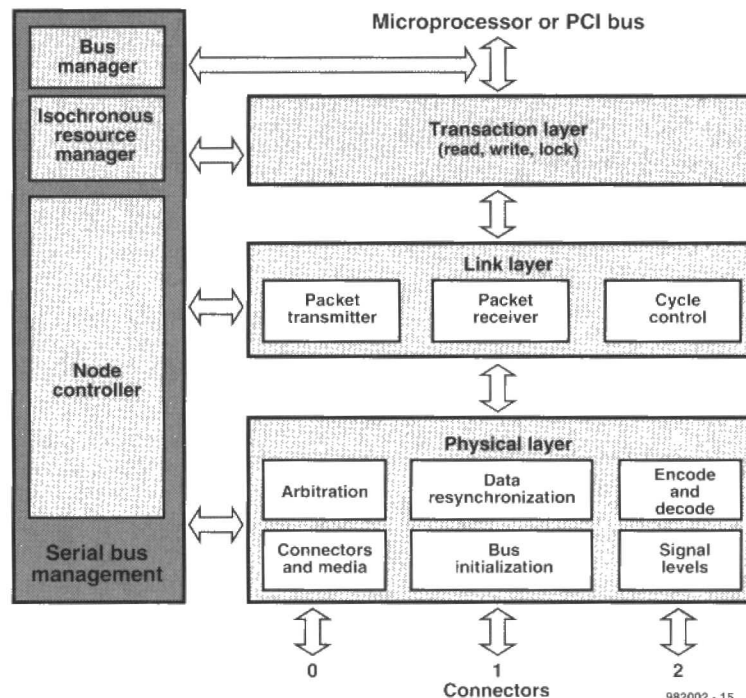


Figure 5. The FireWire protocol has three layers which communicate with each other.


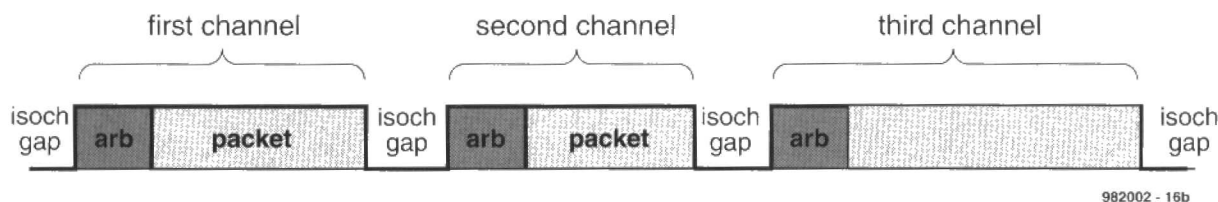
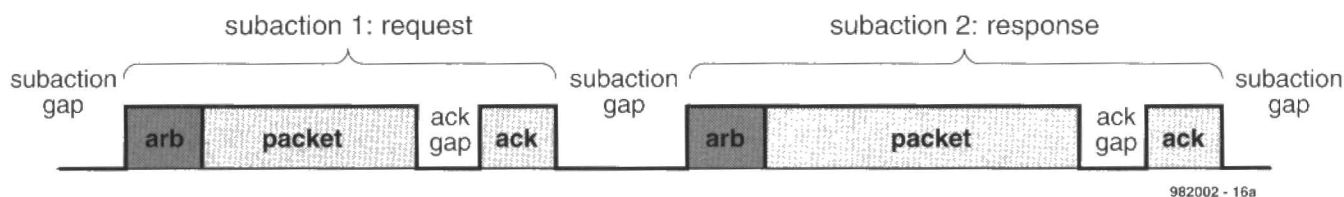


Figure 6. This timing diagram illustrates the difference between data transmissions using asynchronous subactions (a) and isochronous subactions (b).

Design by B. Oehlerking

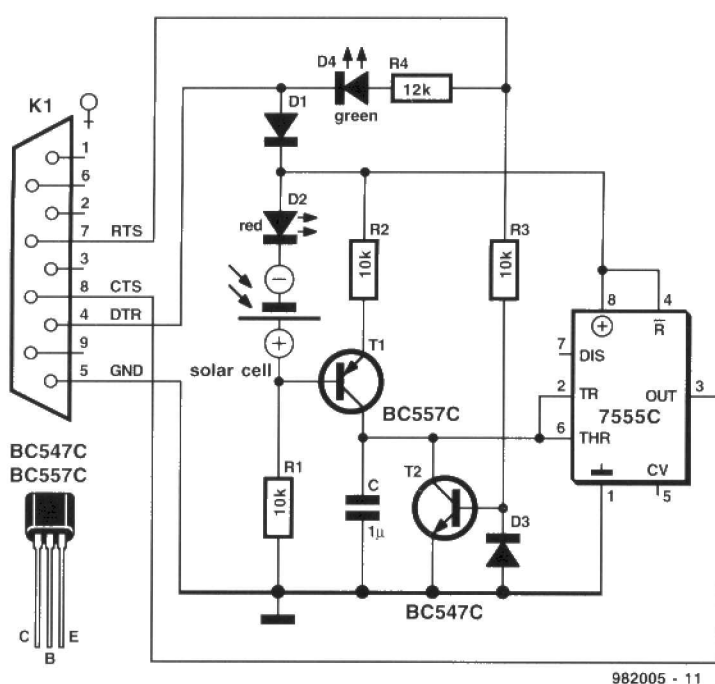

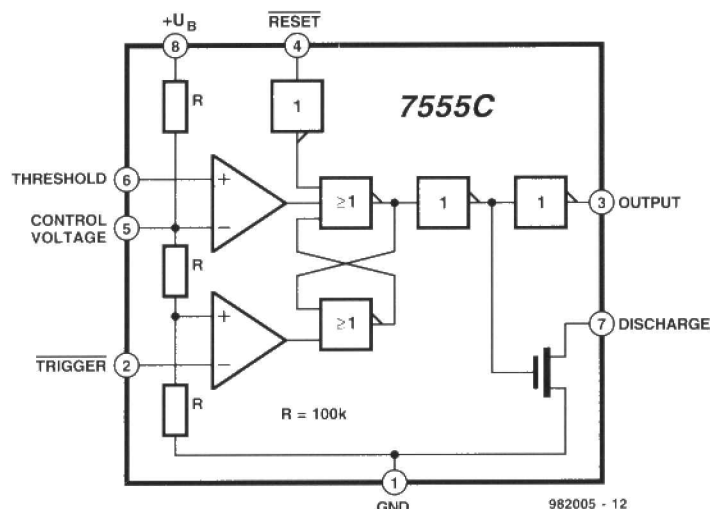


Figure 2. Internal structure of the TLC7555 CMOS timer used in the circuit.

Table 1.

DTR	RTS	D4	D2	CTS
off = -10 V, on = +10 V		red	green	off = 0 V, on = +10 V
off	off	off	off	off
on	off	off	on	off
off	on	on	off	off
on	on	off	on	on

charging is inversely proportional to the measured light intensity.

Figure 3 shows the flowchart of a suggested program which measures and evaluates the time interval. Admittedly, a software loop is not an ideal solution since it makes the program dependent on the speed of the computer used. Unfortunately, Visual BASIC offers no alternative when it comes to time measurement at reasonable accuracy. The program you find on the disk with order number **986002-1** (see Readers Services page) is only intended as an example to help you write your own software for the interface.

Because most RS232 interface lines are at ± 10 V, diode D1 is needed as a polarity reversal protection. Diode D3 prevents a too negative potential at the base of T2.

Construction of the circuit should be

straightforward. The few parts that go into the circuit are easily fitted on a small piece of veroboard or strip-board. The solar cell mentioned in the parts list (450 mV) has two screw connections at the back, which double as mechanical fasteners and electrical contacts. The interface is connected to the PC by way of 2 to 3 metres long 10-way flatcable (of which only four wires are used), which is connected to the circuit using an IDC (clamp-on) connector, and to the PC's RS232 port via a 9-way sub-D socket.

The program offering a test mode in which DTR and RTS may be controlled separately, the hardware may be tested with relatively simple means. The test program also reads the status of the CTS line. The consequences of the different levels of DTR and RTS for the LEDs and the CTS line are listed in Table 1.

(9852000)-1

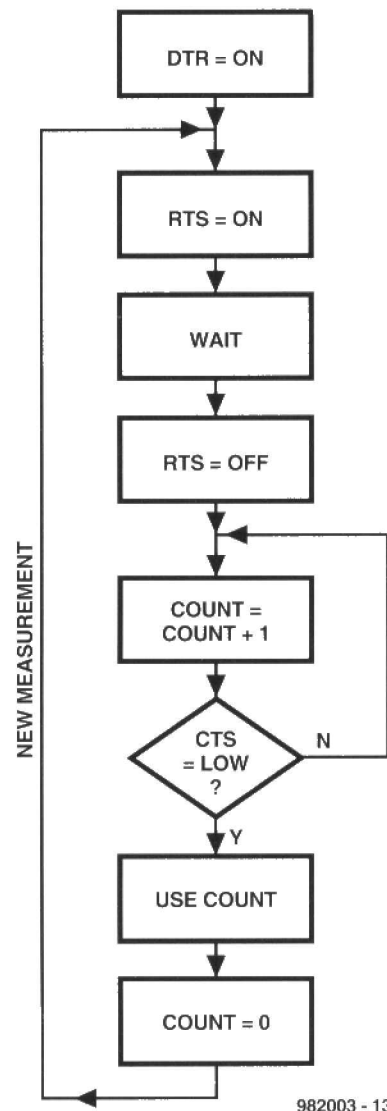


Figure 3. Structure of the demo and test program written in Visual BASIC. The full program is available on disk.

ULTIBOARD Studio
FOR PRIVATE USE AT £69
ULTIBOARD STUDIO LITE INCL. VAT

AFFORDABLE BY EVERYONE...

The Studio Lite consists of ULTIcap schematic capture, ULTIboard PCB design and ULTroute GXR autorouter. Both Windows 95 and DOS versions are included in the CD-ROM. Actually you only pay for the 5 manuals! In which, besides tutorials and manuals, even shapes are described! Ideal for hobby and study and with sufficient capacity (500 pins). If higher capacity is needed you can opt (now or later) for an upgrade to the Studio Unlimited, without capacity limits, for £ 68 (incl. VAT). There are no further options or hidden extras, the ULTIboard Studio program is complete!

ULTIMATE TECHNOLOGY
Unit 1, Lodges Barn, Coxbury Lane,
St. Briavels, Lydney, Glos GL15 6QJ
phone: 01594-810100
fax 01594-810200

SEE ALSO THE ADVERTISEMENT ELSEWHERE IN THIS ISSUE

electronics on-line

no more peeping



Toms on the Internet

New and very unwelcome on the Internet are traders who secretly collect personal data on web users. The tiniest amount of personal information seems to be sufficient these days to enable these peeping Toms to reach final conclusions about your interests and preferences. Despite massive protests of data protection authorities, there is brisk trade in databases compiled in this way. As a result, the unwitting web user is bombarded with megabytes of unsolicited information (junk mail) from less reputable Internet traders.

Browsing the Internet invariably leaves traces on your own PC as well as on the network server of your ISP (Internet Service Provider). For example, each site you visit is recorded in the History file, and you make your e-mail address known to the server with each download. Along with this address comes a lot of personal data that belongs with your account. Web users will create bookmarks, compile URL lists and 'favourites' folders. An increasingly popular way of collecting data is by means of cookies. These are small files containing individual data, which are stored on the web user's PC for easy retrieval by Internet traders. Mind you, cookies can be very useful, for instance, to keep a permanent record of, say, your client number with a certain supplier, or other salient information. In this way, cookies avoid the hassle of typing personal data over and over again as you come back often to a certain web site.

Unfortunately, this information also lends itself to illegitimate use, and there is a disturbing increase in the number of cases in which this has actually happened. Although all modern web browsers allow users to reject cookies, actually doing so is annoying because the repeated warnings tend to slow you down when time is at a premium (always remember your phone bill). In some cases, it is even impossible to access a web site without accepting a cookie.

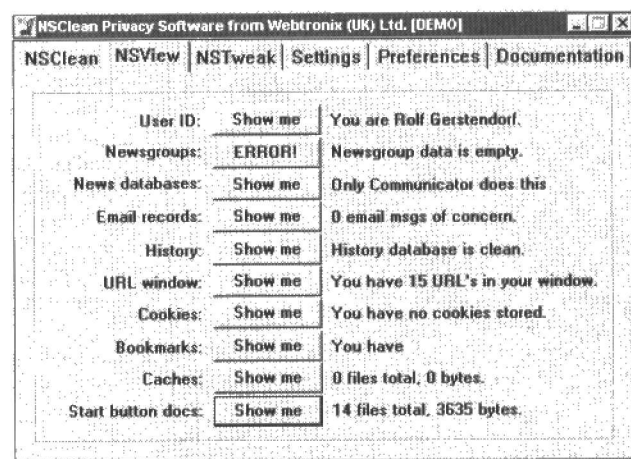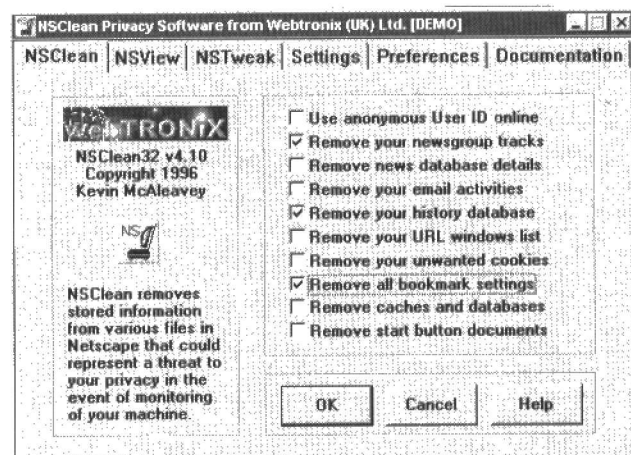UK-based Internet provider Webtronix now offers a program called NSClean (for Netscape) or IEClean (for Internet Explorer) which records all access to the various memories (hard disk and cache) as you surf the Internet, and destroys all traces again the moment you log off. The home page



of Webtronix may be found at <http://www.webtronix.co.uk/wsc.htm>. The programs are capable of detecting the various targets areas (History folder, URL window, cookies, bookmarks, etc.), allowing targeted clearing or retaining of individual areas (including individual entries).

Another interesting feature of NSClean and IEClean is the in-built alias function. At the press of a button, you can change your e-mail address into a fictitious one, for as long as the PC is on-line. In this way, you do not (unwittingly) disclose your identity when accessing an ftp site.

NSClean and IEClean cost £29.95 for the 16-bit Win3.x version, or £34.95 for the 32-bit Windows95/NT versions. Credit card owners may download the programs straight away. Obtaining this software by ordinary mail is also possible, P&P is then £5.

(985013-1)

introduction to digital signal processing

Part 2 Sampling and digital filters

After last month's brief excursion into sampling, this instalment takes a look at the effects sampling has and then takes the first steps into digital filter technology.

Shannon's sampling theorem (1949) states that, in a pulse-coded system, two samples per cycle will completely characterize a band-limited signal, that is, the sampling rate must be twice the highest-frequency component. In practice, the sampling rate is at least five times the highest frequency.

It will be seen that the theorem is invalidated when the highest frequency is more than half the sampling rate.

SOUND PROGRAMME

MUSIC1 <return> generates a sound programme of 60 single tones, each separated from the next and preceding one by a semitone. The lowest frequency is 40 Hz and the highest 14 kHz, that is, the programme spans a range of more than five octaves. The tones are sampled by MUSIC1.WAV at a rate of 44.1 kHz. The conditions of the theorem are fulfilled, which is verified by a good audible sound.

UNDERSAMPLING

If the sound generated in the previous paragraph is sampled at a rate of only 11,025 kHz, that is 1/4 of the original rate, we speak of undersampling (see Figure 3). It is executed by DWN

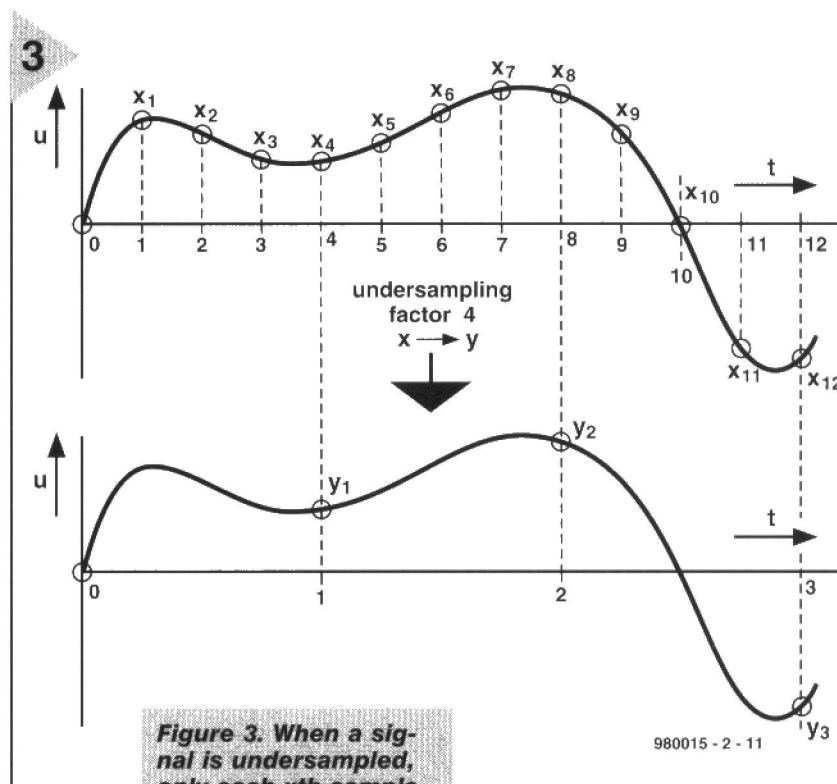


Figure 3. When a signal is undersampled, only each x th sample is taken.

SMPL1.EXE, whereby

MUSIC1.WAV is converted to a file MUSIC2.WAV. The undersampling factor is indicated by DWN\$MPL1\inp =MUSIC1.WAV\ out =MUSIC2.WAV\factor=4 <return>. This means that only tones lower than $11,025/2=5512.5$ Hz can be reconstructed properly. Sampling of the higher-frequency tones results in a phenomenon known as aliasing. This gives rise to a tone erroneously taking on the identity of an entirely different frequency when recovered.

ALIASING FREQUENCIES

Aliasing frequencies are not random: they can be accurately predicted. If, for instance, a sinusoidal signal of frequency $f_0 < f_s/2$ is sampled at a rate equal to f_s , definite sample values are obtained. Each signal of frequency $m(f_s - f_0)$ or $m(f_s + f_0)$, where $m=1, 2, 3, \dots$, generates the same sample values associated with f_0 - see Figure 4.

After sampling has taken place, these frequencies cannot be distinguished from one another. To prevent

Aliasing

The effect of aliasing may be compared to that seen on a cinematographic or video film when a spoked wheel of a vehicle turns at such a speed that successive samples (frames of the film) catch the wheel at slightly earlier or later positions. Between one frame and the next a spoke turns to almost the same position as formerly occupied by an adjacent spoke. The result is to make the wheel appear to rotate much more slowly or even backwards.

this situation arising, an analogue-to-digital converter (ADC) is usually preceded by a low-pass filter that suppresses the aliasing frequencies.

LOW-PASS FILTER

The low-pass filter used to suppress aliasing frequencies must be a digital type. Digital filtering is completely different from analogue filtering. Analogue filtering processes signals in the frequency domain, whereas digital filtering does so in the time domain. So, if a certain frequency domain response is required, it is necessary to convert this response into the equivalent time domain. So, let us see what happens when we try to use an analogue filter (see Figures 5 and 6).

During a sampling interval $\Delta T = t_{k+1} - t_k$, input voltage u changes but little, but attains the value u_k . The output voltage will not change much either, so that an almost constant current $i = (u_k - v_k)/R$ flows through resistor R . At the onset of the sampling interval, the potential across the capacitor is v_k . It is charged by i during the sampling period to attain the potential

$$v_{k+1} = v_k + i \Delta t / C = v_k + (v_k - u_k) / RC \Delta t.$$

If we solve this for u_{k+1} , we obtain

$$v_{k+1} = r v_k + u_k (1 - r), \text{ where } r = 1 - (\Delta t / RC).$$

This is the calculation prescription for the first digital filter. The program is on the CD-ROM under the title LP1.EXE; the source code, LP1.PAS is given in Figure 7.

The example shows that not all programs for digital signal processing need to be long and tedious. It is, of course, admitted that most of the routine work has been done by program library SIGLIB.PAS.


The filter is tested by processing file MUS1.WAV (also listen to it!) on the CD-ROM. This is done by calling up

```
lp1 \r=0.995 \scale=10 \inp=
mus1.wav \out=tmp.wav <return>.
```

Listening to the resulting signal makes the distinction between tmp.wav and the original signal very clear.

Some experiments may be carried out with the filter. For instance, try out several values for r , but note that this should not be greater than unity to prevent the filter becoming unstable.

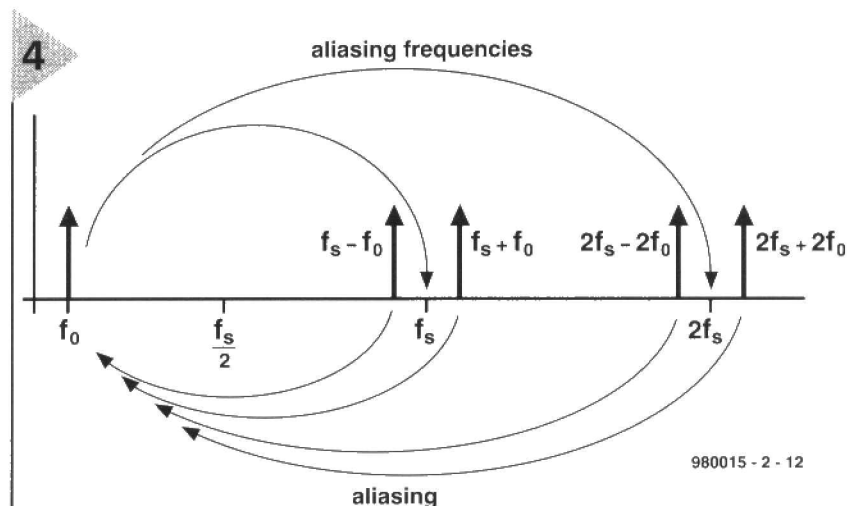Just listening to a filter's performance is, of course, not the best test. For a proper test, a couple of test signals are needed to analyse, say, the frequency response in the time and frequency domains. These signals may be derived from a pulse generator.



980015 - 2 - 12

Figure 4. Aliasing causes equivalent frequencies to be produced from dissimilar samples.


PULSE GENERATORS

The CD-ROM contains a couple of pulse generators. The first and simpler is indicated by PULSE1.EXE. This generates a very brief pulse that has only one sampling value which is not zero: the value of all others is zero. The position and amplitude of the pulses can be set by relevant parameters. This elementary signal is very important and will be used frequently in experiments later in this series of articles.

Another pulse generator is found under STEP1.EXE. This generates a simple step signal with predestined amplitude and position. For instance, calling up DO XLP1.SPP generates the signals shown in Figure 8. That at the top represents the reaction of filter tmp.wav to pulse1.wave, and that at the bottom, tmp.wav, the slowly rising response to step1.wav.

As before, this experiment may be repeated with various values of r . For instance, what happens when $r = -0.9$? However, this kind of response does not give a very clear picture of the performance of the low-pass filter. A better one is obtained by the use of a sweep generator, which is also available on the CD-ROM.

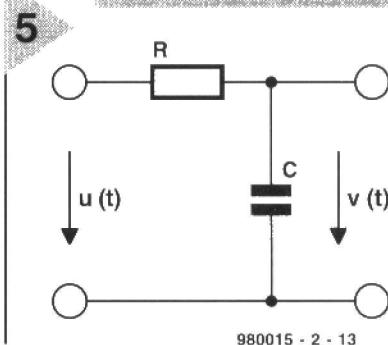When DO XLP2.SPP <return> is called up, a sweep sig-




980015 - 2 - 13

Figure 5. An RC network used as an analogue low-pass filter.

nal of 1–1000 Hz is generated (top of Figure 9) and applied to the low-pass filter. The amplitude of the output signal (at the bottom) drops with rising frequency.

Another possibility is to apply white noise to the filter and view the output signal. But for that purpose, it is necessary to first analyse and examine signal spectra.

Figure 6. Step response of the digital low-pass filter.

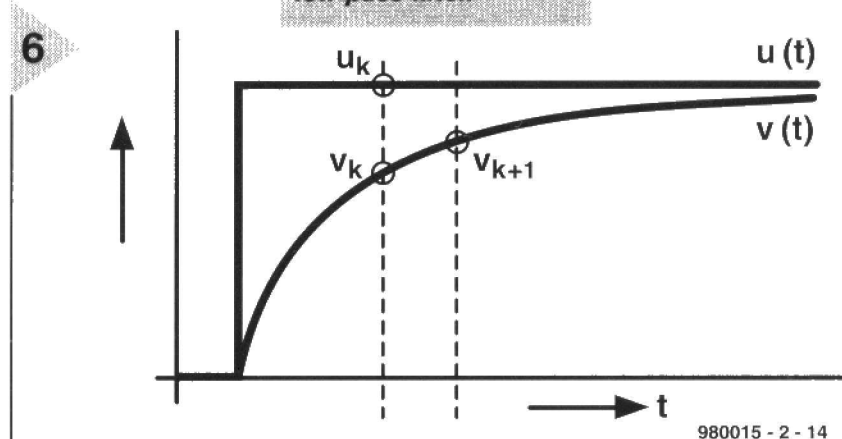

980015 - 2 - 14

7

```

001 program lpl ;
002 uses dos,crt,graph ;
003
004 {$I SIGLIB.PAS }
005
006 var k:int ;
007     y,scale,r:float ;
008
009 begin
010 start('simple lowpass') ;
011 scale:=1.0           ; set par real('\scale=',scale) ;
012 r:=0.95              ; set par real('\r=',r) ;
013 inp fn:='puls1.wav'  ; set par string('\inp=',inp fn) ;
014 out fn:='tmp.wav'    ; set par string('\out=',out fn) ;
015
016 open inp(inp fn) ;
017 open out(out fn) ;
018
019 y:=0 ;
020 for k:=1 to nsamples do
021 begin
022 output(scale*y) ;
023 y:=r*y+(1-r)*input ;
024 if (k mod 2000)=0 then write('.') ;
025 end ;
026 stop ;
027 end.

```

Figure 7. Pascal source code for the digital filter.

SPECTRUM ANALYSER

An introduction to DSP would not be of great value without a facility to view, examine and analyse signal spectra. Therefore, the CD-ROM contains program SPEC1.EXE (source code SPEC1.PAS) which enables the spectra of wave files to be calculated and viewed.

To calculate a spectrum, SPEC1.EXE uses a discrete Fourier transform (DFT), which derives $n/2$ amplitudes

that are associated with frequencies 0 Hz (d.c.) to $f_c/2$ from n values. In the present program, $n=4096$. The amplitude levels are shown on a logarithmic

Figure 8. Pulse and step response of the low-pass filter.

Lines 1–5 form the head of the program and declare that program library SIGLIB.PAS will be used.

Lines 6–7 stipulate the requisite variables when line 10 calls up the initialization of SIGLIB.PAS

Lines 11–14 determine the parameters; if required (owing to procedures in SIGLIB.PAS) the actual parameters called for by the program.

Lines 16–17 actuate the data input and output of the WAV files.

Line 19 initializes the value of the filter. The procedure in lines 20–25 executes the actual filter operation.

In line 22, the actual output value of the filter is written in the output data file.

Line 23 contains the actual filter algorithm.


Line 26 closes all files and thus the program.

scale to obtain a wider range of values.

Experiment XSPEC1.SPP generates two signals of frequency 193.7988 Hz (tmp1.wav) and 196.4905 Hz (tmp2.wav) respectively from 4096 samples at a rate of 44.100 samples/s. If the DFT is applied to these signals, the spectra shown in Figure 10 are obtained.

It appears as if the first signal (tmp1.wav – top left) consists of only

8

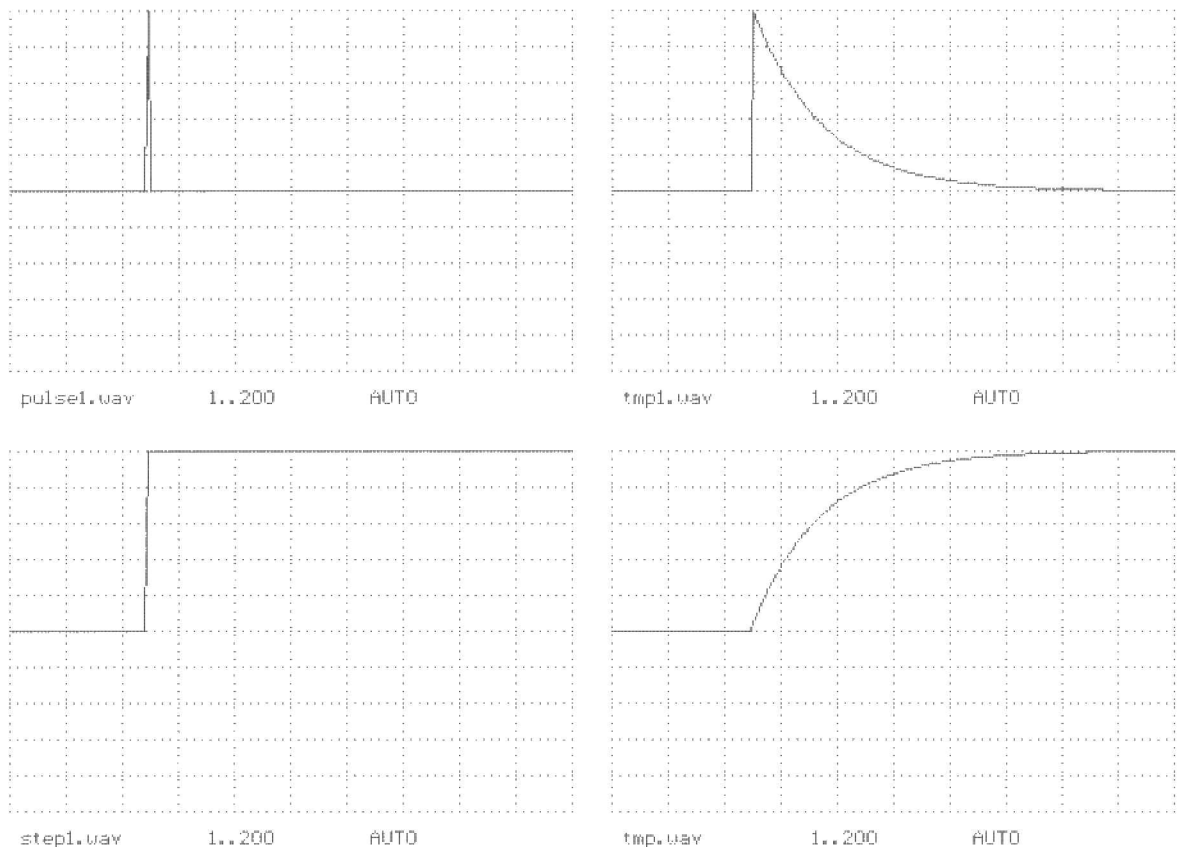

980015 - 2 - 16

9

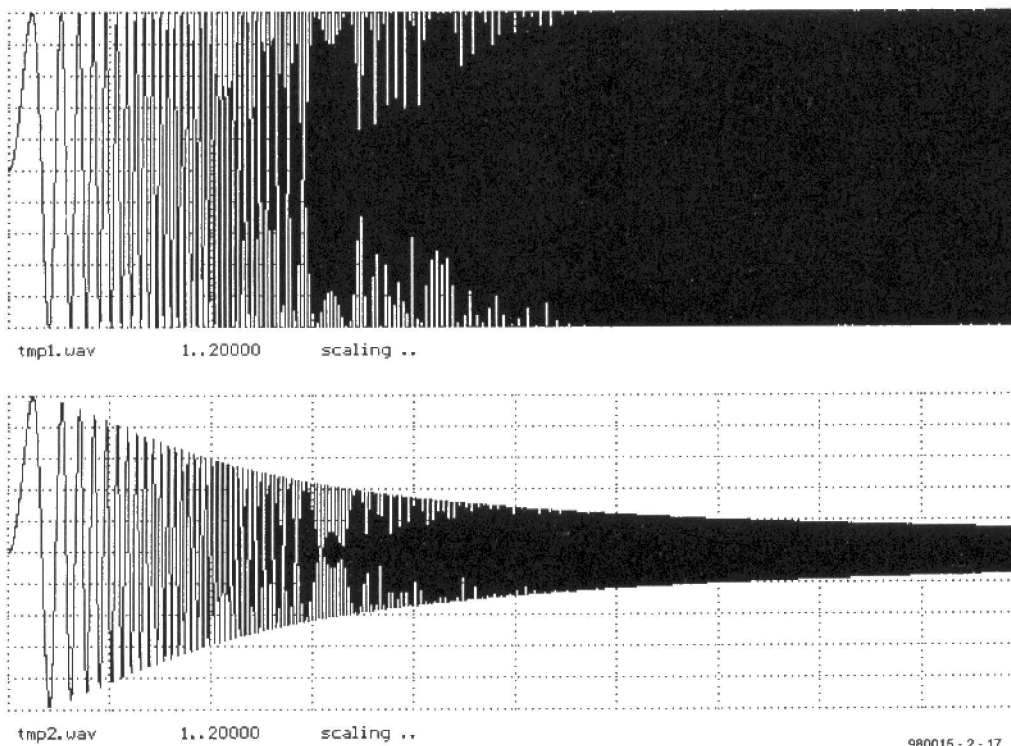


Figure 9. Passage of a signal from a sweep generator through a low-pass filter.


Figure 10. Spectra of sinusoidal signals: at the top without the window function, and at the bottom with it.

one frequency. On the other hand, the second signal (tmp2.wav – top right) has a 20 dB peak, but the spectrum at either side does not drop off very much.


How does the DFT conclude that there are some of a great

many frequencies in the signal? The answer lies in Figure 11, which shows that in the case of signal tmp1.wav a whole number of complete cycles fits exactly in the region enclosed by the 4096 sampling points. This is not so in case of the other signal. The value of


10

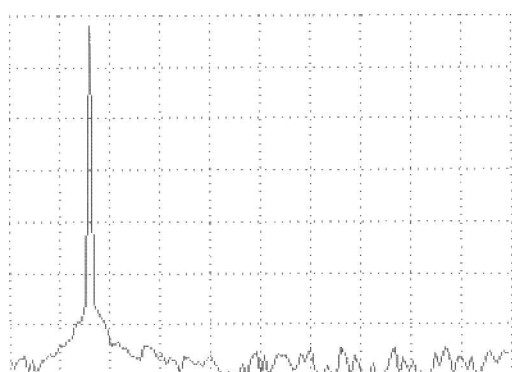


tmp1.wav ya = 0.0 yb = 140.0
fa = 0.0 fb = 1200.0 cur = -1.0

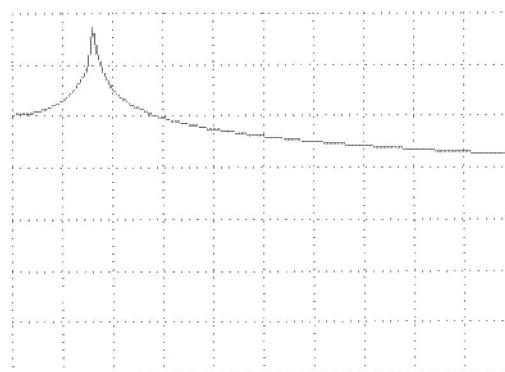

tmp2.wav ya = 0.0 yb = 140.0
fa = 0.0 fb = 1200.0 cur = -1.0

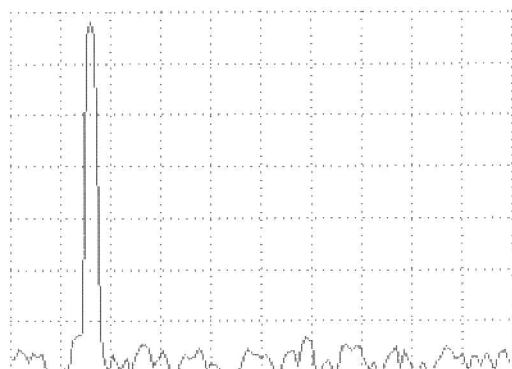

tmp1.wav (w) ya = 0.0 yb = 140.0
fa = 0.0 fb = 1200.0 cur = -1.0

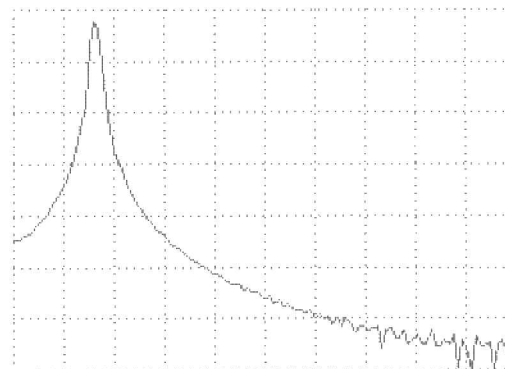

tmp2.wav (w) ya = 0.0 yb = 140.0
fa = 0.0 fb = 1200.0 cur = -1.0

980015 - 2 - 18

11

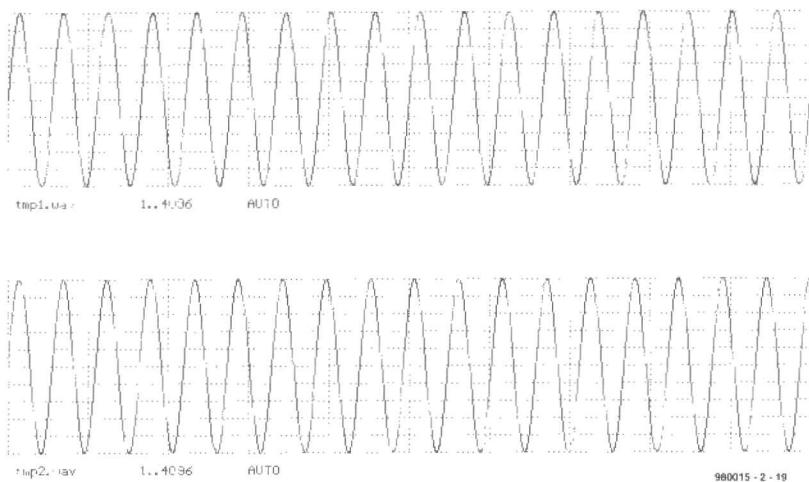


Figure 11. Signals may fit well or not so well in the window of the spectrum analyser.

this signal at the left is 0, while at the right 18.5 cycles fit in the 4096-point region. Because of this, all possible oscillations are required (and thus shown up by the DFT) to display the signal.

WINDOW FUNCTION

Obviously, the situation in the previous paragraph is not satisfactory, since the DFT should generate a line-shaped spectrum of signal tmp2.wav also. This is obtained when the input signal is multiplied (top of Figure 12) by a window function (at the centre). This signal then undergoes a DFT and results in that displayed at the bottom.

The window function ensures that the signal becomes compatible with


the DFT. The spectra of the signals subjected to the window function are shown at the bottom of Figure 10. It will be seen that the spectrum of tmp2.wav is now clearly line-shaped, but that the line produced by tmp1.wav has broadened slightly – this is the price to be paid for the window function. The spectrum analyser on the CD-ROM gives a choice of working with or without the window function. The window function will be met again when filter synthesis will be discussed.

Next month's instalment will continue with the subject of filtering and also deal with the spectrum analysis of some real signals.

[980015-2]

Figure 12. Windowing is simply the multiplication of the signal with a window function.

12

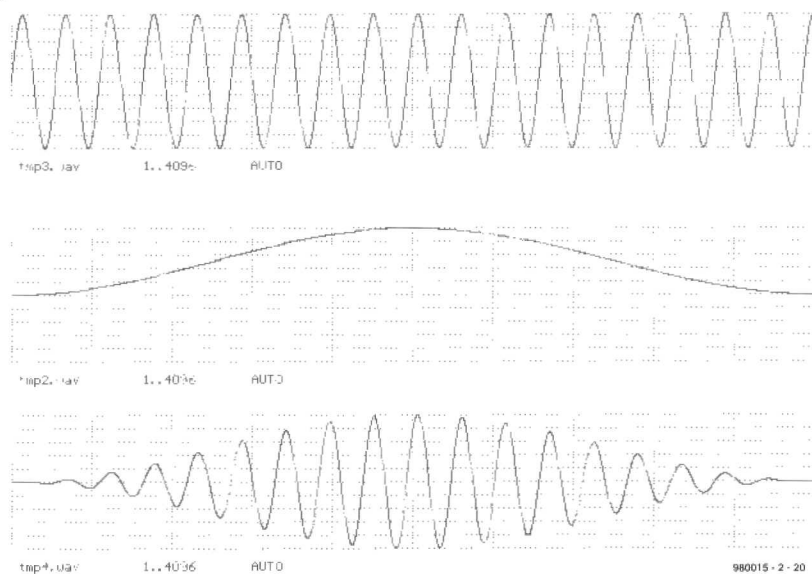

Chaotic Minds

Working neatly and efficiently is considered by many to be a virtue. Our mums and teachers told us to work neatly and we pass the word on. But does all that order and tidiness really get us anywhere? Do these virtues serve any higher purpose?

I'm not so sure, you know. At least, I have reasons to start doubting. Look at hobby gardeners. The biggest tomatoes and the finest lettuce always seem to grow in chaotic little gardens with a drab little tool shed built from totally unrelated parts. By contrast, you will find that the 'neat' gardener with his built-from-a-kit shed or weather-proof garden box is constantly bogged down by bad luck, bugs and what have you, and he or she can just about manage to grow a decent cabbage.

Similar observations apply to many electronics designers. The most ingenious circuits and original ideas seem to spring from the minds of people whose desktop alone presents a view that throws the neat-minded into a fit. Behind such a desk, cluttered with all things real and beyond imagination, sits a designer, peacefully being ingenious. His spectacles are held together by pieces of sticking plaster, and he doesn't seem the slightest bit worried about the fact that he's wearing two different socks.

You should suppress any tendency you may suddenly feel to give him a good talking to about tidiness. It's not only pointless, but even dangerous! I have heard of a case where a sheer genius, after a short absence from his beloved desk, was confronted with a working room cleaned up (or out) by his spouse. He could not bear it. Although about a year long intensive treatment in a psychiatric clinic has made him reasonably communicative again, I doubt he will ever return to his former self.

What sort of person are you? A genius, a clever sloven, or just a sloven? Don't worry about it, you are in good company. Men like Socrates, Mozart, Einstein and Marconi were not exactly famous for tidiness. Still, you can't deny that they had very well-structured thoughts about various things that really matter.

S. van Rooij

AM/FM antenna impedance matching IC



The U4253BM and U4254BM ICs are integrated AM/FM antenna matching circuits in bi-CMOS* technology. They are intended particularly for car applications and may be used with wind-screen, roof and bumper antennas. The U4254BM chip has a lower noise figure than the U4253BM and a different AM amplifier stage with two outputs. Apart from the additional AM output (pin 11 which is not connected in the U4253BM), the pinouts of the two devices are identical.

FUNCTIONAL DESCRIPTION


The U4253BM/U4254BM impedance matching circuit (see block diagram in Figure 1) compensates for cable losses between the antenna and the car radio which is usually placed far away from the antenna.

The FM amplifier provides excellent noise performance. External components are used to adjust the gain and

* Integrated circuits that contain both bipolar and CMOS transistors. This combination allows the advantages of both processes to be exploited.

A TEMIC Semiconductors Application

Figure 1. Block diagram of the AM/FM antenna impedance matching IC.

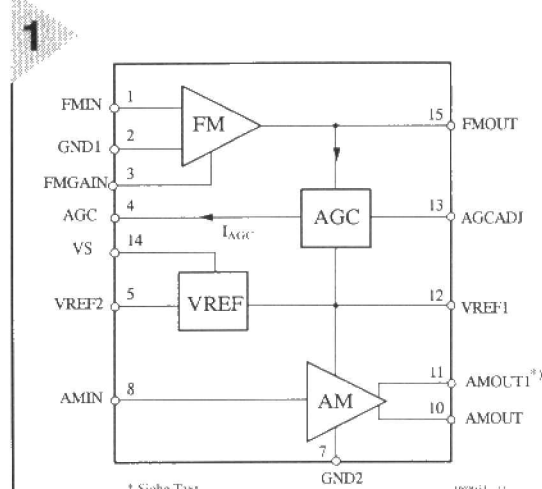

the input-output matching impedance. Therefore, it is possible to adjust the amplifier to various impedances (usually 50, 75 or 150 Ω).

To protect the amplifier against input overload, an Automatic Gain Control (AGC) is included on the chip. The AGC observes the a.c. voltage at

resistor which is connected between FMGAIN and GND1. To influence the a.c. gain of the amplifier, a resistor is connected in series with a capacitor between FMGAIN and GND1. The capacitor has to be a short at frequencies ≥ 100 MHz.

AGC (pin 4)

Direct current flows into the AGC pin at high FM antenna input signals. This current has to be amplified via the current gain of an external p-n-p transistor that feeds a p-i-n diode. This diode dampens the antenna input signal and

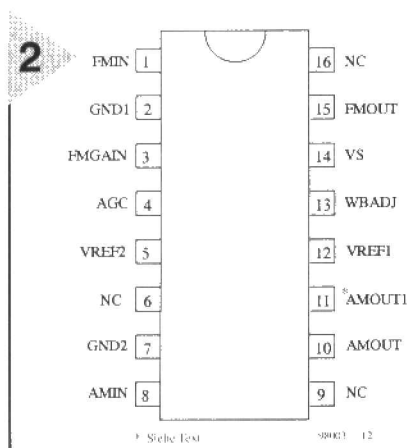


Figure 2. Pinout of the AM/FM antenna impedance matching IC.

the FM amplifier output, rectifies this signal, and delivers direct current to dampen the input antenna signal via an external p-i-n diode.

The threshold for the AGC is adjustable. Simple and temperature-compensated biasing is possible owing to the integrated voltage reference V_{Ref2} .

The AM part consists of a buffer amplifier. The voltage gain of this stage is about unity. The input resistance is 470 k Ω and the input capacitance less than 10 pF. The output resistance is 125 Ω . An excellent dynamic range is achieved owing to the CMOS source follower stage.

PIN DESCRIPTION

The pinout is shown in Figure 2. Note that pins 6, 9, 11 (U4253BM only), and 16 are not connected.

FMIN (pin 1) (Figure 3a)

FMIN is the input of the FM amplifier. It is the base of a bipolar transistor. A resistor or a coil is connected between FMIN and VREF2.

GND1 (pin 2)

To avoid crosstalk between AM and FM signals, the circuit has two separate ground pins. GND1 is the ground for the FM part.

FMGAIN (pin 3) (Figure 3b)

The direct current of the FM amplifier transistor is adjusted by an external

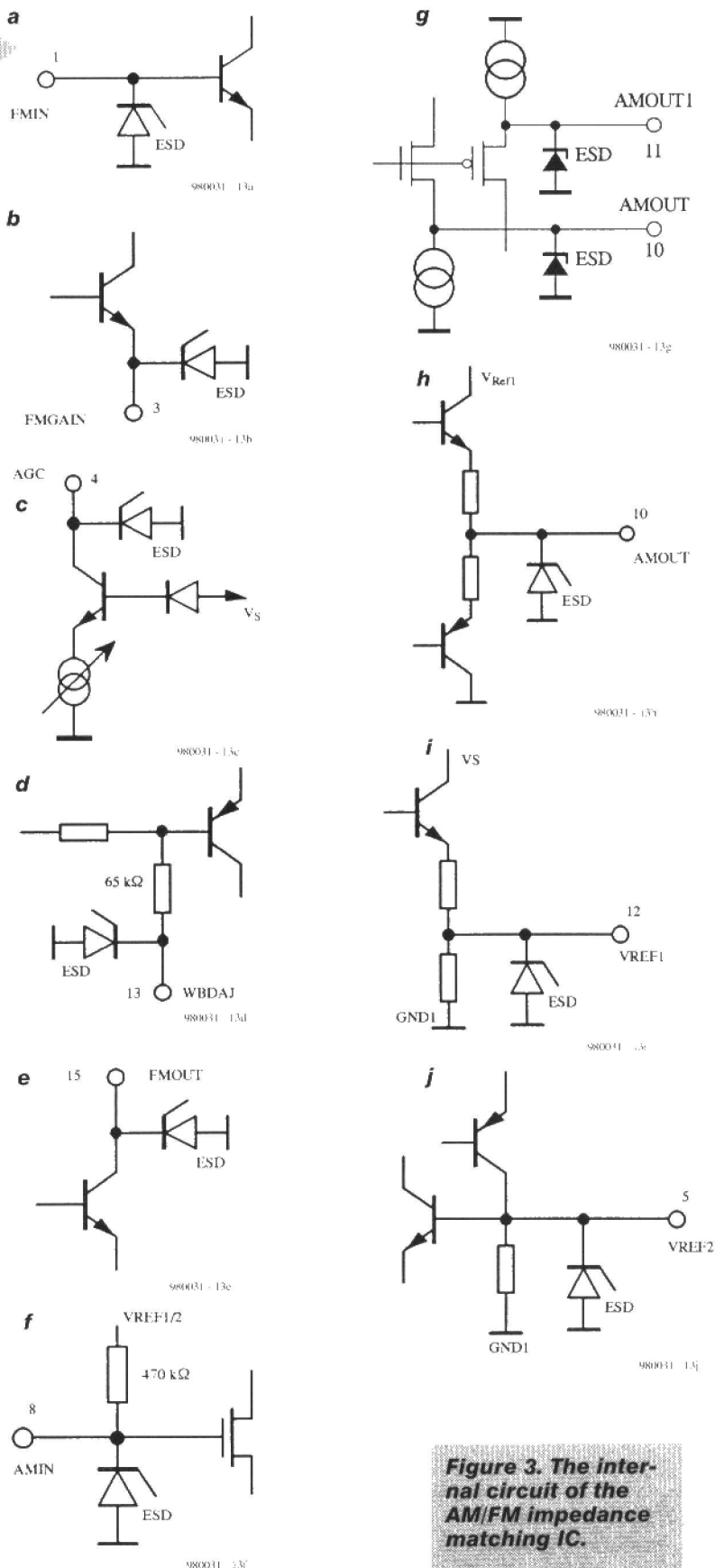


Figure 3. The internal circuit of the AM/FM impedance matching IC.

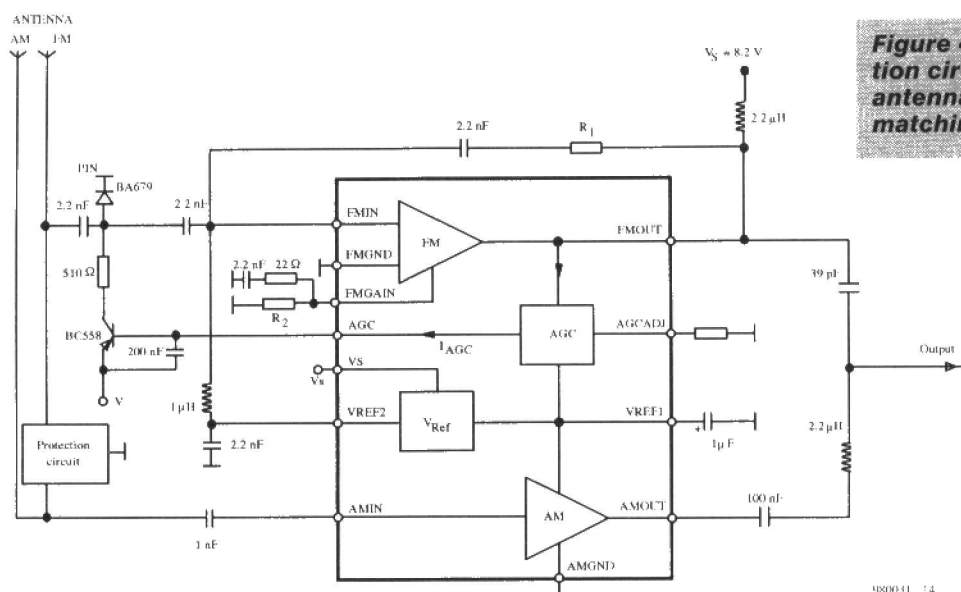


Figure 4. Typical application circuit of the AM/FM antenna impedance matching IC.

Table 1. Electrical Characteristics $V_S = 8\text{ V}$, $T_{amb} = 25^\circ\text{C}$, unless otherwise specified

Parameters	Test Conditions / Pins	Symbol	Min.	Typ.	Max.	Unit
Supply voltage	Pin 14	V_S	7.2	8	8.8	V
Supply currents	Pin 14	I_S		4		mA
Reference voltage 1 output, ($I_{12} = 0$)	Pin 12	V_{Ref1}		5.5		V
Reference voltage 2 output, ($I_5 = 0$)	Pin 5	V_{Ref2}		2.6		V
Temperature dependence of V_{REF2}	Pin 5	$V_{ref2}/\Delta T$		-1		mV/K
AM amplifier						
Input resistance	Pin 8	R_{AMIN}		470		k Ω
Input capacitance	Pin 8	C_{AMIN}			10	pF
Output resistance	Pin 10	R_{OUT}		200*		Ω
Voltage gain	Pin 10 / Pin 8	a		0,85		
Output noise voltage (rms value)	Pin 10, pin 8 to ground via 15pF; $B = 6\text{ kHz}$, 150 kHz to 300 kHz, 500 kHz to 6.5 MHz	V_{N1} V_{N2}		-2 -6		dB μ V dB μ V
2nd harmonic	Pin 10, pin 8 to ground via 15pF, $f_{AMIN} = 500\text{ kHz}$, Output voltage = 110 dB μ V		-60**			dBc
FM amplifier						
Supply current limit	I_{AGC} , $I_{AGCADJ} = 0\text{ A}$, Pin 15	I_{15}		33	35	mA
Input resistance	$f = 100\text{ MHz}$ Pin 1	R_{FMIN}		50		Ω
Output resistance	$f = 100\text{ MHz}$ Pin 15	R_{FMOUT}		50		Ω
Power gain	$f = 100\text{ MHz}$ Pin 15/ Pin 1	G		5		dB
Output noise voltage	Pin 15 $f = 100\text{ MHz}$, $B = 120\text{ kHz}$	V_N		0		dB μ V
3rd order output intercept	$f = 100\text{ MHz}$ Pin 15			132		dB μ V
AGC						
AGC input voltage threshold	$f = 100\text{ MHz}$ Pin 15 pin 13 grounded; AGC threshold DC current is 10 μ A at Pin 4	V_{th1}		96		dB μ V
AGC input voltage threshold	$f = 100\text{ MHz}$ Pin 15 pin 13 not connected; AGC threshold DC current is 10 μ A at Pin 4	V_{th2}		106		dB μ V
AGC output current	AGC active	I_{AGC}			1.2	mA

* 125 Ω for U4254BM

** -65dBc for U4254BM

protects the amplifier input against overload. The maximum current which flows into the AGC pin is about 1 mA. In low-end applications, the AGC function is not necessary and the external components can then be omitted.

VREF2 (pin 5) (Figure 3j)

For the d.c. biasing of the FM amplifier, a second voltage reference circuit is integrated. Because of temperature independence of the collector current, the output voltage has a negative temperature coefficient of about -1 mV K^{-1} . To stabilize this voltage an external capacitor of a few nF to ground is recommended.

GND 2 (pin 7)

This pin is the ground connection for the AM amplifier.

AMIN (pin 8) (Figure 3f)

The AM input has an internal bias voltage. The direct voltage at this pin is $V_{\text{Ref1}}/2$. The input resistance is about 470 k Ω and the input capacitance is smaller than 10 pF.

AMOUT (U4253BM only)

(pin 10) (Figure 3h)

This pin is the output of the AM amplifier in the U4253BM. The direct voltage at this pin is almost $V_{\text{Ref1}}/2$. The output impedance is about 200 Ω . The output capacitance is smaller than 10 pF.

AMOUT and AMOUT1 (U4254BM)

(Pins 10 and 11) (Figure 3g)

The buffered AM amplifier consists of a complementary pair of CMOS source followers. The transistor gates are connected to AMIN. Pin 10 is the NMOS transistor's source, whereas pin 11 is the PMOS transistor's source. Owing to the two different direct voltage levels at these pins, they have to be connected together via an external capacitor of about 0.1 μF . This technique enables an excellent dynamic range to be achieved.

VREF1 (pin 12) (Figure 3i)

VREF1 is the stabilized voltage for the AM amplifier and the AGC block. To achieve good noise performance at LW frequencies, it is recommended that this pin is connected to ground via an external capacitor of about 1 μF .

WBADJ (U4254BM)

AGCADJ (U4253BM)

(pin 13) (Figure 3d)

The threshold of the AGC can be adjusted by varying the direct current at this pin. If the pin is connected directly to GND1, the threshold is set to 96 dB μV at the FM amplifier output. If a resistor is connected between this pin and GND1, the threshold is

Table 2 – Features

- High dynamic range for AM and FM
- Integrated AGC for FM
- High intercept point 3rd order for FM
- FM amplifier adjustable to various cable impedances
- High intercept point 2nd order for AM
- Low noise output voltage
- Low power consumption

Table 3 – Absolute maximum ratings

Reference point is ground (pin 2 and 7)

Parameters	Symbol	Value	Unit
Supply voltage	V_s	8.8	V
Power dissipation, P_{tot} at $T_{\text{amb}} = 85^\circ\text{C}$	P_{tot}	460	mW
Junction temperature	T_j	150	$^\circ\text{C}$
Ambient temperature	T_{amb}	-40 to +85	$^\circ\text{C}$
Storage temperature	T_{stg}	-50 to +150	$^\circ\text{C}$
Electrostatic handling	$\pm V_{\text{ESD}}$	2000	V

Table 4 – Cable impedance vs resistor values

FM cable impedance (Ω)	R_1 (Ω)	R_2 (Ω)
50	150	22
75	270	33
100	390	51
125	470	86
150	620	160

shifted to higher values with increases resistance. If the pin is open, the threshold is set to 106 dB μV .

VS (pin 14)

This pin is linked to the positive supply voltage (7.2–8.8 V).

FMOUT (pin 15) (Figure 3e)

The FM amplifier output is the open collector of a bipolar r.f. transistor. It should be linked to VS via a coil.

TYPICAL APPLICATION

A typical application circuit is shown in Figure 4. In this, it is assumed that the antennas for reception of long-wave and medium-wave (LW/MW) signals and very-high-frequency (VHF) signals are of different lengths. The antennas are linked to the circuit via a protection circuit.

Whereas the AM antenna is linked directly to the input of the AM section via a 0.1 μF coupling capacitor, the FM antenna is connected to the FM section via a p-i-n diode attenuator. Before and after the attenuator cou-

pling capacitors block any direct voltage.

The antenna impedance is matched to the input impedance of the FM section by resistors R_1 and R_2 . The value of these resistors for various antenna impedances is given in Table 4.

The 1 μH choke between VREF2 and the input of the FM section prevents the antenna signal being short-circuited by the 0.0022 μF decoupling capacitor to ground.

The 2.2 μH choke following the 0.1 μF coupling capacitor at the AM output presents a very low impedance to AM signals, but a very high impedance to VHF signals.

[980031]

TEMIC U.K. Ltd.

Easthampstead Road
Bracknell, Berkshire RG12 1LX
United Kingdom


Tel: 44 1344 707 300

Fax: 44 1344 427 371

stage-lighting control

with DMX512 protocol

Before the computer age, it required quite a number of assistants to control the stage lighting in a theatre. Today, however, even here the computer has proved its usefulness as a tool. With the DMX512 (**D**igital **M**ultiple**X** for 512 units) standard, a computer can control the entire lighting system, including ancillary functions such as the colour filters and dimmers. In this setup, a simple interface cable enables the computer to control up to 512 separate lighting units.

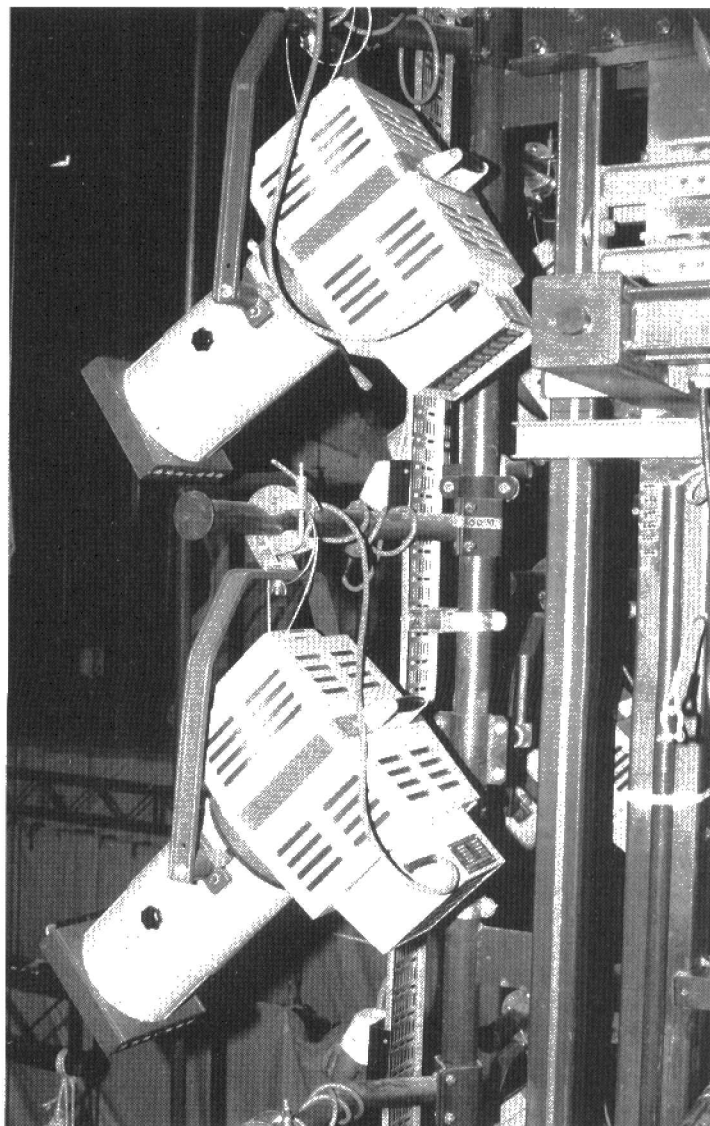

Some of us theatre-goers may remember the large theatre lights that were manually operated. Each light required at least a pair of hands – a labour-intensive and therefore costly affair. When electronic control units, and later the computer, became available, many theatres adopted analogue lighting control systems that were much simpler to operate, and therefore more cost-effective.

However, over the past ten years or so, digital control systems controlled by computer have become the norm.

In most smaller theatres, the set of instructions developed for the United States Institute for Theatre Technology (USITT), code-named DMX-512, has been adopted. This is an efficient, yet simple, digital protocol, accepted in many parts of the world, which enables all aspects of the stage lighting to be controlled by a computer.

IN TIMES GONE BY...

In the early years of (analogue) electronic control units, an analogue signal was required for each control channel,

By our Editorial Staff

that is, each lighting function that had to be controlled. What's more, a separate cable or pair of wires in such a cable was needed for each of these functions. This cable had to distribute linear control voltages of 0–10 V according to an internationally accepted set of rules. Evidently, although this is a practical setup when there are not all that many lights involved, it becomes cumbersome and costly when many lights are to be controlled, because it results in many or very thick cables. However, for the technicians involved, the use of low voltages means that it is a safe system that can be checked with a simple multimeter.

With the increase of technical facilities whereby modern projectors fulfil more and more functions, the analogue system becomes more and more impracticable. Each piece of equipment needs several channels, which makes the cabling ever more complicated. Today, some lighting units provide 25–30 functions.

In larger theatres, these difficulties with analogue systems led in the early 1980s to the introduction of digital control systems, which in the mid-1980s resulted in the USITT adopting the digital DMX-512 standard. In this system, each pair of wires can control up to 512 functions. In practice, of course, the number is restricted to 32. However, each unit being controlled may use several channels at a time, so that a fair amount of the total available capacity is used.

Although the DMX-512 protocol is not new, it may not be known to many readers. Moreover, a successor is already being developed: the DMX-B. Fortunately, the new set of standards is backwards compatible with the DMX-512, so that older equipment remains usable.

EFFICIENT AND EFFECTIVE

The DMX-512 Standard was last modified and officially laid down as a


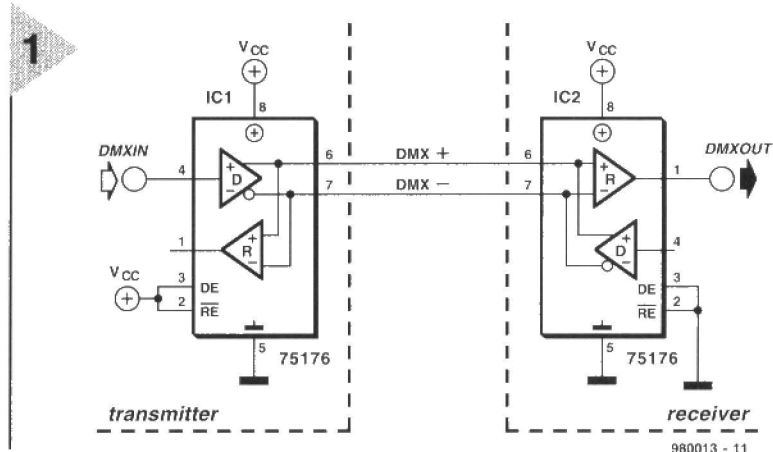


Figure 1. Basic layout of a simple transmitter and receiver used in the DMX-512 system. The driver is a standard driver for the RS485 system and is readily available.

norm by the USITT in 1990. It is based on the much more widely used RS485 Standard. A basic layout of a DMX-512 link between transmitter and receiver, both of which use the same driver, is shown in Figure 1. Interconnection is via a symmetrically controlled pair of wires.

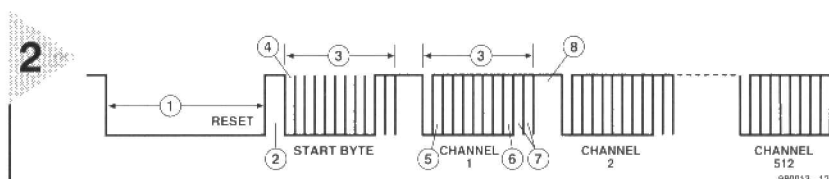The data are transmitted asynchronously serially over the wires. The settings are sent sequentially, that is, first the level for dimmer 1, then that for dimmer 2, and so on, until the levels for all connected dimmers (up to 512)




no.	name	min.	typ.	max.	unit
1	reset		88	88	μs
2	mark	8	-	1	μs
3	frame	43.12	44.0	44.48	μs
4	start bit	3.92	4.0	4.08	μs
5	LSB	3.92	4.0	4.08	μs
6	MSB	3.92	4.0	4.08	μs
7	stop bit	3.92	4.0	4.08	μs
8	mark (between frames)	0	0	1.00	s
9	mark (between trains)	0	0	1.00	s

Figure 2. The timing diagram shows the maximum width of a data block with which up to 512 lighting units can be controlled. In this setup the repetition rate is 44.1 Hz.

How to make a terminator

Terminators are of great importance to ensure good and reliable communication, but, owing to their small size, are easily mislaid. It is, therefore, useful, to be able to make one at low cost.

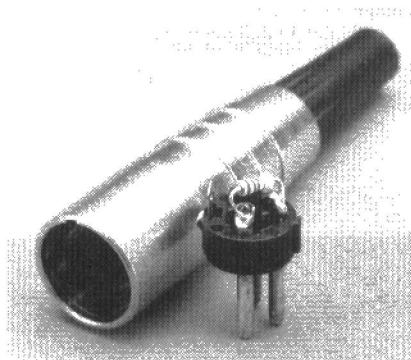Remove the hood from an XLR plug and solder a 120 Ω, 0.25 W resistor between pins 2 and 3, and replace the hood. That's all! The photograph shows a completed terminator.



3

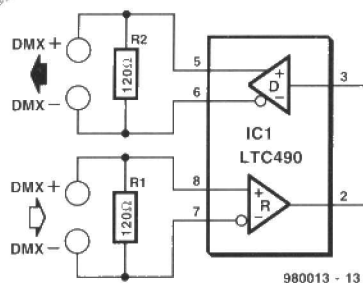


Figure 3. When lines longer than about 1 metre are needed, a bus repeater as shown will be essential.

have been sent.

The reset pulse is followed by a mark signal that indicates the onset of communication. Normally, the mark signal must be at least $8\mu\text{s}$ long, but there are systems which are able to recognize a mark-to-break width of $4\mu\text{s}$; these are coded DMX-512/1990 ($4\mu\text{s}$).

The onset of a cluster of bytes is marked by a reset signal that is followed by a start byte. This is followed by the brightness data for the first dimmer in the shape of an 8-bit value 0–255, that is, 00_{16} – FF_{16} . The relationship of this value with respect to the present brightness setting is a matter for the dimmer itself. For instance, the manufacturer of the dimmer may give it a control curve according to which its brightness increases or decreases. In

4

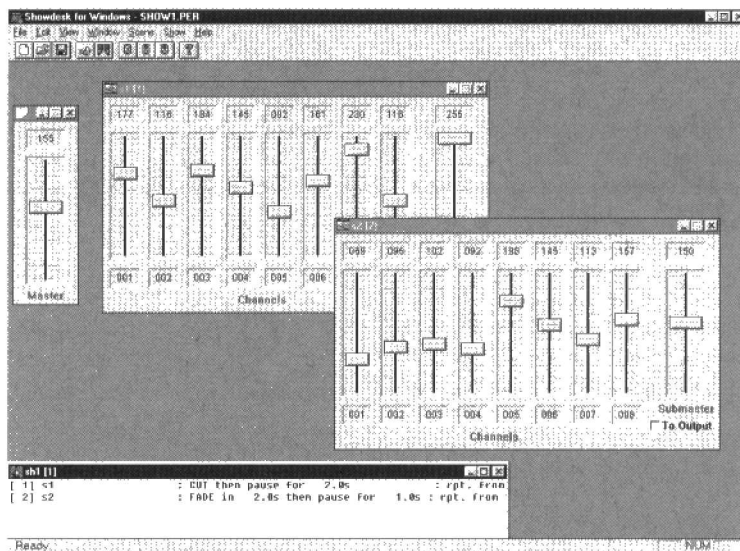


Figure 4. To get a better idea of the facilities provided by the DMX-512 standard, download a demo version of ShowDesk from web site <http://www.fpltd.com>

the case of lamps whose brightness must change rapidly, use may be made of a shutter; the DMX-code then arranges the opening and closing of the shutter.

Each DMX-512 instruction consists of a start bit, eight data bits, and two stop bits (one frame). In the quiescent state, the level on the communication line is high (mark), whereas the active level is low (break or space). The break signal itself is not less than $88\mu\text{s}$ wide, a time that corresponds to two frames. The system recognizes the break as a reset signal, whereupon all current operations are dis-


continued.

The next step is the transmitting of a number of $n+1$ frames, each of which contains the setting of one of the connected dimmers. The first transmitted frame, that is, the start byte, marks the onset of the series of commands and has a fixed value 00_{16} . This indicates that the settings refer to the dimmers. Because of this start code, standards that use a different start code for controlling other types of unit may be added at a later date. For

this reason, the connected dimmers must not react when the communication is

Figure 5. A modern control room from where the lighting manager controls the stage lighting resembles a computer centre.

5

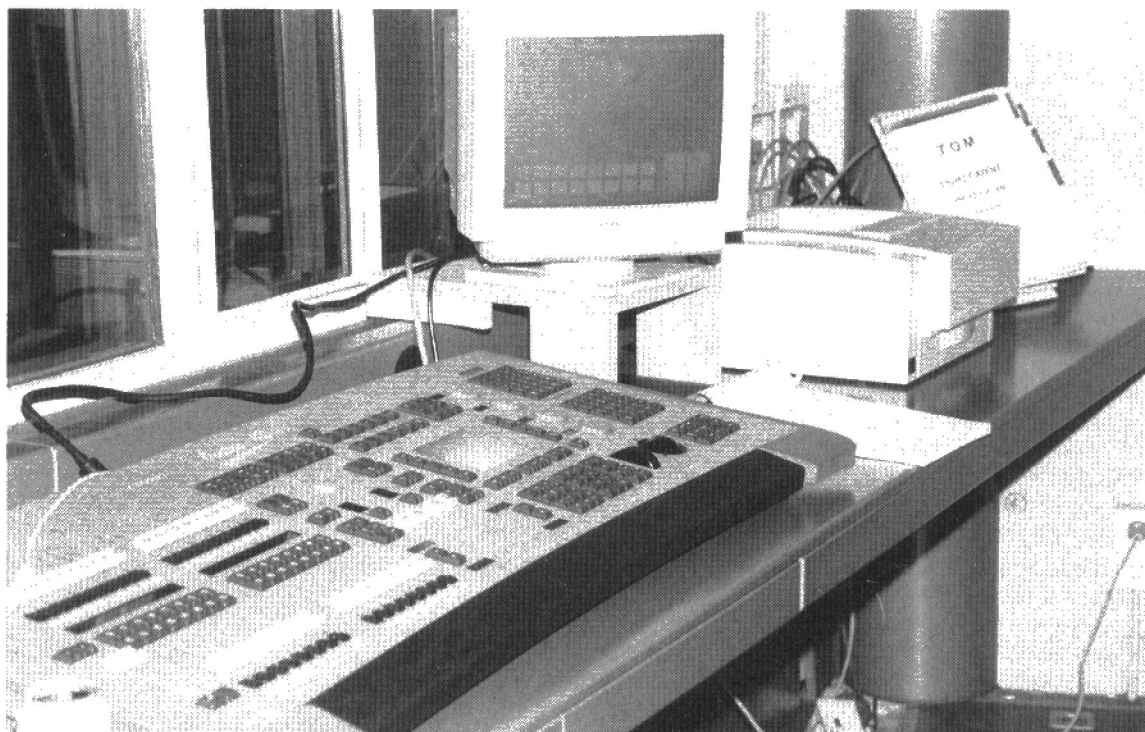

6

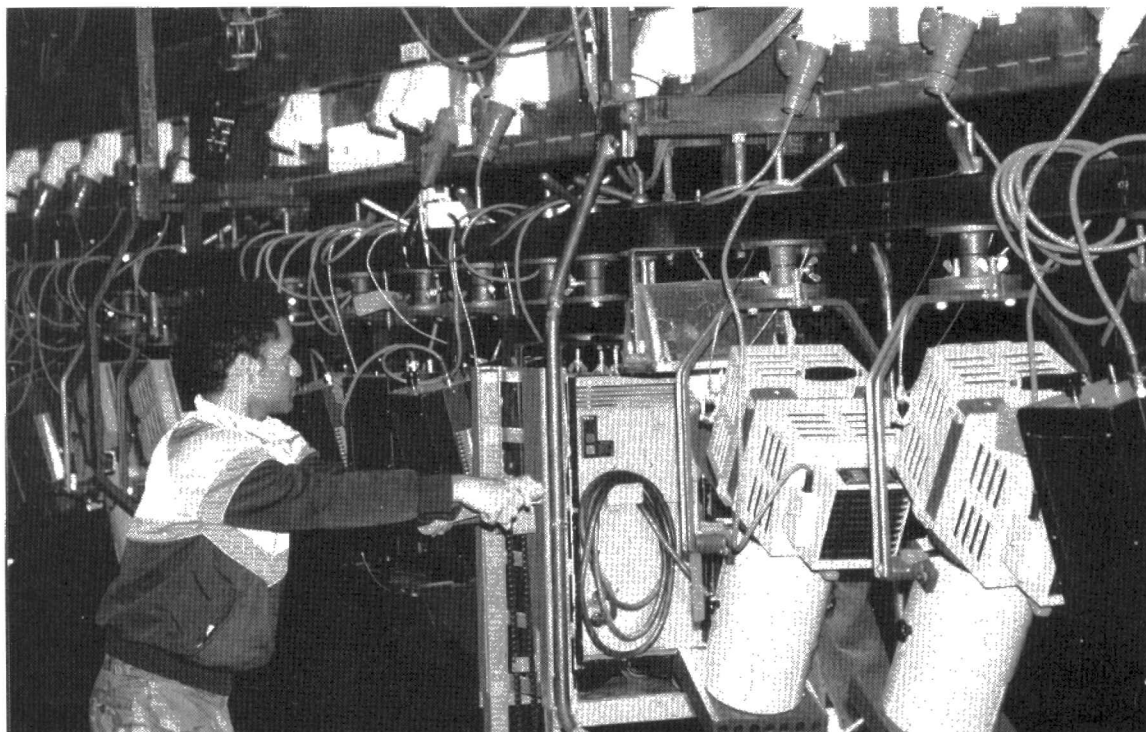


Figure 6. Modern theatre lights may have more than 25 functions. For each of these functions, the light uses a DMX address.

begun with a start code other than 00_h.

TIMING

As mentioned earlier, the DMX-512 standard supports up to 512 dimmers; a minimum is not stipulated. After the data has been transferred to the final dimmer in the chain, the data line returns to the quiescent state (mark). The next reset signal indicates that a new transfer of data is imminent. It is imperative that two sequential setting instructions are separated by an interval (pause) of not less than 1196 μ s.

The data rate in the DMX-512 standard is 250 kbit/s. Since one bit lasts for 4 μ s, a complete instruction, including the stop and start bits, takes 44 μ s. The timing diagram in Figure 2 shows a complete sequence of 512 bytes, the data stream required for the theoretical maximum of 512 dimmers. When all times are added, the maximum time duration is 22,668 μ s, which corresponds to a repetition rate of 44.1 Hz. From this, it is clear that the use of the maximum number of dimmers restricts the speed of operation.

The DMX-connection allows 32 lighting units to be linked to the bus. There is no limitation as to the number of addresses that each of these units can handle.

CABLES AND ALL THAT

The cables carry rectangular-wave signals at a frequency of 250 kHz maximum. Each signal may contain com-

ponents at frequencies up to 2.5 MHz. This means that in the DMX system cables must be used that are quite different from the ones used in analogue systems. No longer can standard cable with simple connectors be used: specific types of cable with corresponding connectors are imperative.

As mentioned earlier, the system is based on the RS485 interface, which is an improvement of the earlier RS422 system. The improvements make possible more connections to the bus and additional space for more masters. The latter facility is not used in the DMX512 system, but the former enables applications within a network. Although the RS485 standard limits the length of the cable, exceeding the specified length within reason will not create difficulties: distances of up to 1 metre (3.3 ft) are perfectly usable, provided that the final unit in the chain is terminated correctly into an impedance of 120 Ω .

If larger distances need to be spanned, a bus repeater should be used. The circuit of such a repeater is shown in Figure 3. Note that both the input and output are terminated into 120 Ω . The DMX-512 standard does not specify the electrical isolation.

SOME LIMITING VALUES

It is important that the driver can handle signal levels between 1.5 V and 5 V at a common-mode potential between -7 V and +12 V.

The leakage current at the output should not exceed 100 μ A during an output signal.

The input impedance of the receiver must be not lower than 12 k Ω , while the output load must not exceed 60 Ω .

Short-circuit currents of 150 mA to earth and 250 mA to the positive supply line are permissible.

This article is based on information available in the relevant Internet information from Soundlight (<http://www.soundlight.de/techtips/dmx512/dmx512.htm>).

[980013]


Pinout of connectors used

5-way AXR (XLR) plug

pin	function
1	earth (screen)
2	DMX-
3	DMX+
4	n.c. (may be linked to DMX-)
5	n.c. (may be linked to DMX+)

3-way AXR (XLR) plug


pin	function
1	earth (screen)
2	DMX-
3	DMX+

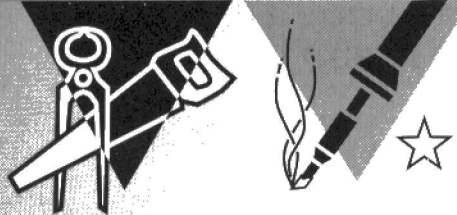

functional trinket

reacts to sound pressure

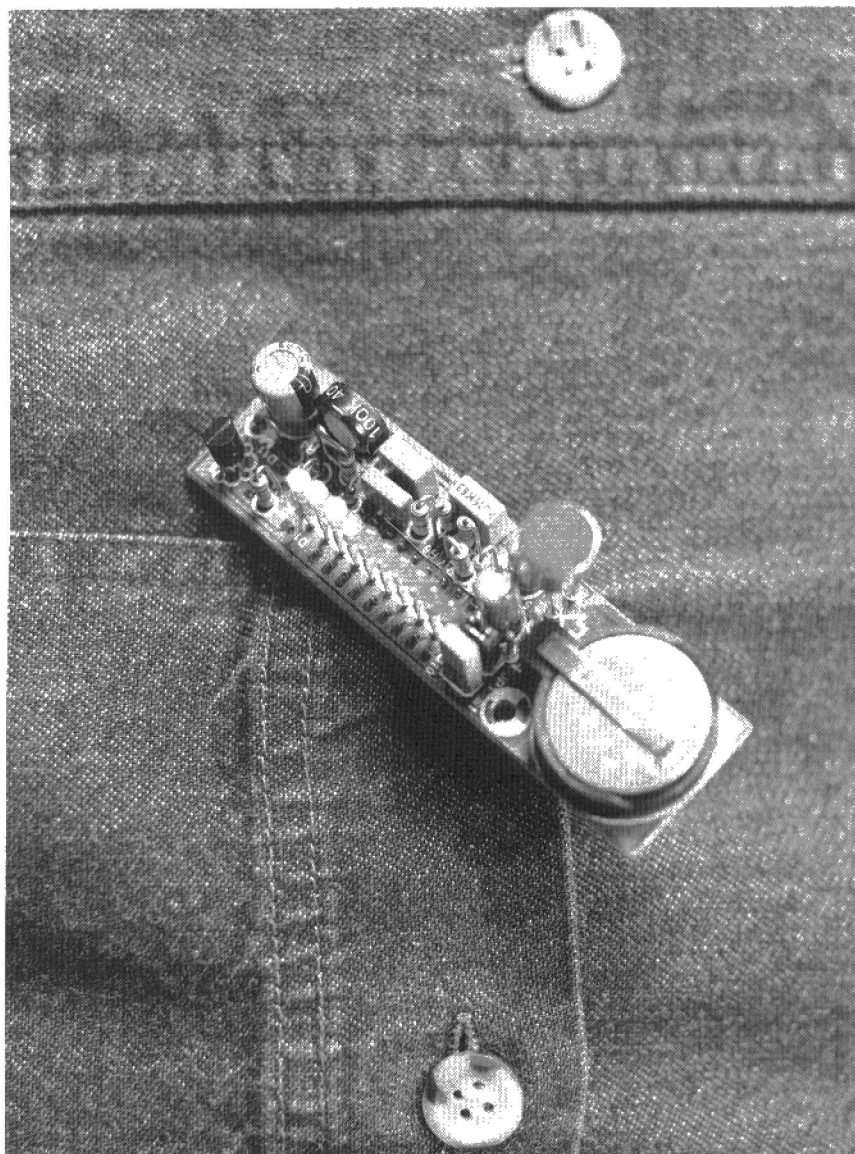Strictly speaking, a trinket cannot be functional, but the title of this article is apt. It is a kind of miniature VU meter whose LED bar fluctuates in rhythm with ambient sound. Owing to its modest dimensions, it can easily be worn as an adornment which, in a disco or at a party, will, no doubt, draw the attention of many.



Nowadays, not many things surprise us any more. In this age of high technology, we are used to all kinds of new discoveries and developments, and technical ingenuity. Mobile telephones, portable CD players, watches with built-in alarm: what is there left to impress us with? Not only satellite TV, but also a radio-controlled vehicle on


the planet Mars are accepted as a commonplace.

Of course, this is true not only in the world of science and technology, but also in other spheres of human interest. It is not easy to dream up something really new or innovative – something that draws a spontaneous reaction of “Fancy that” or “How do

Design by T. Giesberts



2

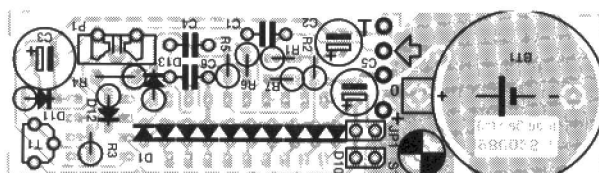

time from a small, low-voltage battery.

The final design is shown in **Figure 1**. The sound is picked up by a tiny electret microphone MIC₁. It has a diameter of about 10 mm (0.4") and contains an integrated impedance equalizer that also functions as amplifier. The supply line to this amplifier is set by R₁ to just under half the supply voltage (test point A). The output of the microphone is applied to sensitivity control P₁ via capacitor C₁.

The signal at the wiper of P₁ is applied to operational amplifier IC₁. This stage has a twofold function: amplifier and, in conjunction with D₁₂ and D₁₃, single-phase rectifier. Its amplification is determined by the ratio R₃:R₄; with values as specified, it amounts to $\times 6$. This results in a direct voltage at its output (pin 6) that varies in accordance with the strength of the signal picked up by the microphone. This voltage is averaged to some extent by network R₆-C₄ to prevent very rapid fluctuations, which would lead to an unstable display.

The display is formed by a bar of ten LEDs that are controlled by the well-known Type LM3915 driver (IC₂). The driver comprises a voltage reference source, an accurate potential divider and ten comparators, each of which can control an LED directly. The potential difference between two successive LEDs corresponds to a sound pressure difference of 3 dB.

The direct voltage applied to pin 5 of IC₂ can be converted to a single, wandering LED (dot mode) or to a fluctuating bar display (bar mode) via pin 9. In the dot mode, the contacts of jumper JP₁ must remain open; in the bar mode, they should be closed.

CONSTRUCTION

The design of the printed-circuit board in **Figure 2** is a compromise between small size and ease of construction. This has been accomplished by accommodating IC₁ and IC₂ on the track side of the board instead of as normal on the component side. Note that soldering these components requires a small soldering iron with a very fine tip.

The circuit is powered by a 3 V lithium cell that is fitted on to the board with the aid of a specially available holder. Note that the +ve terminal must point upward.

The microphone is soldered directly to the pins marked with an input arrow.

On/off switch S₁ may be replaced (as it is in the prototype) by a jumper, which is smaller than a switch.

Note that D₂-D₁₀ are all placed in the same direction, but D₁ the other way around.

FINALLY

The completed prototype board is

3

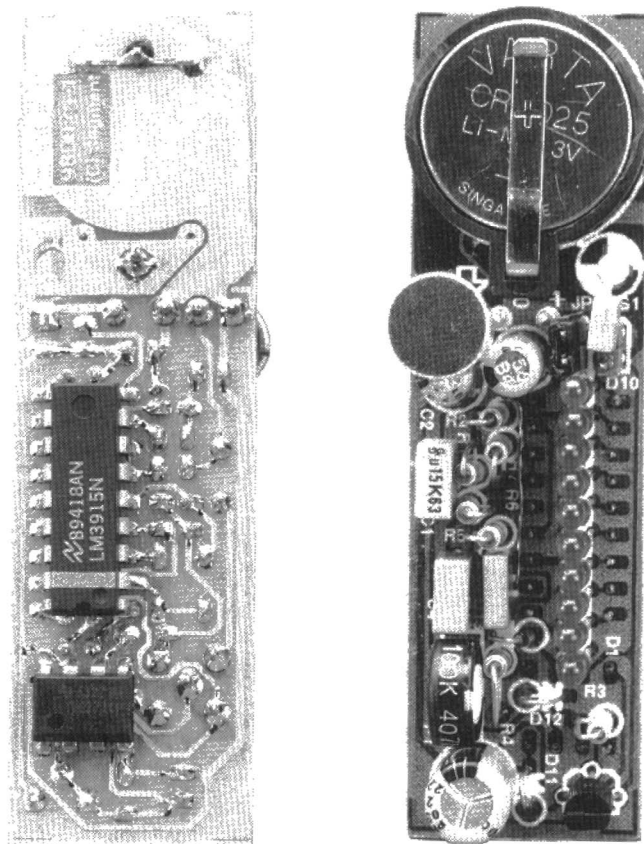


Figure 3. Both sides of the completed prototype board. Soldering the ICs in place requires a steady hand and a fine-tipped soldering iron.

shown in **Figure 3**. A clip to enable the board to be fastened to a lapel or similar may be soldered or glued at the underside near the battery (if soldered, take care not to cause a short-circuit).

There are, of course, other possibilities of construction: for instance, the LEDs may be clustered together away from the board (which can then be hidden in, say, a breast pocket). The two sections can then be linked by a mini cable. Ingenious readers can, no doubt, think of different constructions.

The LEDs specified have a small outer edge. This edge must be filed or cut away with a sharp knife to enable these diodes to be placed close together on the board.

Although problems are highly unlikely, the voltage level at three test points is given in the circuit diagram to facilitate faultfinding.

Depending on the type of microphone used, it may be necessary to change the value of R₁ to obtain a voltage of 1 V at test point A. If this is done, it is advisable to check the offset

at the output of the op amp across pins 4 and 5 of IC₂ (without microphone). If this is higher than 100 mV, it is advisable to replace IC₁.

The sensitivity of the circuit with a standard electret microphone and P₁ set to maximum is arranged to give a full display for a sound pressure input level of 100 dB. Note that a sustained input at this level is dangerous for your hearing. If the sensitivity is considered insufficient, it may be increased by giving R₃ a value of 1.5 k Ω or even 1.2 k Ω .

BATTERY

The circuit draws a current of about 6 mA with all LEDs out, about 12 mA in the dot mode, and up to 22 mA with all LEDs on in the bar mode. Since a Type CR2025 battery has a capacity of 120 mAh, and a CR2032 one of 170 mAh, the trinket will continue to light even when the party lasts until the early hours – certainly in the dot mode.

[980025]

READERS SERVICES

ELEKTOR ELECTRONICS

FEBRUARY 1998

GENERAL

Printed-circuit boards (PCBs), self-adhesive front panel foils, ROMs, EPROMs, PALs, GALs, microcontrollers and diskettes for projects which have appeared in *Elektor Electronics* may be ordered using the Order Form printed opposite. The form may also be used to order books (private customers only).

- » If no product description is given, then the item is a ready-made printed circuit board (PCB).
- » Items not listed here may not be available any more.
- » The artwork for making a PCB which is not available ready-made through the Readers Services may be found in the relevant article.
- » EPROMs, GALs, PALs, (E)PLDs, MACHs, PICs and other microcontrollers are supplied ready-programmed.

Prices and item descriptions subject to change. The publishers reserve the right to change prices without prior notification. **Prices and item descriptions shown here supersede those in previous issues.** E. & O.E.

PAST ISSUES

Past issues, if available, should be ordered from **Worldwide Subscription Service Ltd, Unit 4, Gibbs Reed Farm, Pashley Road, TICEHURST TN5 7HE, England, telephone (+44) 1580 200657, fax (+44) 1580 200616, email www.subscription@virgin.net.**

Prices of past issues (except July/August and December), including postage for single copies, are £3.20 (UK and Eire); £3.50 (surface mail outside UK); £3.75 (air mail Europe); £4.50 (airmail outside Europe). Prices of past July/August and December issues, including postage for single copies, are £4.25 (UK); £4.50 (surface mail outside UK); £4.75 (airmail Europe); and £5.50 (airmail outside Europe).

PAST ARTICLES

For information on past articles, please contact our Editorial and Administrative Office in Dorchester, telephone (01305) 250995; fax 250996, email elektor_uk@compuserve.com.

Article title or item	Order code	Price £	Price US\$
-----------------------	------------	---------	------------

SPECIAL PRODUCTS

ELEKTOR ELECTRONICS ITEM TRACER 1985-1997. (on 3.5-inch floppy disk) 986011-1 10.00* 20.00*
* reduced price for subscribers. Normal price: £11.75 or US\$23.50.

ELEKTOR ELECTRONICS µP-µC HARDWARE & SOFTWARE 97-98 ON CD-ROM.
Compilation of 100+ prize-winning entries in the 1997 Microprocessor Design Competition. Disclaimer: software supplied as is, not tested by Elektor 986001-1 16.50 33.00

ELEKTOR ELECTRONICS DATASHEET COLLECTION 1 ON CD-ROM 16.50 33.00

ELEKTOR ELECTRONICS VOLUME 1996 ON CD-ROM, incl. Electronics Workbench working demo 31.50* 63.00*
* reduced price for subscribers. Normal price: £35.50 or US\$71.00

ELEKTOR ELECTRONICS VOLUME 1995 ON CD-ROM 37.00* 74.00*
* reduced price for subscribers. Normal price: £41.00 or US\$82.00

ELEKTOR ELECTRONICS SOFTWARE COMPETITION 1996/97 ON CD-ROM.

Compilation of all prize-winning entries. Disclaimer: software supplied as is, not tested by Elektor 976003-1 15.75 31.50

ELEKTOR ELECTRONICS HELP DISK.

Component colour band decoder software on 3.5-inch disk 966022-1 10.00 20.00

FEBRUARY 1998

Frequency Display & VFO Stabilizer:
- PCB only 980004-1 9.75 19.50
- PIC only 986502-1 14.25 28.50
- Disk only 986006-1 6.25 12.50
AVC for PCs 980023-1 11.00 22.00
Functional Trinet 980025-1 7.00 14.00
Light Intensity Measurement with a PC:
- Disk only 986002-1 7.25 14.50
JFET Tester Not Available
Simple Electronic Metronome Not Available

JANUARY 1998

Portable Sound Pressure Meter 970085-1 9.25 18.50
Stereo Microphone Input Adaptor for PC 980007-1 9.75 19.50
Electronic Die 980021-1 7.00 14.00

DECEMBER 1997

Running Lights for Christmas:
- PCB & 8751 970086-C 28.25 56.50
- 8751 only 976517-1 19.00 38.00
Handyman/AT90S1200 Programmer:
- Docking station PCB, shuttle PCB, diskette 970090-C 20.25 40.50
- Docking station PCB only 970090-2 7.50 15.00
- Handyman shuttle PCB only 970090-1 4.25 8.50
Diskette only 976017-1 11.75 23.50
Smartcard Reader/Writer
- PCB, disk & PIC16C84 970068-C 35.00 70.00
- PIC16C84 only 976512-1 19.50 39.00
- Disk only 976014-1 8.75 17.50

Article title or item	Order code	Price £	Price US\$
-----------------------	------------	---------	------------

PIC Controlled Light Barrier:
- PCB Not Available
- PIC only: 976503-1 14.75 29.50

NOVEMBER 1997

Hygrometer 970065-1 11.00 22.00
Video Copy Processor:
- PCB & EPM7032 970066-C 34.75 69.50
- EPM7032 only 976514-1 27.50 55.00
Stereo Microphone Amplifier 970083-1 19.25 38.50
PC as 4-channel Logic Analyser:
- PCB Not Available
- software on disk 976012-1 8.75 17.50

OCTOBER 1997

4-Way Serial Port Switch 970057-1 12.00 24.00
12-bit ADC Interface:
- PCB and disk 970060-C 10.50 21.00
- Disk only (also for CPU Thermometer) 976011-1 5.75 11.50
Infra-red Controlled Noise-less Volume Control Frequency Meter and Event Counter Module:
- PCB and PIC16C56 970077-C 34.25 68.50
- PIC only 976505-1 25.50 51.00
DC Nullifier for Oscilloscope Input:
- PCB 970063-1 12.50 25.00
- P25032 CPLD chip 976513-1 20.25 40.50
- Disk only 976016-1 5.00 10.00
Directional Microphone 970079-1 8.25 16.50

SEPTEMBER 1997

Data Acquisition System:
- PCB, EPROM and disk 970059-C 33.00 66.00
- PCB only 956510-1 12.25 24.50
- disk only 956010-1 8.75 17.50
Centronics Relay Card 970053-1 11.25 22.50
Dual Continuity Tester 970020-1 7.50 15.00
Chipcard Reader/Programmer:
- PCB and disk 970050-C 13.50 27.00
- disk only 976010-1 8.50 17.00

JULY/AUGUST 1997

RGB Video Amplifier 974042-1 12.25 24.50
Digital Tester 974012-1 13.25 26.50
LM2574 Switch-Mode Power Supply 974024-1 7.50 15.00
Selective Door Chime 974025-1 8.50 17.00
Yamaha DB50XG Stand-Alone Soundcard 974100-1 14.75 29.50

JUNE 1997

80C537 Microcontroller Board:
- PCB, GAL & EPROM 970048-C 58.00 116.00
- GAL only 976511-1 14.75 29.50
- EPROM only 976510-1 14.00 28.00
- Monitor doc file on disk 976008-1 8.00 16.00
Remote Control by Telephone:
- program on disk 976005-1 8.75 17.50
Earth Leakage Meter 970046-1 13.25 26.50
Car Battery Monitor 970025-1 16.50 33.00

Extra: supplement on microprocessors

Multi-Purpose LCD with 68HC11:
- control program on disk 976009-1 11.25 22.50
Mini PIC Programmer and Mini Programmer for Serial EEPROMs

Article title or item	Order code	Price £	Price US\$
- PIP02 software on disk	978007-1	5.50	11.00
MAY 1997			
Long-Distance I/O Link: - PCB & 89C2051 970041-C 25.25 50.50 - 89C2051 only 976508-1 17.50 35.00			
Advanced LCR Meter: - PCB, GAL & EPROM 970028-C 62.50 125.00 - GAL 22V10 976506-1 26.50 53.00 - EPROM 27C512 976507-1 7.75 15.50 - Front panel foil 970028-F 13.50 27.00 Wideband Millivolt Meter 970021-1 21.50 43.00 Compact Power Amplifier 970043-1 19.75 39.50			

APRIL 1997

Digital Thermostat:
- PCB & PIC16C54 960112-C 32.50 65.00
- PIC16C54 only 966501-1 22.50 45.00
µP-Controlled Mixer Board:
- PCB & ST62T25B 970037-C 32.75 65.50
- ST62T25B only 976502-1 24.50 49.00
- PCB only 970037-1 10.25 20.50
- Software on floppy (AD) 976006-1 6.00 12.00
PIC-controlled Home Alarm System:
- PCB & PIC 16C84 970022-C 30.50 61.00
- PIC16C84 only 976501-1 23.50 47.00
General-Purpose Power Supply 970036-1 8.50 17.00
Opto-to-Coaxial Audio Converter 970031-1 7.00 14.00

MARCH 1997

EPROM Programmer:
- PCB 970010-1 15.75 31.50
- Control software on CD-ROM no. 976003-1
Battery-Operated AF Signal Generator 970003-1 10.00 20.00

FEBRUARY 1997

Battery-Powered Preamplifier 960094-1 34.25 68.50
Motor Controller for R/C Models:
- PCB and PIC16C84 960095-C 22.75 45.50
- PIC 16C84 only 966510-1 19.00 38.00
68HC11 Emulator:
- PCB and diskette 970008-C 28.00 56.00
- Diskette only 976002-1 11.25 22.50
Simple Inductance Meter:
- PCB and diskette 970009-C 15.25 30.50
- Diskette only 976001-1 8.75 17.50
Talking Doorbell 970015-1 10.50 21.00

JANUARY 1997

Dongle Switch 960089-1 7.00 14.00
Magnetic-Field Meter 960100-1 8.50 17.00
Speed Regulator for Model Trains 960113-1 8.50 17.00
Monitor to Guard Fridge Temperature 970001-1 8.00 16.00

DECEMBER 1996

20-bit A/D converter 960110-1 22.75 45.50
Remote Control by Visible Light 960068-1 11.00 22.00
Primary-Battery Refresher 960106-1 11.25 22.50
RS232 data acquisition card:
- PCB, PIC and disk 960098-C 35.50 71.00
- disk only 966019-1 7.25 14.50
- PIC 16C71 only 966508-1 24.00 48.00
Hands-On Electronics:
- MicroCap V demo disks 966021-1 4.00 8.00
Electrically Isolated I²C bus 964062-1 6.75 13.50
Centronics I/O Port 964116-1 18.50 37.00
Mains Voltage Cleaner 964070-1 10.25 20.50

NOVEMBER 1996

ST62 Programmer:
- PCB and disk 960105-C 16.75 33.50
- PCB only 960105-1 12.75 25.50
- disk only 966018-1 6.00 12.00
Hands-On Electronics:
- MicroCap V demo disks 966021-1 4.00 8.00
Headphones Amplifier 960109-1 6.25 12.50
50W A.F. Amplifier 960079-1 8.00 16.00
Infra-red RS232 Link:
- PCB and disk 960107-C 15.25 30.50
- disk only (Temic files) 966020-1 8.00 16.00
Steam-Engine-Noise-Generator 960087-1 7.75 15.50

OCTOBER 1996

Video Test Chart Generator:
- PCB, EPROM and disk 960076-C 79.50 159.00
- EPROM 966507-1 39.00 78.00
- EPROM 27C040 966507-2 24.50 49.00
- Disk only 966011-1 7.00 14.00
Mini Flash Programmer:
- PCB and software (disk) 960078-C 21.25 42.50
- Software only (disk) 966015-1 12.25 24.50
Mini Metal Detector 960075-1 5.50 11.00
Darkroom Timer 960086-1 11.75 23.50
Sampling Rate Converter:
- PCB and ST62T10 960093-C 28.75 57.50
- ST62T10 (IC2) 966511-1 19.50 39.00
Thrifty Crystal Oven 960071-1 12.75 25.50
Electric-Bulb Tester 960091-1 6.00 12.00
Multi-Purpose Paspari: I/O Unit (disk only) 966013-1 7.00 14.00

SEPTEMBER 1996

Digital maximum thermometer:
- PCB and ST62T10 960010-C 27.75 55.50
- ST62T10 (IC1) 956515-1 19.50 39.00

Article title or item	Order code	Price £	Price US\$
Standby Unit for TV Economy Digital Compass 960063-1		12.00	24.00
RS232-Interface for A/D Converter ICL7106: - software on disk 966016-1		6.00	12.00
JULY/AUGUST 1996			
Continuity Tester UPBS-1		1.95	3.90
Symmetrical Power Supply UPBS-1		1.95	3.90
50-MHz dBm Meter 964039-1		16.50	33.00
Precision Battery Capacity Meter 964040-1		8.00	16.00
Video Fader 964076-1		12.25	24.50
Inexpensive AD/DA Converter: - PCB 964092-1		Not Available	
- software on disk 966009-1		7.00	14.00
Single-Chip AF Power Amp 964104-1		6.25	12.50

JUNE 1996

Flash EPROM Programmer/Emulator:
- PCB + disk 960077-C 33.00 66.00
- disk only 966017-1 16.00 32.00
Keyboard Swap for PCs 950126-1 7.00 14.00
Stop that Barking! 960035-1 5.50 11.00
23cm ATV preamplifier 960072-1 7.50 15.00
Pulsimeter 960005-1 10.25 20.50
Burglar Deterrent Lighting 960022-1 7.25 14.50

MAY 1996

Digital VU meter (2):
- PCB + EPROM (946646-1) 950098-C 36.00 72.00
- EPROM 27C512 946646-1 17.75 35.50
Surround Sound Subwoofer (3):
- PCB 960049-1 16.75 33.50
Mains Voltage Monitor:
- PCB 960055-1 7.25 14.50
64-Channel Logic Analyser:
- main PCB, disk & IC4, IC5 960033-C 69.75 139.50
- IC4 ispLSI1016 966506-1 27.50 55.00
- IC5 ispLSI1016 966506-2 27.50 55.00
- disk (MSDOS) 966010-1 7.00 14.00
- extension PCBs (3-in-1) 960033-2 17.00 34.00
- IC20/30/40 ispLSI1016 966506-2 27.50 55.00

APRIL 1996

Centronics Interface:
- PCB + disk (966008-1) 960052-C 16.25 32.50
- Disk (Windows) 966008-1 6.00 12.00
PC-Controlled AF Analyser (2):
- Software on disk 966001-1 26.00 52.00

MARCH 1996

PIC-Controlled RDS Decoder:
- PCB + PIC (966505-1) 960050-C 27.50 55.00
- PIC 16C84 966505-1 22.75 45.50

FEBRUARY 1996

SIMM tester:
- PCB + EPROM (966503-1) 960039-C 28.25 56.50
- EPROM 966503-1 10.25 20.50
I²C Interface for Centronics port:
- PCB + disk (946202-1) 950063-C 20.25 40.50
- control software on disk 946202-1 12.25 24.50

JANUARY 1996

DECEMBER 1995
Micro PLC System:
- PCB + 87C750/51 + disk 950093-C 44.50 89.00
- 87C750/51 956514-1 24.50 49.00
- control software on disk 956016-1 10.00 20.00

NOVEMBER 1995


OCTOBER 1995
MatchBox BASIC computer:
- PCB, 87C51, disk and Quick Reference Card 950011-C 59.25 118.50
- 87C51 956508-1 43.50 87.00
- Course diskette (DOS) 956009-1 11.50 23.00
- Quick Reference Card 950011-P 3.25 6.50

SEPTEMBER 1995

HexFET power amp upgrade:
- amplifier PCB 930102 12.75 25.50

For availability of older items, please contact our Dorchester office.

Elektor Electronics slipcase

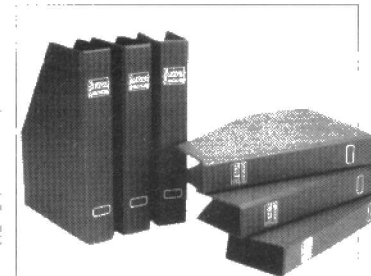

Price £2.95 + P&P £1.50 UK £2.00 outside UK

Experts Are Getting Smart...

that's why, at Smart, we have selected only the best products for you

New Windows based Universal Programmer

- For true Windows 3.1x and WIN 95 compatibility
- Programmes devices ranging from 8 pins to over 300 pins
- Supports over 3,000 different ICs – 3 volt and 5 volt variants
- Uses fast approved algorithms
- DOS version also available
- 30 day money-back trial period

Regular price £795.00


**SPECIAL INTRODUCTORY
PRICE £695.00**



PIC Emulator with Real Time Trace

- Supports PIC 12/16/17 Microcontrollers
- Real Time transparent emulation to 33MHz
- **3 and 5 volt support**
- Runs under DOS, Win 3.x or WIN 95
- Windows IDE supports your Assembler or Compiler
- External break probe – may be conditional with internal software breakpoints
- 8k by 24 bit real time trace buffer
- Complete system includes emulator, MPASM, software, cables, trace probes, etc...

Complete System from only £583.00

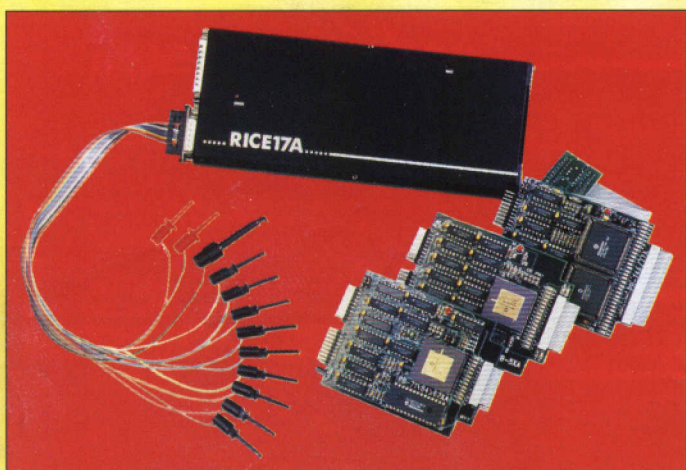

Low Cost Programmers

EMP-10

- Portable
- EPROM, E² PROM and Flash memories to 8 Mbits
- 8051 family including Atmel Flash
- Optional adaptor for serial E²PROM

**Only
£199.00**

EMP-20

- Portable
- Memories to 16Mbits
- 8051's and basic GALs
- Optional family modules for:
Serial E²PROMs and PSD's
Microcontrollers:
Microchip, Zilog, SGS, Intel, Motorola...
Programmable Logic:
AMD MACH, Xilinx, Altera, Lattice...

**Only
£350.00**

All prices exclude carriage and VAT.

To receive a brochure, register for the introductory offer or if you simply need free advice contact us –

Phone: +44 (0)181 953 9292 • Fax: +44 (0)181 953 9299

E-Mail: Sales@Smartcom.co.uk

Mail: Unit 11 Stirling Industrial Centre, Stirling Way, Borehamwood, Herts, WD6 2BT, England

Web visitors welcome: <http://www.Smartcom.co.uk>

EMULATORS • SIMULATORS • COMPILERS • ASSEMBLERS • PROGRAMMERS



SMART
COMMUNICATIONS

...the experts' expert